



# Understanding Design and Operation of Successive Approximation Register (SAR) ADC

---

ECE 614 - Spring '08

April 28, 2008

By Prashanth Busa




# Talk Outline

---

- Various ADC Architectures
- SAR ADC Introduction and Operation
- Charge Redistribution SAR ADC
- Different SAR ADC topologies
- Comparison with other ADCs
- Summary

# Various ADC Architectures

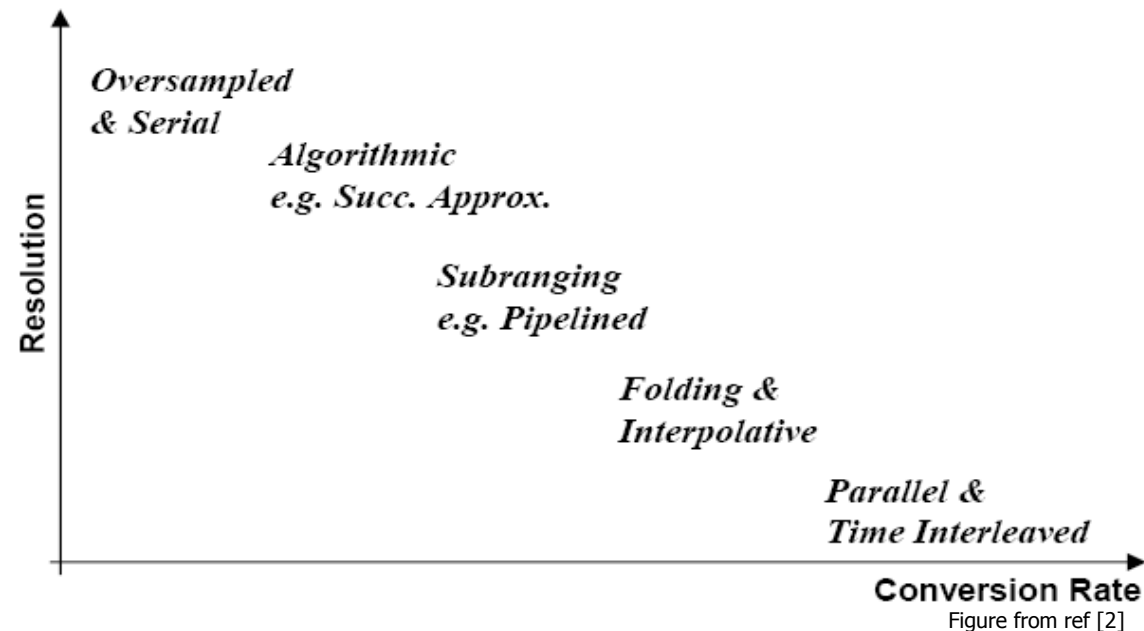

- Plot of Resolution vs Conversion rate.
- SAR ADCs are available from 8-18 bits resolution with sampling rates up to 5Msps.
- Higher accuracy, low power and used in medium speed/medium-high resolution applications.

# SAR ADC History

- ◆ 19" × 15" × 26"
- ◆ 150 lbs
- ◆ \$8,500.00



Courtesy,  
Analogic Corporation  
8 Centennial Drive  
Peabody, MA 01960

<http://www.analogic.com>

- First commercial converter, 1954 "DATRAC" 11-Bit, 50-kSPS SAR ADC Designed by Bernard M. Gordon at EPSCO.
- Today, the state of the art SAR ADC reported is 18 bit, 2Msps fully differential with a single power supply of 2.5v.

# Successive Approximation ADC


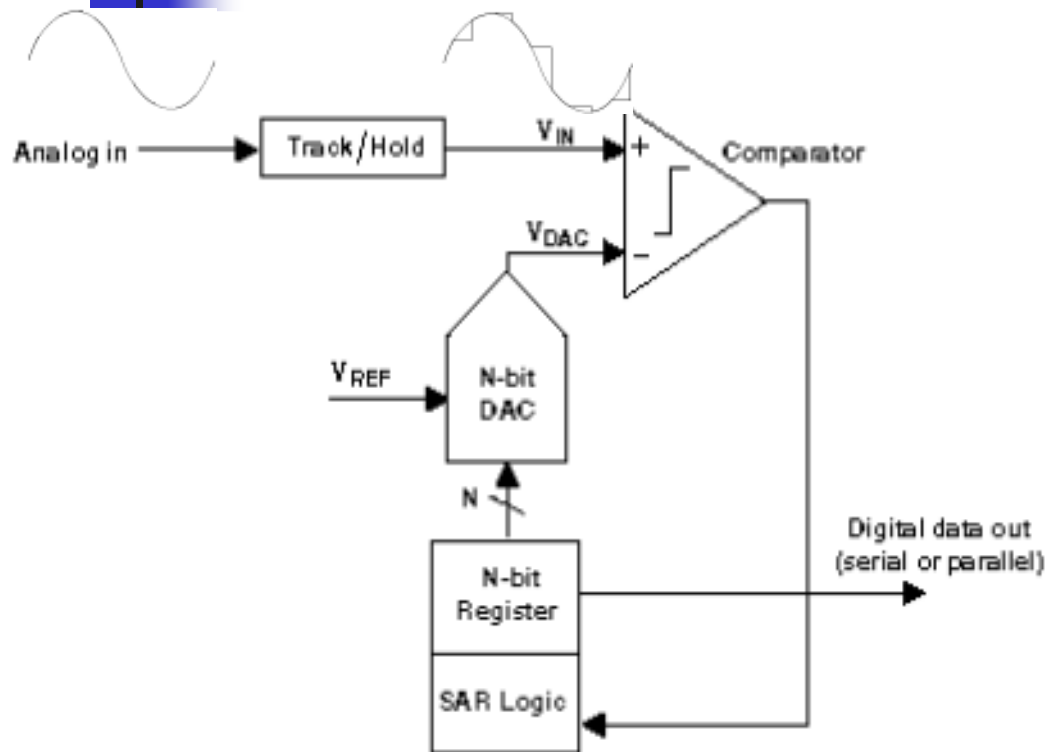


Figure from Maxim semiconductors ref [3]


Simplified SAR ADC Architecture

- Implements Binary search algorithm
- Initially, DAC input set to midscale (MSB = 1)
- $V_{IN} < V_{DAC}$ , MSB remains 1
- $V_{IN} > V_{DAC}$ , MSB set to 0
- Algorithm is repeated until LSB
- End of algorithm, DAC [input] = ADC [output]
- N cycles required for N-bit conversion

# SAR Operation

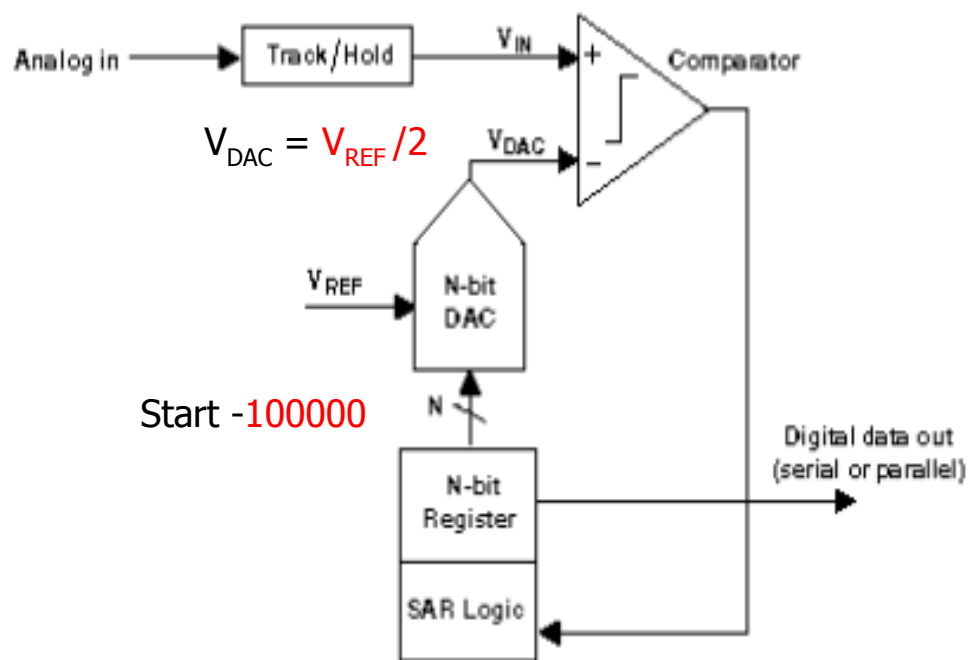

Simplified SAR ADC Architecture

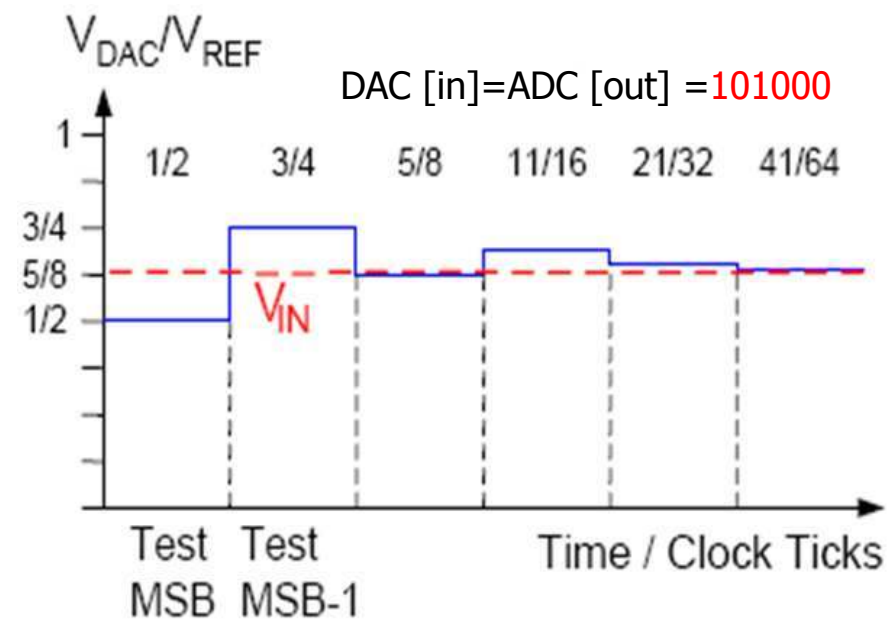

A 6-bit SAR ADC Example,  $V_{IN} = 5/8 V_{REF}$

# SAR Timing diagram


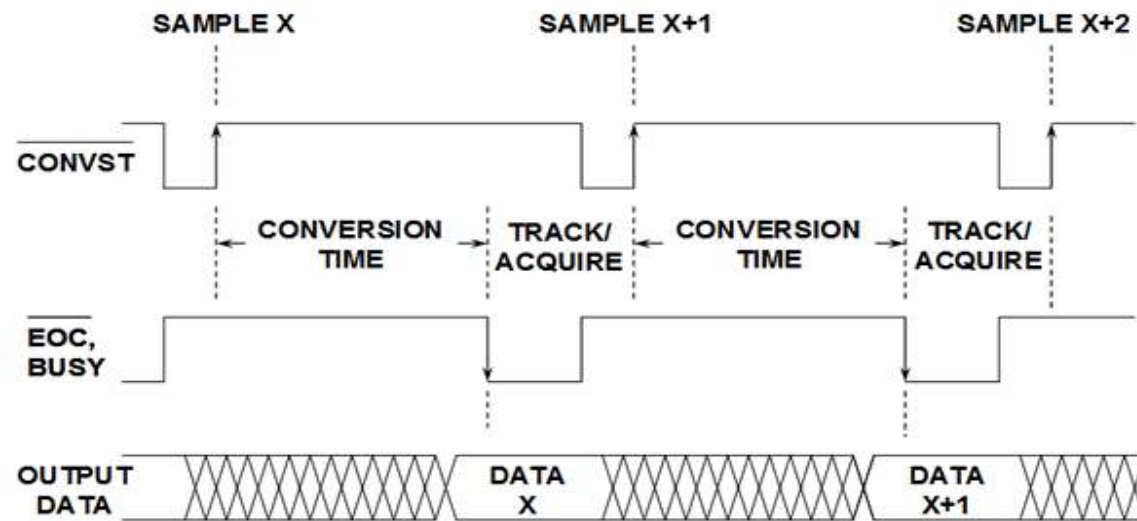


Figure from Analog Devices, ref[4]


- The positive going edge of  $\overline{\text{CONVST}}$  indicates the start of conversion, the input sample and hold is in the hold mode from this edge and various bits are determined using SAR algorithm.
- When  $\overline{\text{CONVST}}$  goes low the busy signal goes high and the BUSY line goes low at the end of conversion process.

# A simple Charge Redistribution DAC


Assuming  $C_1 = C_2$

 

 
Charging  $C_1$  to  $V_{ref}$ ,  $C_2$  grounded



 Discharging  $C_1, C_2$  –  $S_3$  and  $S_4$  closed




 Charge sharing  $C_1, C_2 \rightarrow V_O = V_{ref}/2$





 
## Simple Charge redistribution DAC cont'd



 
If bit = 1, S2 is closed  
= 0, S3 is closed



Depending on input,  
 $V_0 = (V_{\text{ref}}/2 + V_{\text{ref}}/4)$  for S2 closed (b=1)  
 $= V_{\text{ref}}/4$  for S3 closed (b=0)


Figures from ref[2]

# Charge Redistribution SAR ADC

 

- Provides inherent T/H operation.
- Initially,  $S_{reset}$  is grounded and all the capacitors connected to  $V_{IN}$ .
- MSB top plate is opened and MSB cap bottom plate connected to  $V_{REF}$  resulting in  $-V_{IN} + V_{REF}/2$  on the input of comparator.
- If  $-V_{IN} + V_{REF}/2 > 0$ , MSB = 0 else MSB = 1.
- Next cycle MSB-1 bit is connected to  $V_{REF}$ , algorithm is repeated until LSB.

# Charge Redistribution SAR ADC Cont'd..

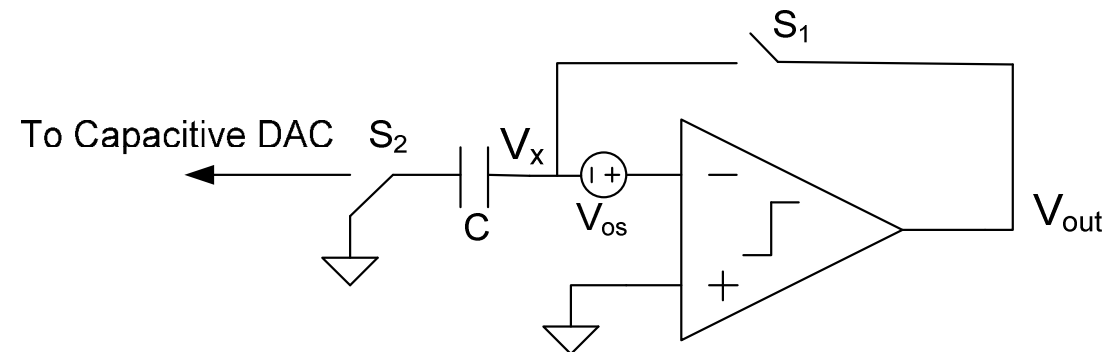

Comparator Offset Cancellation

- Comparator offset needs to be addressed.
- Switch  $S_1$  is closed,  $S_2$  is grounded, storing the offset voltage across the capacitor.
- Now,  $V_x > V_{os}$  results in  $V_{out}$  going high and  $V_x < V_{os}$  results in  $V_{out}$  going low.
- Parasitic capacitance on the top plate is not a concern due to the presence of global negative feedback.

# INL and DNL Calculations

- Linearity of the ADC depends on the capacitor ratio (matching).
- Process should have good capacitors.
- INL is defined as,  

$$|INL|_{\max} = 2^{N-1}(C + |\Delta C|_{\max, INL}) - 2^{N-1} C = 2^{N-1} |\Delta C|_{\max, INL}$$
- For INL to be less than  $\frac{1}{2}$  LSB, maximum  $\Delta C$  is  

$$|\Delta C|_{\max, INL} = C/2^N$$
- DNL is defined as,  

$$|DNL|_{\max} = (2^N - 1) |\Delta C|_{\max, DNL}.$$
- For DNL to be less than  $\frac{1}{2}$  LSB, maximum  $\Delta C$  is  

$$|\Delta C|_{\max, DNL} = C/(2^{N+1}-2).$$
- MSB capacitor accuracy is more critical in determining the DNL!!

From ref[1]



# Charge Redistribution SAR Tradeoffs

---

## Advantages:

- Low power dissipation.
- Inherent T/H operation.
- Offset cancellation is incorporated.
- Requirement of less analog circuitry.

## Disadvantages:

- Need of good capacitive material.
- Large capacitors, making matching difficult.
- Not inherently monotonic.

## Other Charge Redistribution topologies

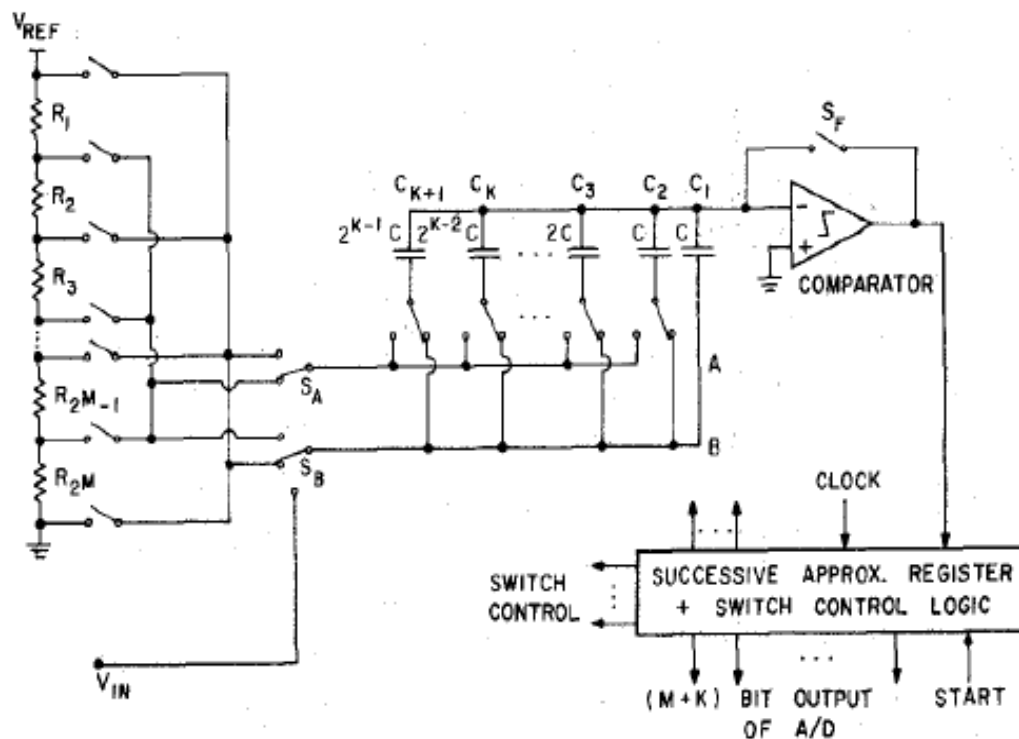


Figure from ref [5]

SAR hybrid ADC Architecture

- Resistor DAC for MSBs and Capacitors for LSBs.
- Operation starts by closing  $S_F$  and charging top plate to  $V_{IN} - V_{OS}$ . Next  $S_F$  is opened and a search is performed in the resistive divider. Finally bottom plates of capacitors are switched from  $S_A$  and  $S_B$  to converge to  $V_{OS}$ .
- ADC is inherently monotonic and there will be no missing codes.



# SAR ADC Configurations

---

- A commonly used Figure of merit (FOM) for ADC's in terms of resolution, bandwidth and power dissipation is given by,

$$\text{FOM} = \frac{10^{(\text{SNR}[\text{dB}] - 1.78[\text{dB}])} \times \left( \frac{\text{Sampling rate}}{2} \right)}{\text{power dissipation}}$$

From ref [6]

- Lower power dissipation gives higher FOM, hence techniques like Switched opamp, reset opamp circuits and boot-strapping techniques have been explored using Successive Approximation ADC's operating at lower VDDs.



## SAR vs other ADCs

---

- A pipelined ADC introduces latency, consumes more power and takes up more area for same resolution. Also requires calibration for more than 12 bits resolution like SAR.
- Flash ADC is much faster, less accurate and takes more silicon area due to the number of comparators  $2^N$  for N bit resolution.
- Oversampled/ $\Sigma$ - $\Delta$  ADCs have low conversion rates, high precision, averaging noise and no requirement for trimming or calibration even up to 16 bits of resolution.
- Power dissipation of SAR ADCs vary with the sampling rate unlike Flash and Pipeline architectures. Hence find applications in PDAs.





## SAR Summary

---

- Critical components are DAC and comparator.
- Settling time of DAC must be less than  $\frac{1}{2}$  LSB and determines the speed of conversion.
- Accuracy of the DAC is critical since an incorrect decision could result in ending up the value in wrong leg of binary tree.
- Comparator should resolve small differences between  $V_{IN}$  and  $V_{DAC}$ .
- The clock frequency should be equal to the sampling frequency multiplied by the number of bits.
- SAR ADCs are efficient, easy to understand and ideally suited for modern CMOS processes.



## References

---

- [1] R. J. Baker, *CMOS Circuit Design, Layout, and Simulation, Revised Second Edition*, Wiley-IEEE, 2008
- [2] [http://webcast.berkeley.edu/EE 247](http://webcast.berkeley.edu/EE%20247)
- [3] [http://www.maxim-ic.com/appnotes.cfm/an\\_pk/1080](http://www.maxim-ic.com/appnotes.cfm/an_pk/1080)
- [4] <http://www.analog.com/>
- [5] David A. Hodges, Bahram Fotouhi "High-Resolution A/D conversion in MOS/LSI" *IEEE Journal of Solid-State Circuits*, vol. SC-14, no 6, December 1979
- [6] R. Thewes J. Sauerbrey, D. Schmitt-Landsiedel "A 0.5-V 1-uW Successive Approximation ADC " *IEEE Journal of Solid-State Circuits*, vol. 38,no 7,July 2003



# Questions ??

---



# Pipeline ADC

**Bill Filipiak**  
**ECE 614**



# Overview

- **Basic Operation**
- **Advantages/Disadvantages**
- **Ideal/Non-Ideal Switching Points**
- **INL/DNL**
- **S/H Design**
- **1.5 Bits/Stage**
- **Summary**

# Basic Operation


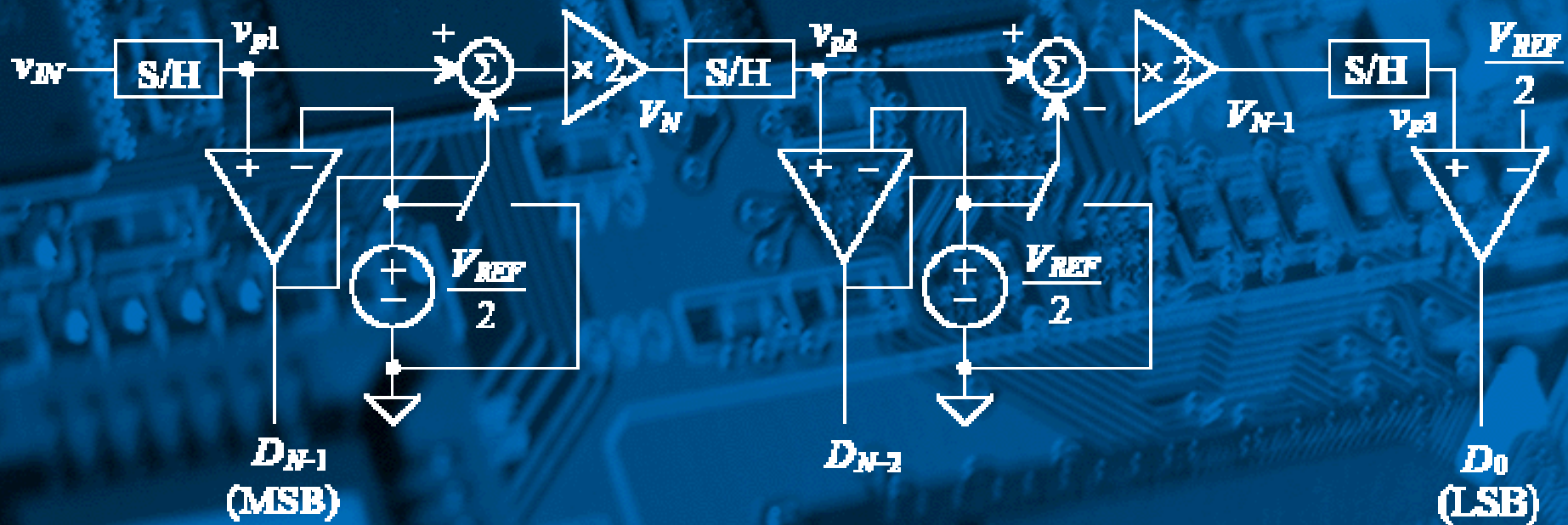


Figure 29.30

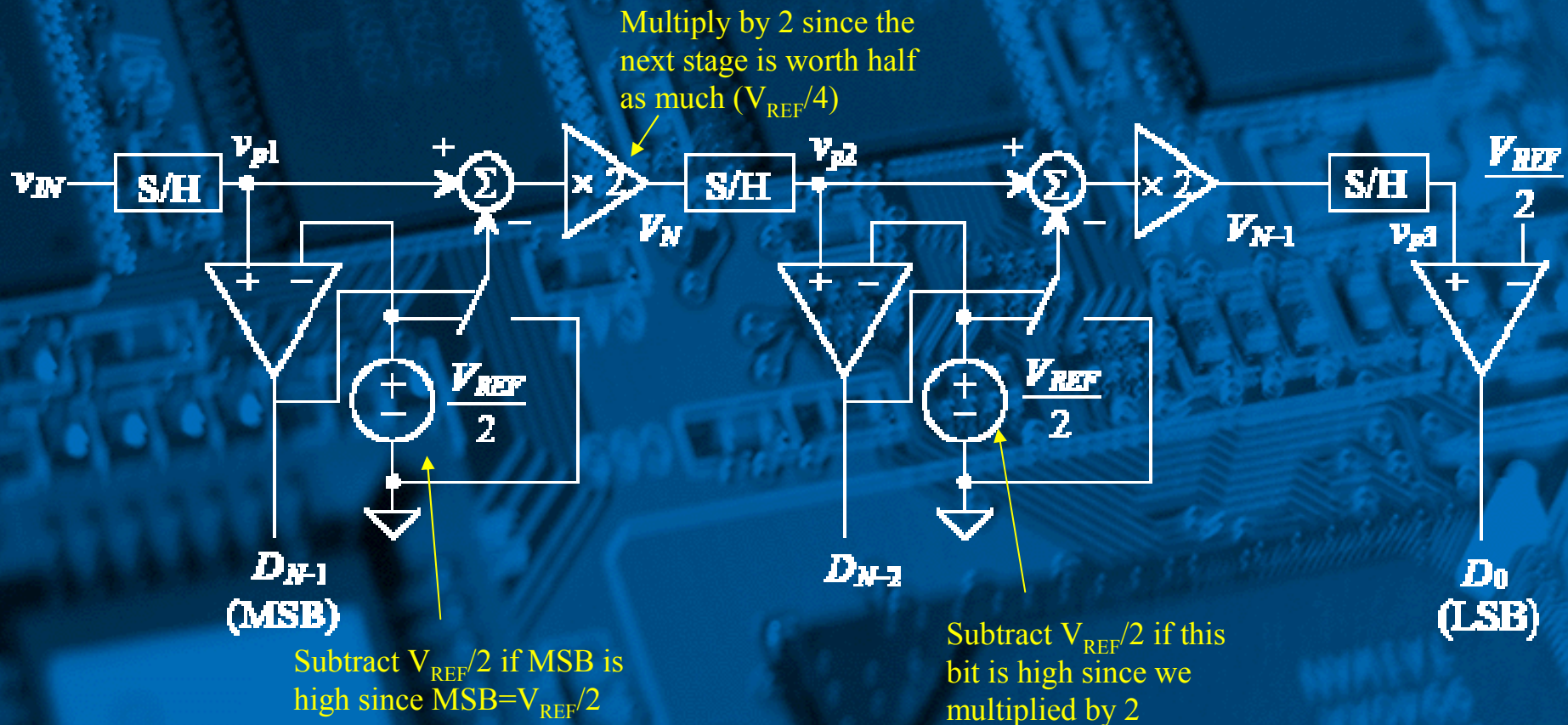


# Basic Operation



Digital Value (2.5V for a 1 and 0 V for a 0) +  $\frac{1}{2}$  of the analog output must always equal the input for each stage

Figure 29.30


# Basic Operation

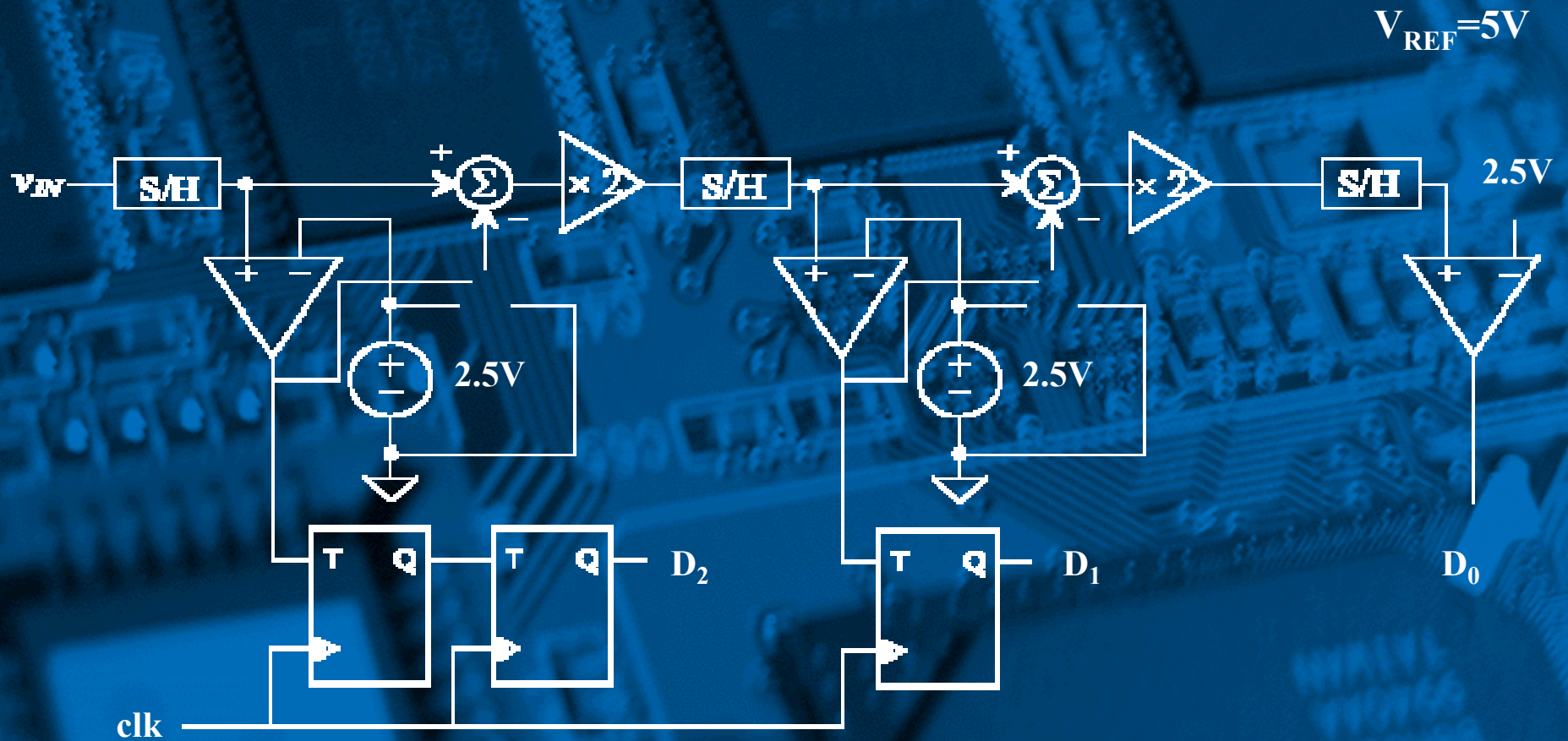


Adapted from Figure 29.30



# Basic Operation

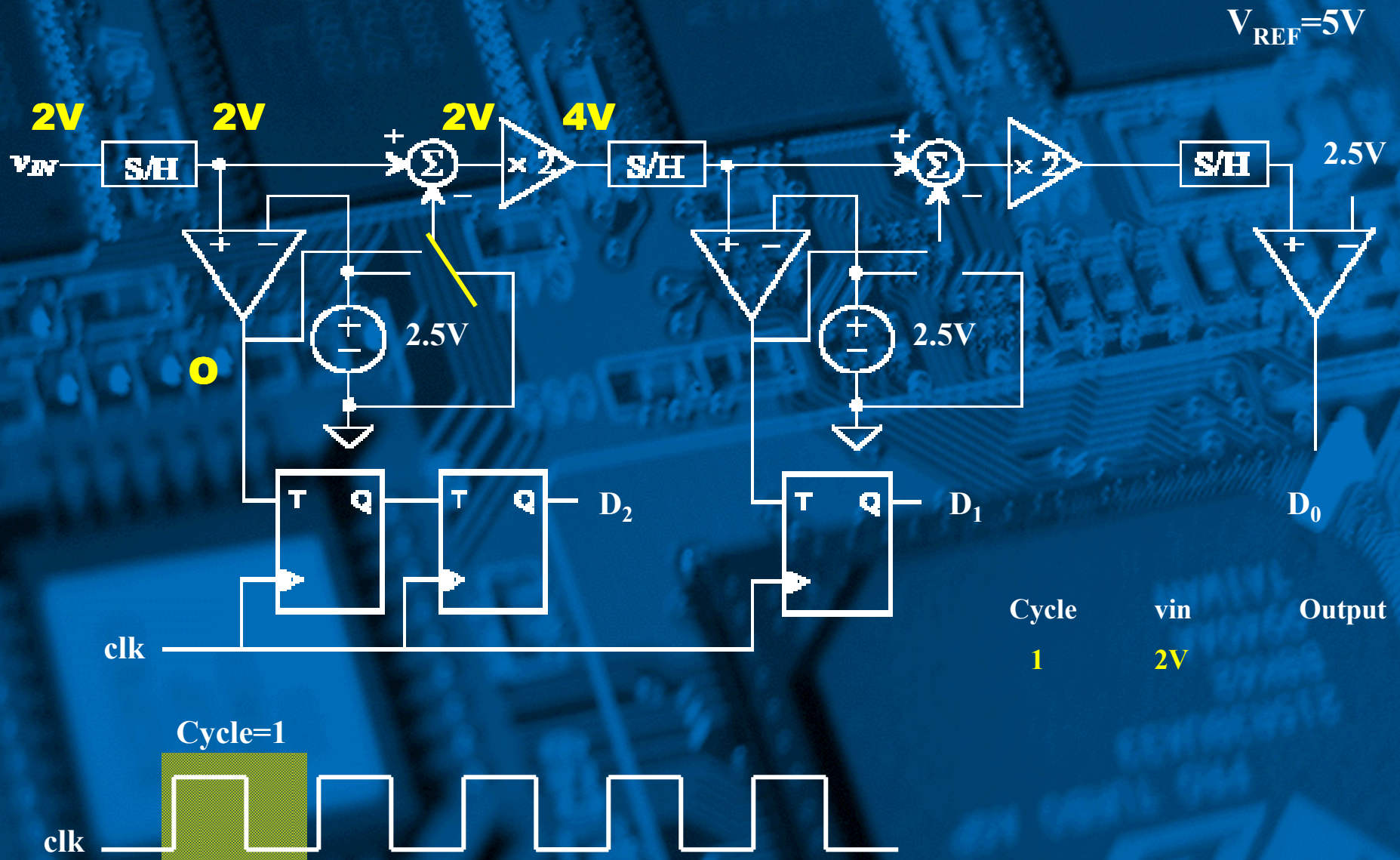


# Basic Operation

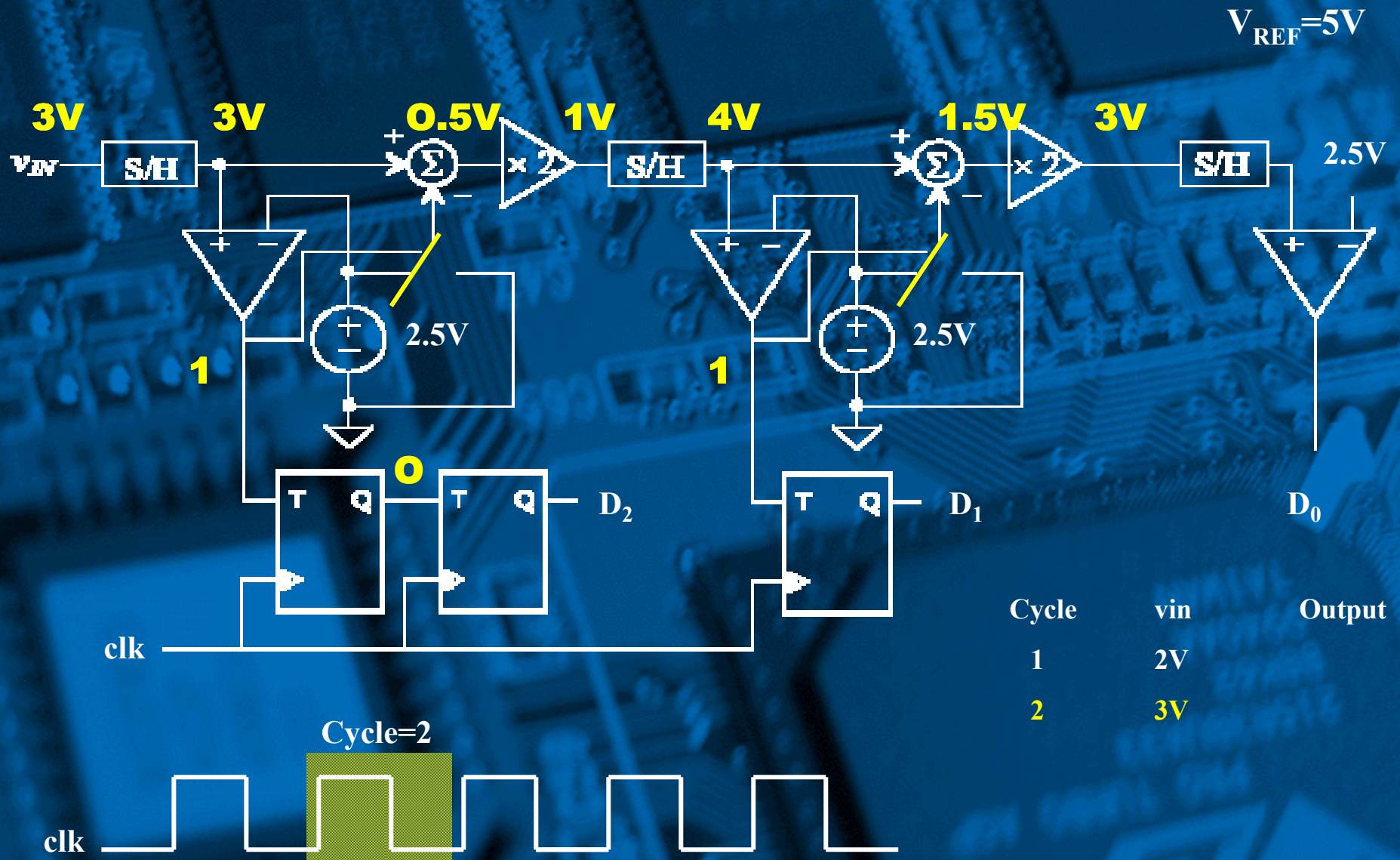




# Basic Operation

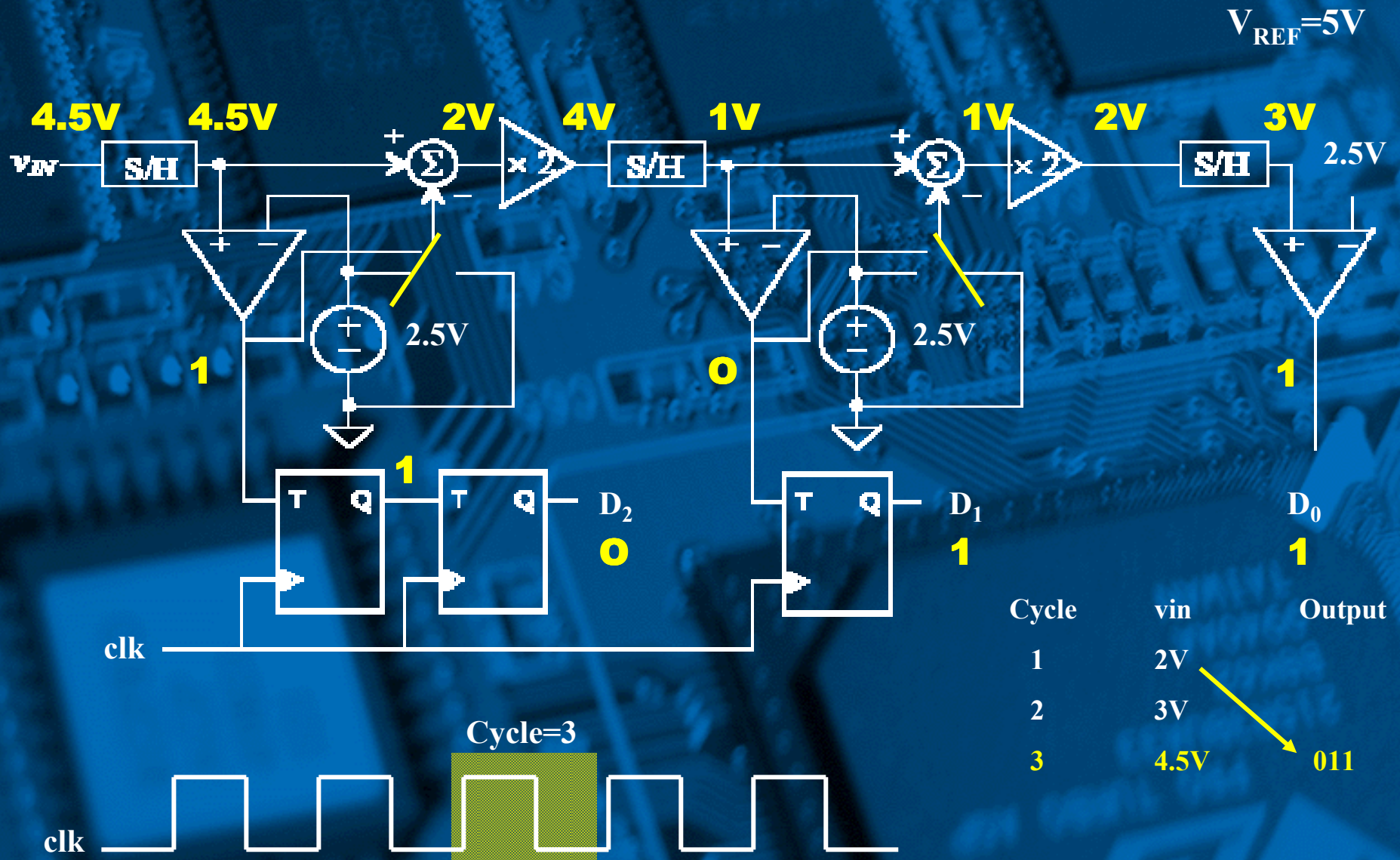


# Basic Operation

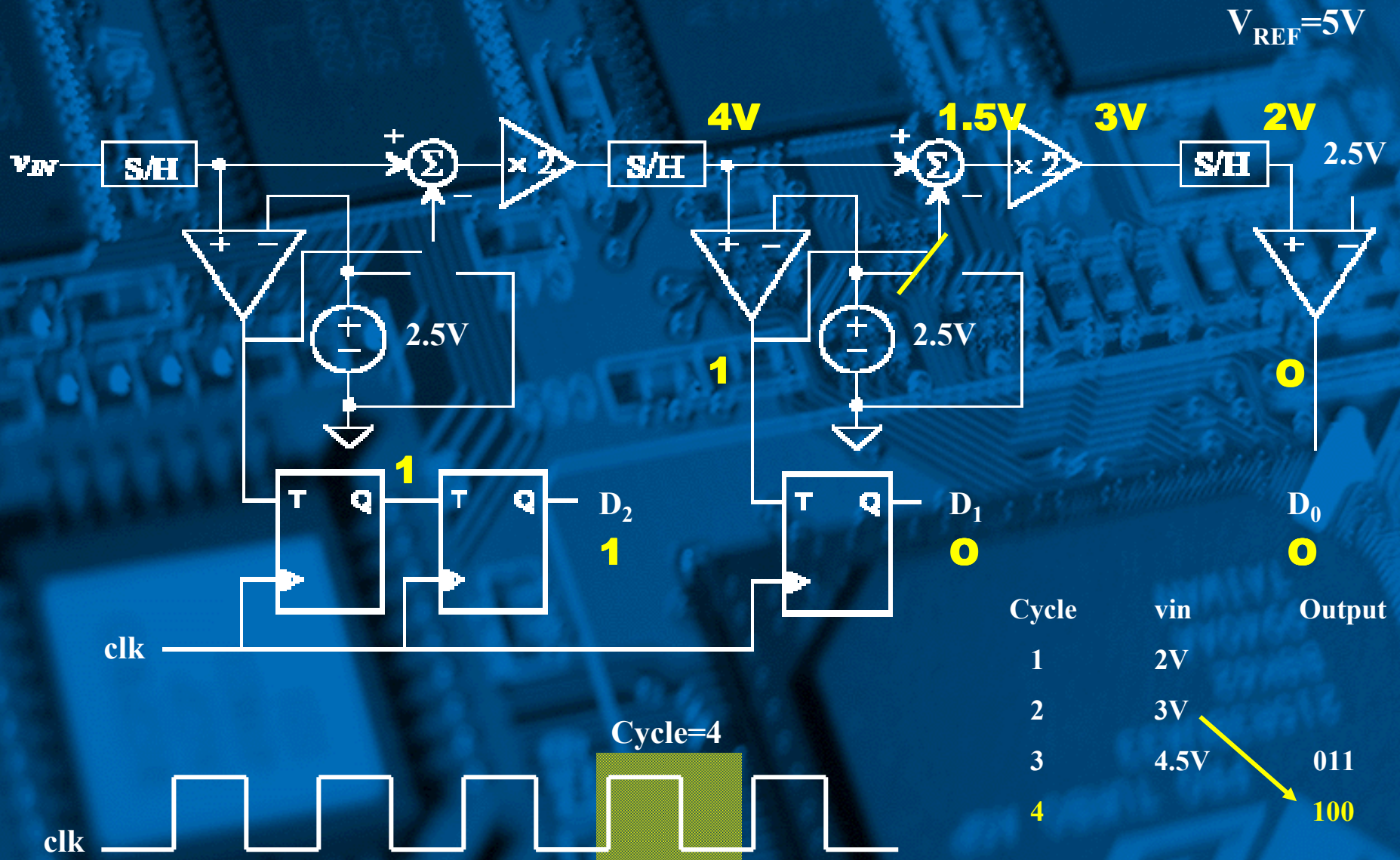



# Basic Operation

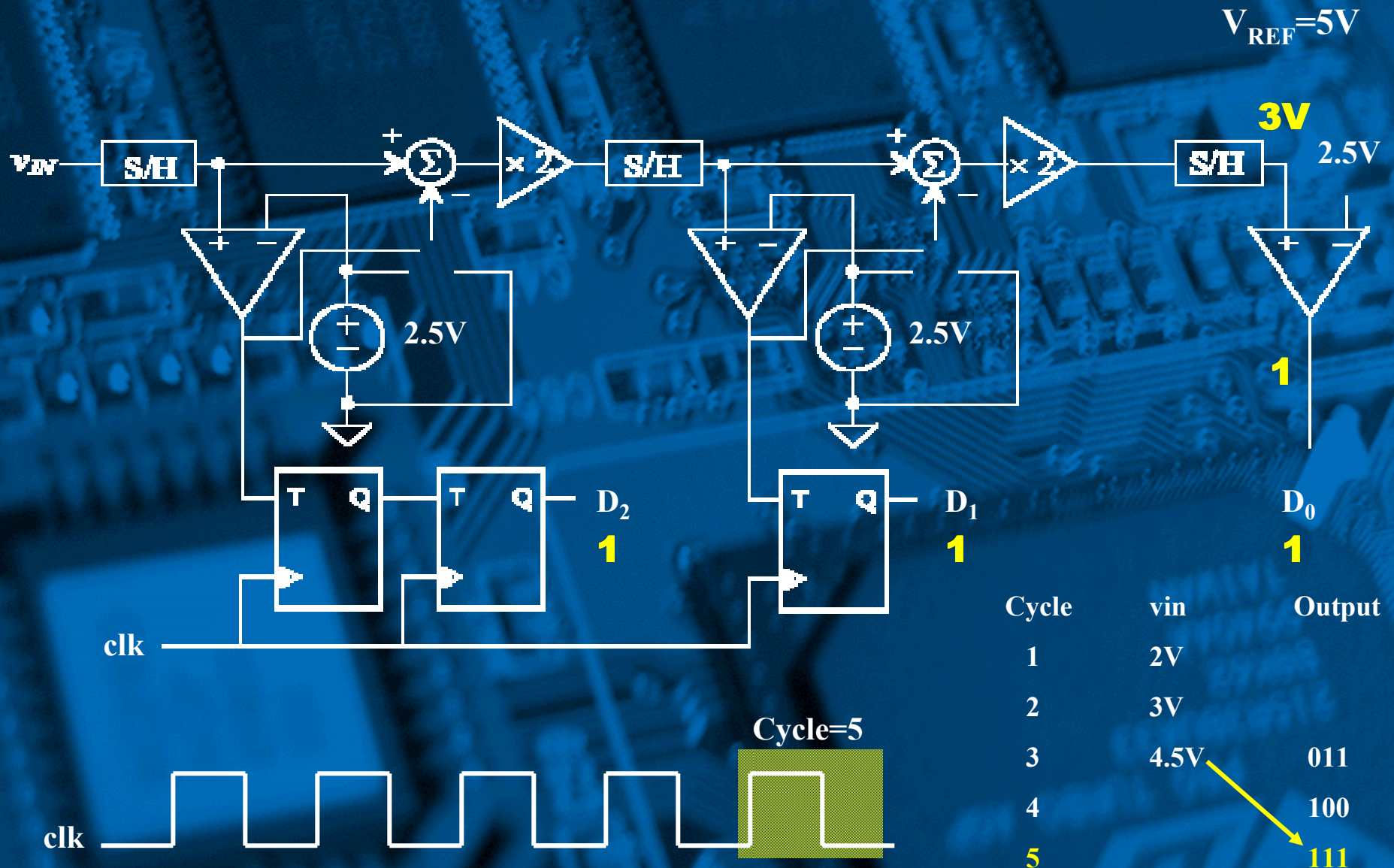

# Advantages


- Low number of comparators (N comparators)
  - Flash ADC requires  $2^N - 1$  comparators
  - Two-step ADC requires  $2(2^{N/2} - 1)$  comparators
- High throughput – One conversion is completed per clock cycle
  - Two-step ADC requires two clock cycles per conversion



# Disadvantages


- Latency of  $N$  clock cycles before the ADC outputs comparison data
- Errors propagate through system since each stage operates on the residue passed from previous stage
  - Accuracy of most significant stages becomes more important than downstream stages

## Switches when

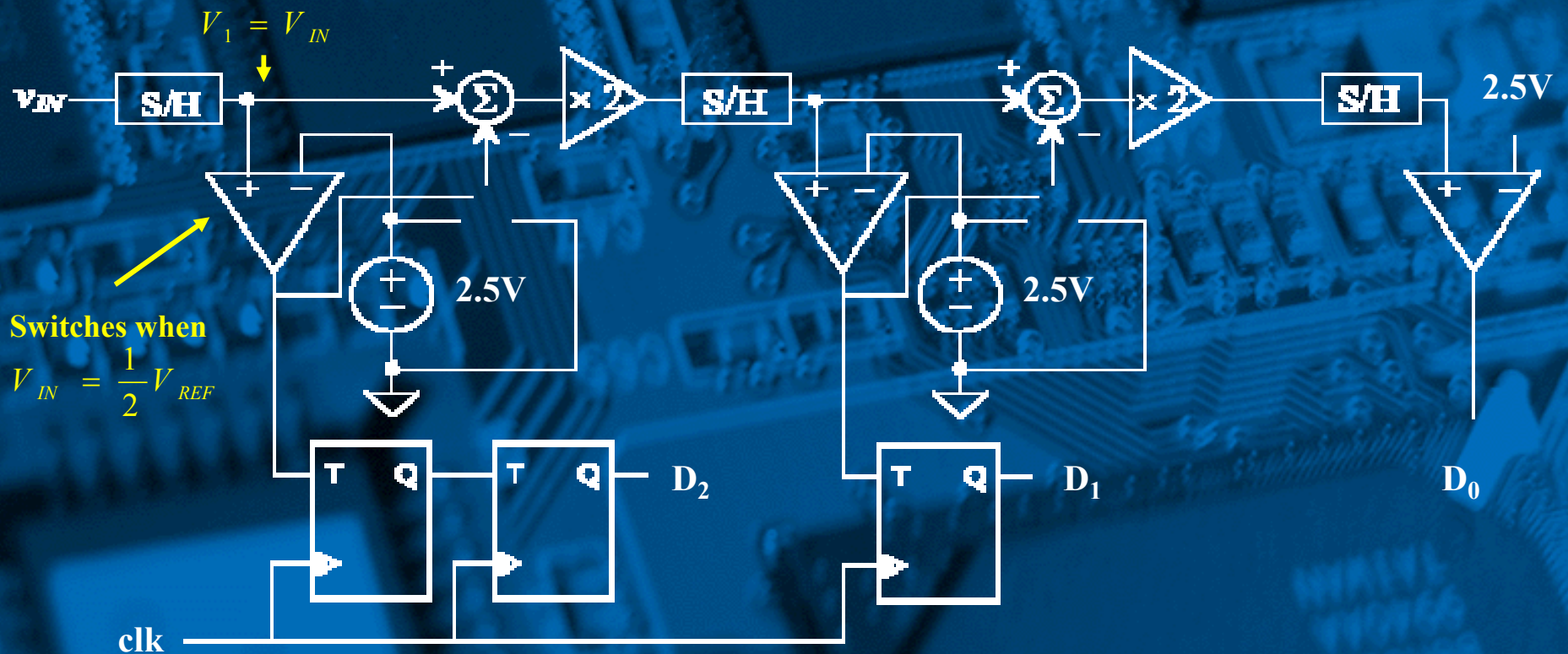
$$V_{IN} = \frac{1}{2} V_{REF}$$




# Ideal Switching Point

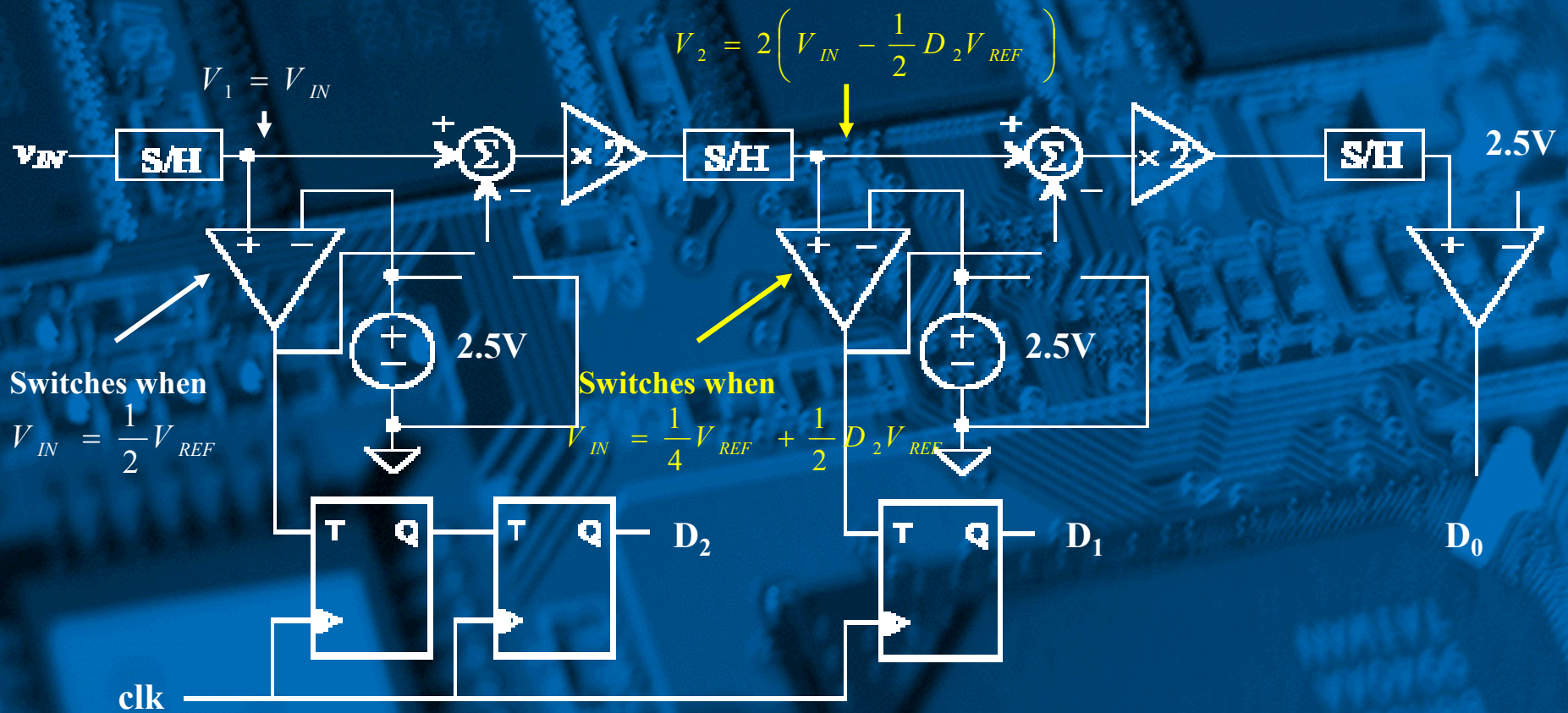

# Ideal Switching Point

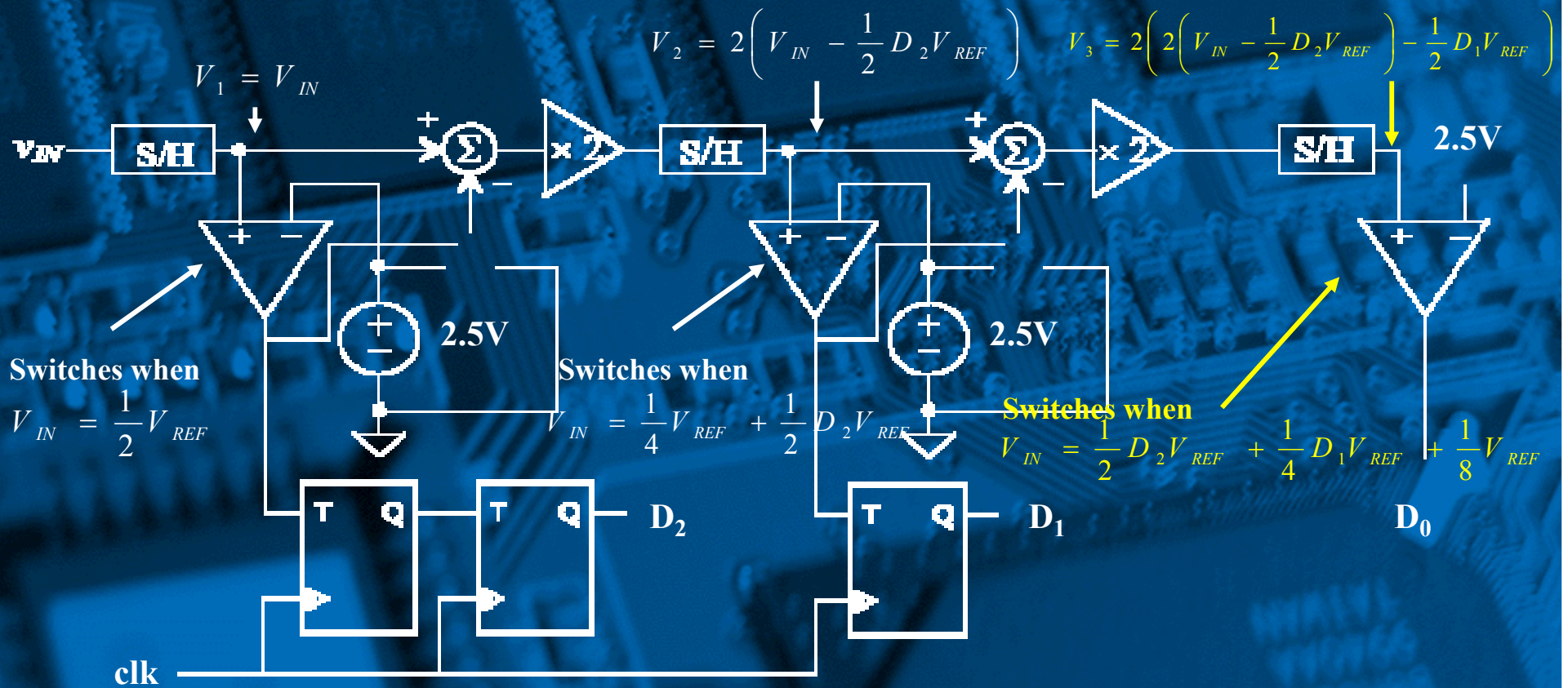



# Ideal Switching Point

- **1<sup>st</sup> comparator switches when:**

$$V_{IN} = \frac{1}{2} V_{REF}$$

- **2<sup>nd</sup> comparator switches when:**

$$V_{IN} = \frac{1}{4} V_{REF} + \frac{1}{2} D_2 V_{REF}$$

- **3<sup>rd</sup> comparator switches when:**

$$V_{IN} = \frac{1}{2} D_2 V_{REF} + \frac{1}{4} D_1 V_{REF} + \frac{1}{8} V_{REF}$$

- **N<sup>th</sup> comparator switches when:**

$$V_{IN} = \frac{1}{2} D_{N-1} V_{REF} + \frac{1}{4} D_{N-2} V_{REF} + \frac{1}{8} D_{N-3} V_{REF} + \dots + \frac{1}{2^{N-1}} D_1 V_{REF} + \frac{1}{2^N} V_{REF}$$



# Quantization

**Digital  
Output**

**Input Range**

**Input Voltage  
( $V_{REF}=5V$ )**

**000**

$$0 \rightarrow \frac{1}{8} V_{REF}$$

**0→0.625V**

**001**

$$\frac{1}{8} V_{REF} \rightarrow \frac{1}{4} V_{REF}$$

**0.625V→1.25V**

**010**

$$\frac{1}{4} V_{REF} \rightarrow \frac{1}{4} V_{REF} + \frac{1}{8} V_{REF}$$

**1.25→1.875V**

**011**

$$\frac{1}{4} V_{REF} + \frac{1}{8} V_{REF} \rightarrow \frac{1}{2} V_{REF}$$

**1.875→2.5V**

**100**

$$\frac{1}{2} V_{REF} \rightarrow \frac{1}{2} V_{REF} + \frac{1}{8} V_{REF}$$

**2.5→3.125V**

**101**

$$\frac{1}{2} V_{REF} + \frac{1}{8} V_{REF} \rightarrow \frac{1}{2} V_{REF} + \frac{1}{4} V_{REF}$$

**3.125→3.75V**

**110**

$$\frac{1}{2} V_{REF} + \frac{1}{4} V_{REF} \rightarrow \frac{1}{2} V_{REF} + \frac{1}{4} V_{REF} + \frac{1}{8} V_{REF}$$


**3.75→4.375V**

**111**

$$\frac{1}{2} V_{REF} + \frac{1}{4} V_{REF} + \frac{1}{8} V_{REF} \rightarrow V_{REF}$$

**4.375→5V**


# Quantization

 


Adapted from Figure 28.19



# Non-Ideal Switching Point

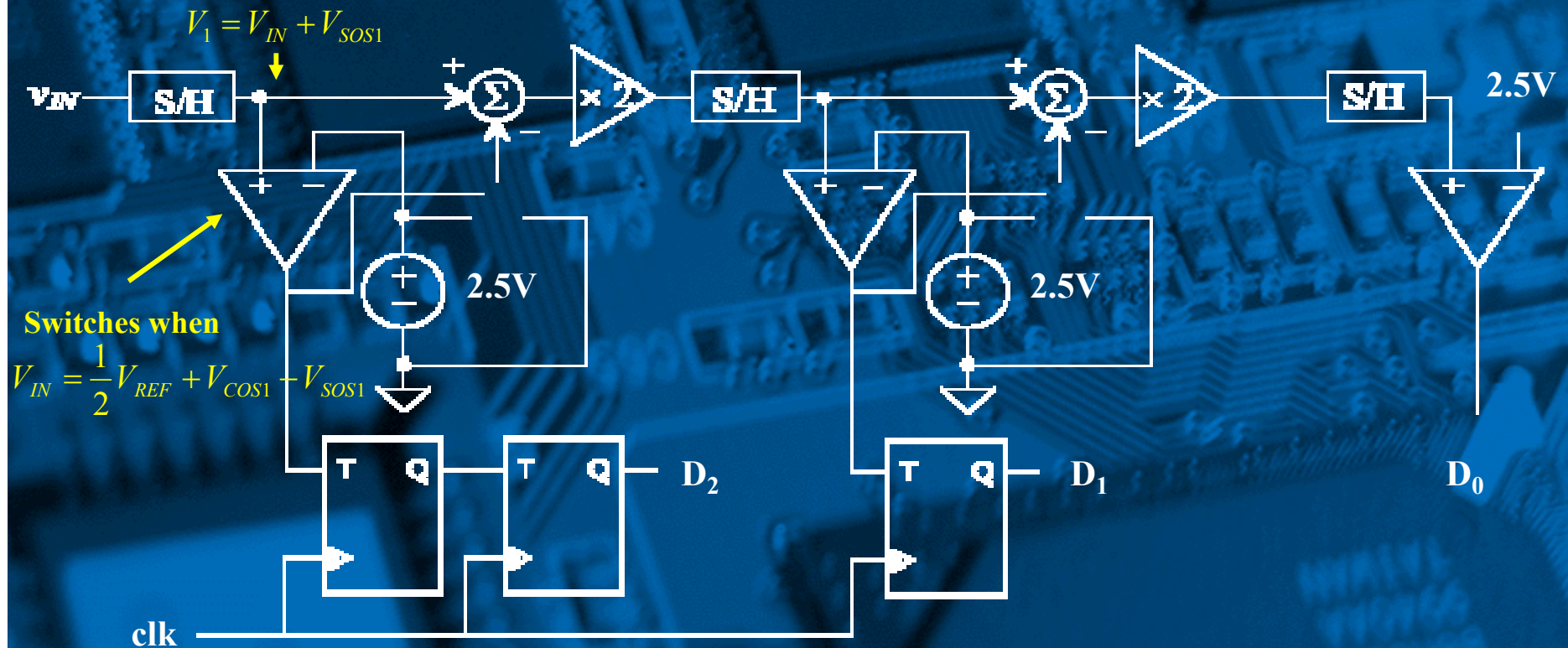


# Non-Ideal Switching Point

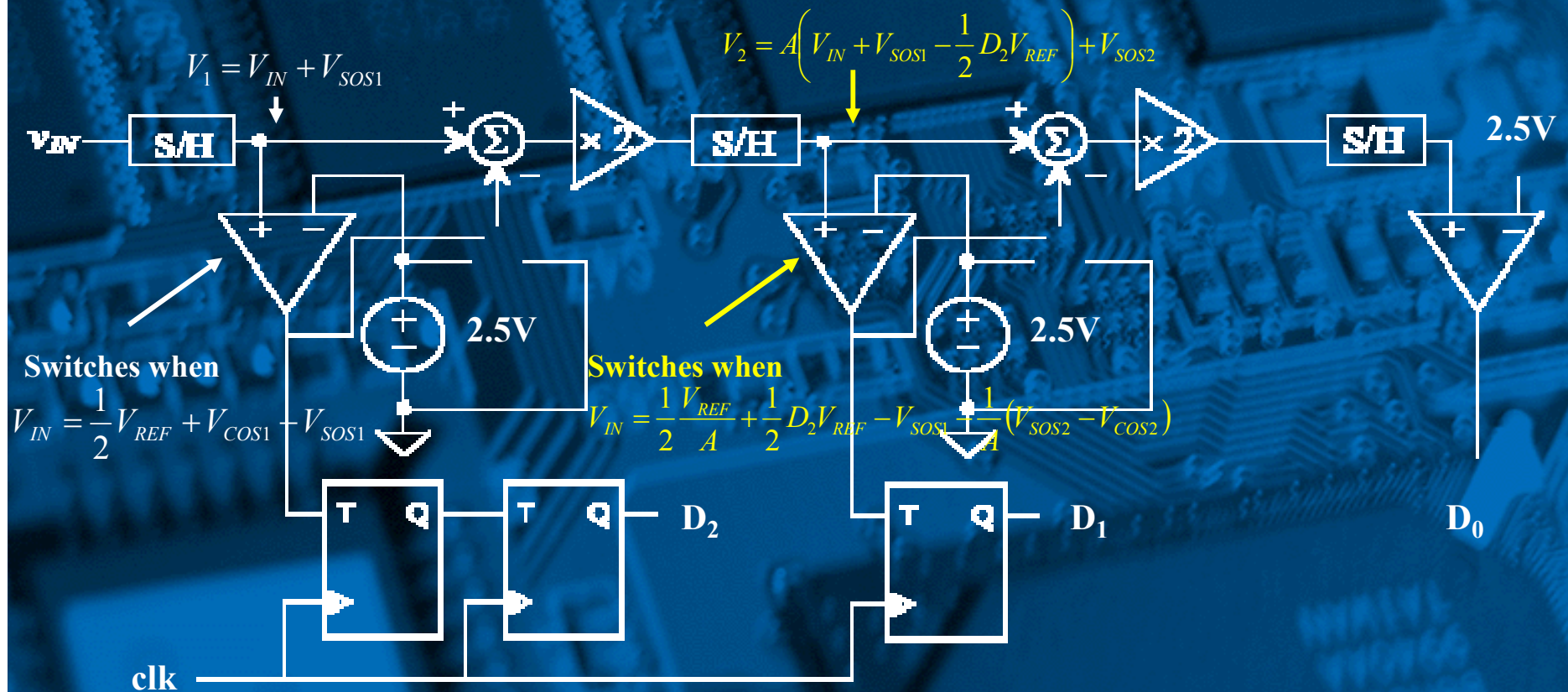



# Non-Ideal Switching Point

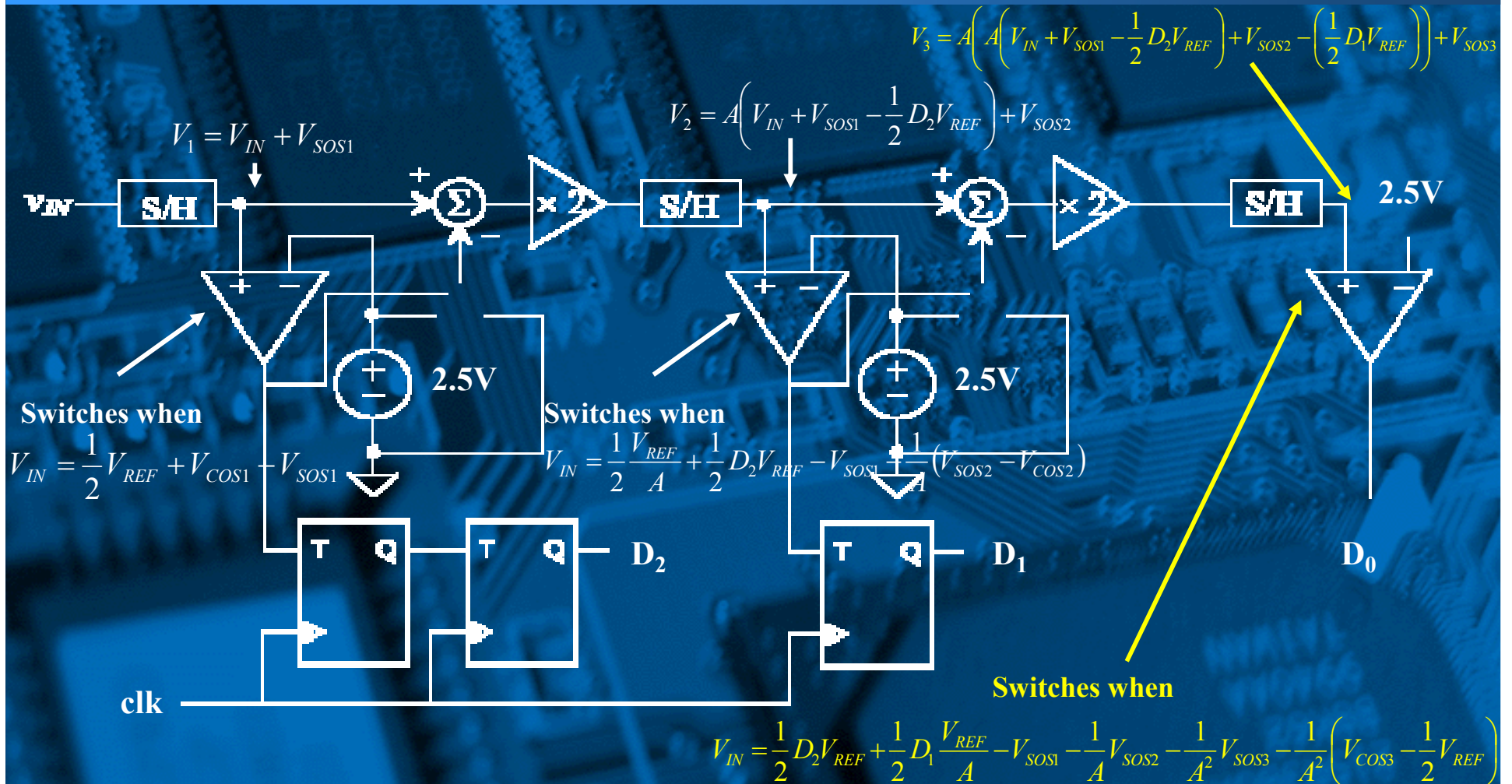



# Non-Ideal Switching Point

- **1<sup>st</sup> comparator switches when:**

$$V_{IN} = \frac{1}{2}V_{REF} + V_{COS1} - V_{SOS1}$$

- **2<sup>nd</sup> comparator switches when:**

$$V_{IN} = \frac{1}{2}\frac{V_{REF}}{A} + \frac{1}{2}D_2V_{REF} - V_{SOS1} - \frac{1}{A}(V_{SOS2} - V_{COS2})$$


- **3<sup>rd</sup> comparator switches when:**

$$V_{IN} = \frac{1}{2}D_2V_{REF} + \frac{1}{2}D_1\frac{V_{REF}}{A} - V_{SOS1} - \frac{1}{A}V_{SOS2} - \frac{1}{A^2}V_{SOS3} - \frac{1}{A^2}\left(V_{COS3} - \frac{1}{2}V_{REF}\right)$$

- **Error from first sample-and-hold propagates through and causes a larger error at the last stage of the converter**
- **This analysis only includes major sources of error (sample-and-hold and comparator)**
- **It also assumes that the gain of each amplifier is A, although in reality, each amplifier may have a different gain error**



# INL

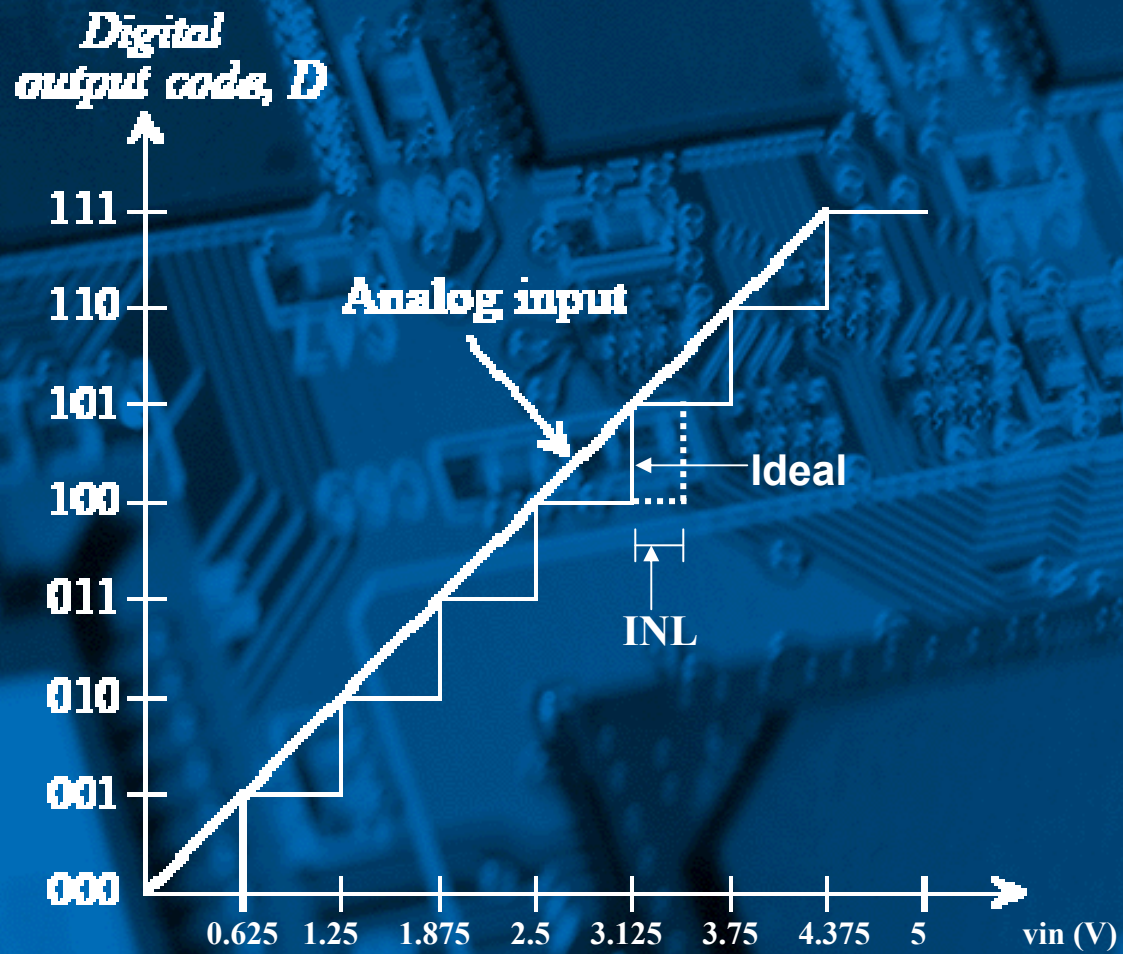

Adapted from Figure 28.23

# INL

- INL is calculated by subtracting the ideal switching point from the non-ideal switching point

- For the first stage:

**Ideal:**  $V_{IN} = \frac{1}{2} V_{REF}$

**Non-Ideal:**  $V_{IN} = \frac{1}{2} V_{REF} + V_{COS1} - V_{SOS1}$

**INL:**  $INL_1 = V_{COS1} - V_{SOS1}$

- For the second stage:

**INL:**  $INL_2 = \frac{V_{REF}}{2} \left( \frac{1}{A} - \frac{1}{2} \right) - V_{SOS1} - \frac{1}{A} (V_{SOS2} - V_{COS2})$

- For the third stage:


**INL:**  $INL_3 = \frac{V_{REF}}{2} \left( \frac{1}{A} - \frac{1}{2} \right) - V_{SOS1} - \frac{1}{A} V_{SOS2} - \frac{1}{A^2} V_{SOS3} - \frac{1}{A^2} V_{COS3} + \frac{V_{REF}}{2} \left( \frac{1}{A^2} - \frac{1}{4} \right)$



# INL

- Worst case addition of offsets must be  $< 1/2$  LSB to be N-bit accurate
- Offsets of later stages are divided by a large gain so they are less important than the first stage
- Less accurate designs can be used for later stages to save power and area

# DNL

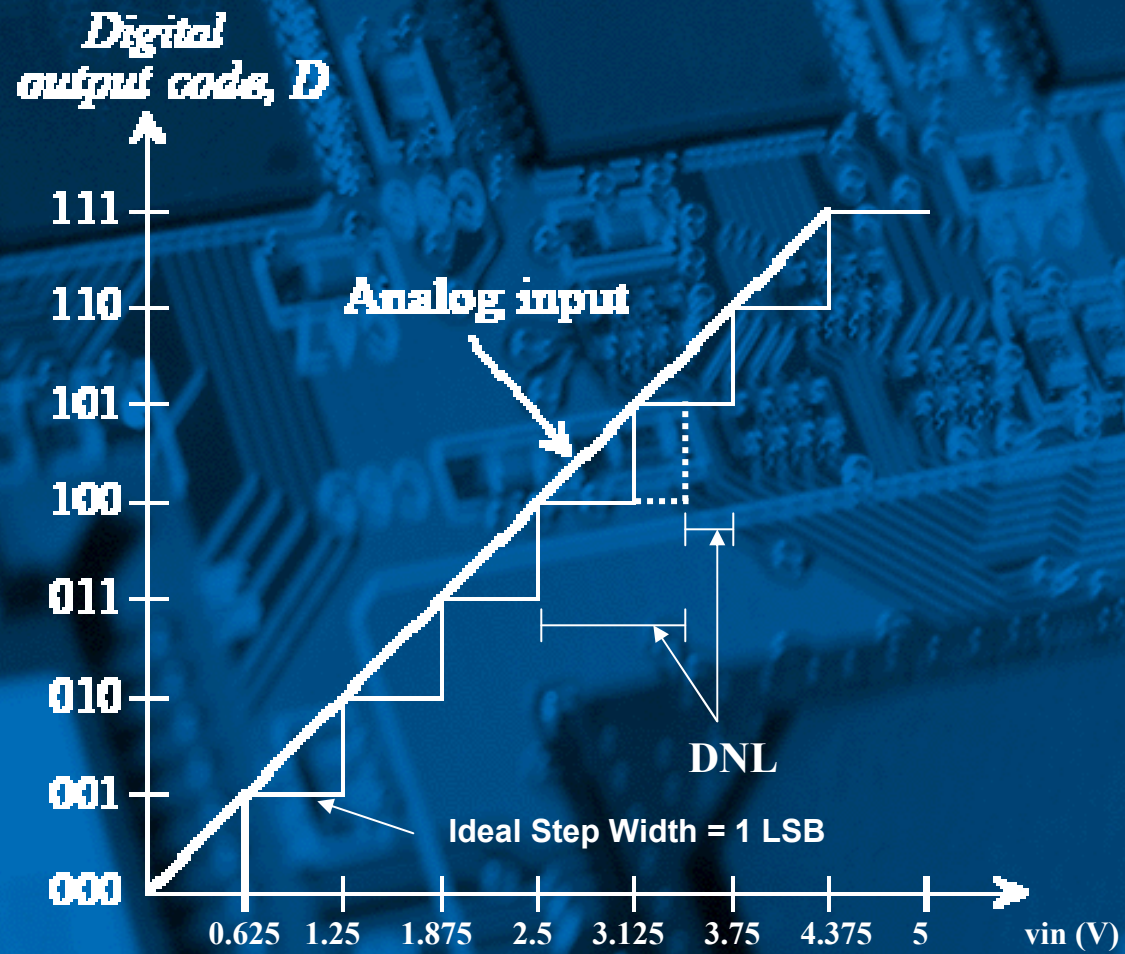


Adapted from Figure 28.23



# DNL


- **DNL is calculated by subtracting the ideal step width (1 LSB) from the actual step width**
- $LSB = \frac{V_{REF}}{2^N} = \frac{V_{REF}}{8}$
- **Worst case DNL tends to occur at the midpoint (switching from 011 to 100)**
- $DNL_{MAX} = V_{IN,SW1} - V_{IN,SW3} - \frac{V_{REF}}{8}$  **which is the point where the MSB switches minus the point where the LSB switches (to get 011) minus 1 LSB**
- **Knowing that the worst case output is 011 for  $V_{IN,SW3}$ :**
$$DNL_{MAX} = \frac{1}{2}V_{REF} + V_{COS1} - \frac{1}{2}\frac{V_{REF}}{A} + \frac{1}{A}V_{SOS2} + \frac{1}{A^2}V_{SOS3} + \frac{1}{A^2}\left(V_{COS3} - \frac{1}{2}V_{REF}\right) - \frac{V_{REF}}{8}$$
- **Notice that the comparator of the first stage and the sample-and-hold of the second stage have the largest impact on the worst case DNL**
- **$DNL_{MAX}$  must be less than  $\frac{1}{2}$  LSB to have N-bit resolution**

# Simulation

 

No Offset


# Simulation

 

200mV offset on first S/H




# Simulation

 


200mV offset on last S/H

# Simulation

 

# S/H Design

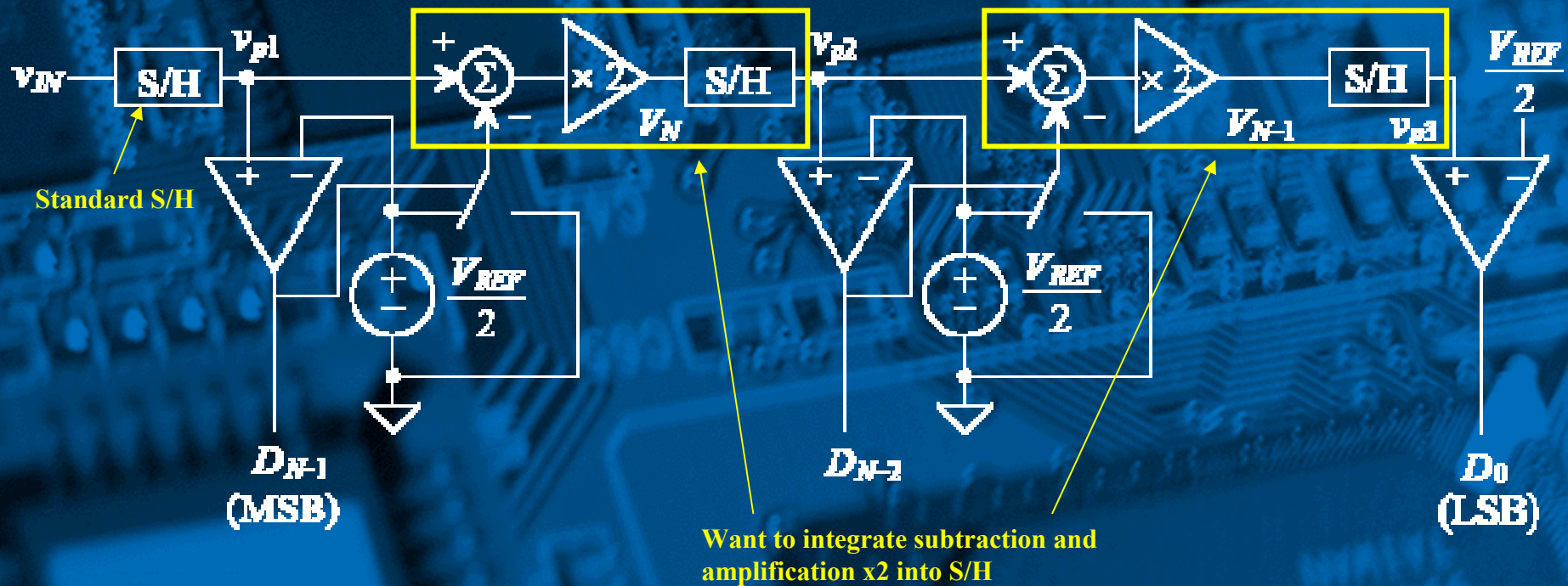


Note that input to S/H is not fully differential so we will use a single ended design

Figure 29.30





# S/H Design

 

Adapted from Figure 34.30
  
# S/H Design

- $Q_{I,F}^{\phi^1} = C_{I,F}(V_{IN} - V_{CM} \pm V_{OS})$
- $Q_I^{\phi^3} = C_I(V_{CI} - V_{CM} \pm V_{OS})$
- $Q_F^{\phi^3} = C_F(V_{OUT} - V_{CM} \pm V_{OS})$
- $Q_I^{\phi^1} + Q_F^{\phi^1} = Q_I^{\phi^3} + Q_F^{\phi^3}$
- $V_{OUT} = \left(1 + \frac{C_I}{C_F}\right)V_{IN} - \frac{C_I}{C_F}V_{CI}$
- $V_{OUT} = \left(1 + \frac{C_I}{C_F}\right) \left( V_{in} - \frac{V_{CI}}{\frac{C_F}{C_I} + 1} \right)$





# S/H Design


- We want to multiply  $V_{IN}$  by 2, so  $C_I = C_F$
- The final output is:

$$V_{OUT} = 2 \left( V_{IN} - \frac{V_{CI}}{2} \right)$$

- We want to subtract  $V_{REF}/2$  from the input, but this implementation will divide  $V_{CI}$  by 2
- This means we need to supply  $V_{REF}$  on  $V_{CI}$  instead of  $V_{REF}/2$  for this implementation to work
- $V_{CI}$  will be either  $V_{REF}$  or GND, depending on the state of the switch
- Notice the op-amp offset is auto-zeroed out, but there is still offset from the switches



# S/H Design

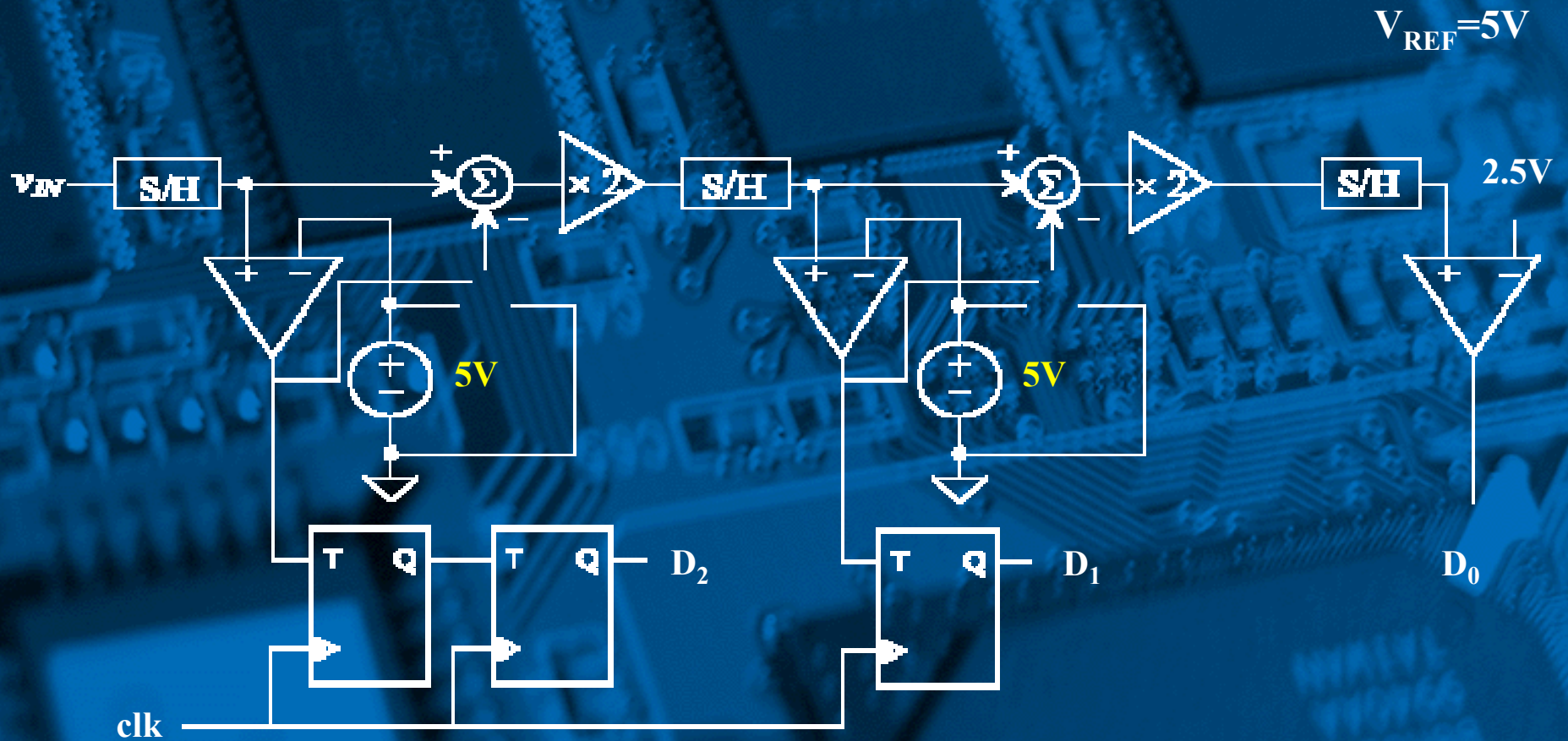

# Simulation






# 1.5 Bits/Stage

- Traditional design uses a single comparator, which results in a single bit per stage and two levels (0 or a 1)
- Two bits per stage would result in four levels (00, 01, 10, 11)
- 1.5 bits per stage means that we use three levels which is based on a thermometer code (00, 01, 11)
- 1.5 bits per stage requires two comparators per stage instead of one as used in the basic design



# 1.5 Bits/Stage

 

$$V_{OUT} = 2(V_{IN} - \bar{a}\bar{b}0 - \bar{a}bV_{CM} - ab2V_{CM}) + V_{CM}$$

$$V_{OUT} = 2\left(V_{IN} + \bar{a}\bar{b}\frac{V_{CM}}{2} - \bar{a}b\frac{V_{CM}}{2} - ab\frac{3V_{CM}}{2}\right)$$

↑  
Difficult to add and subtract using  
single sided design

This does not account for the fact that  
the S/H will divide  $V_{CM}$  by 2, so these  
would need to be compensated

Adapted from Figure 34.51

# 1.5 Bits/Stage


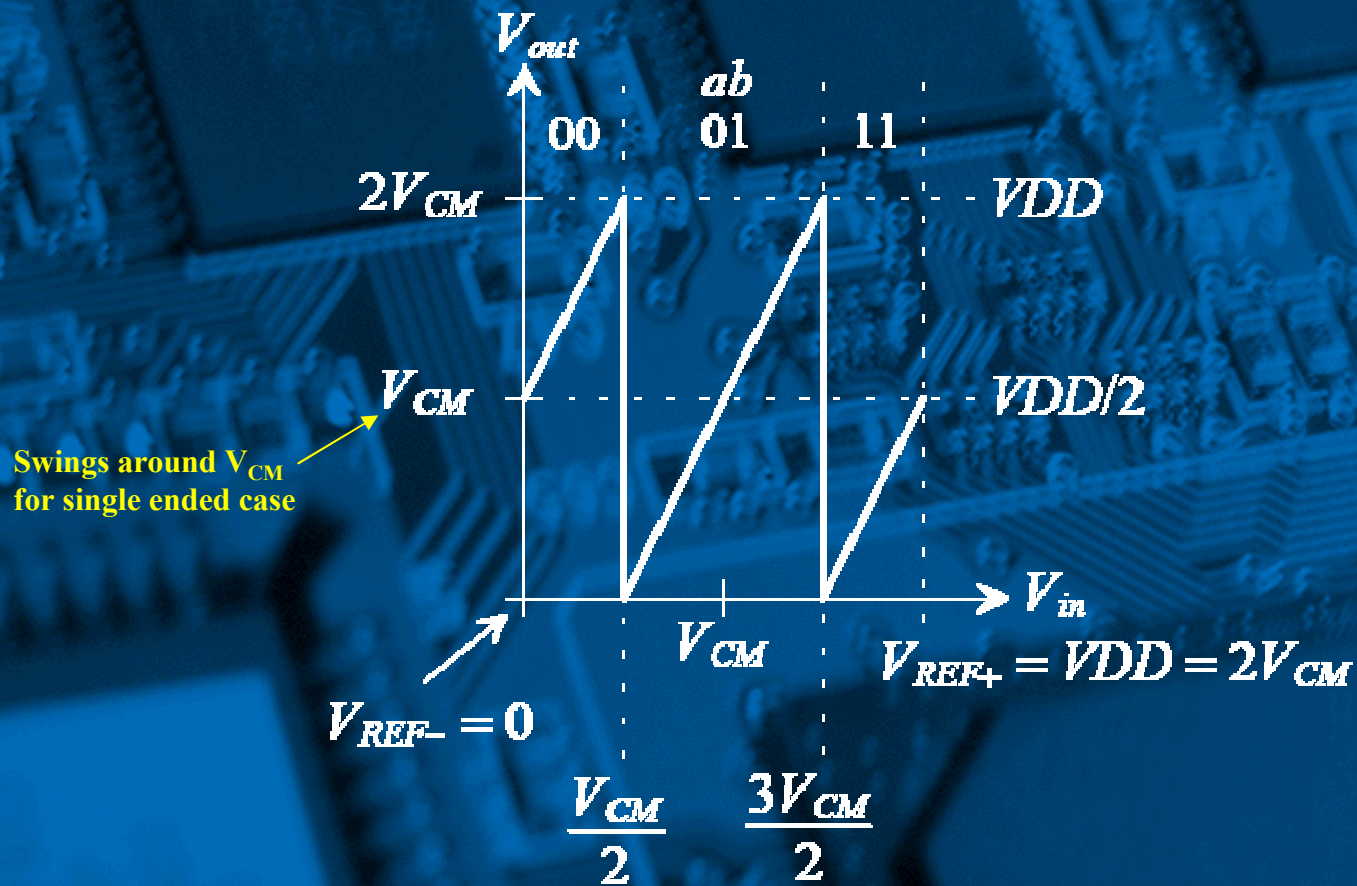


Figure 34.50

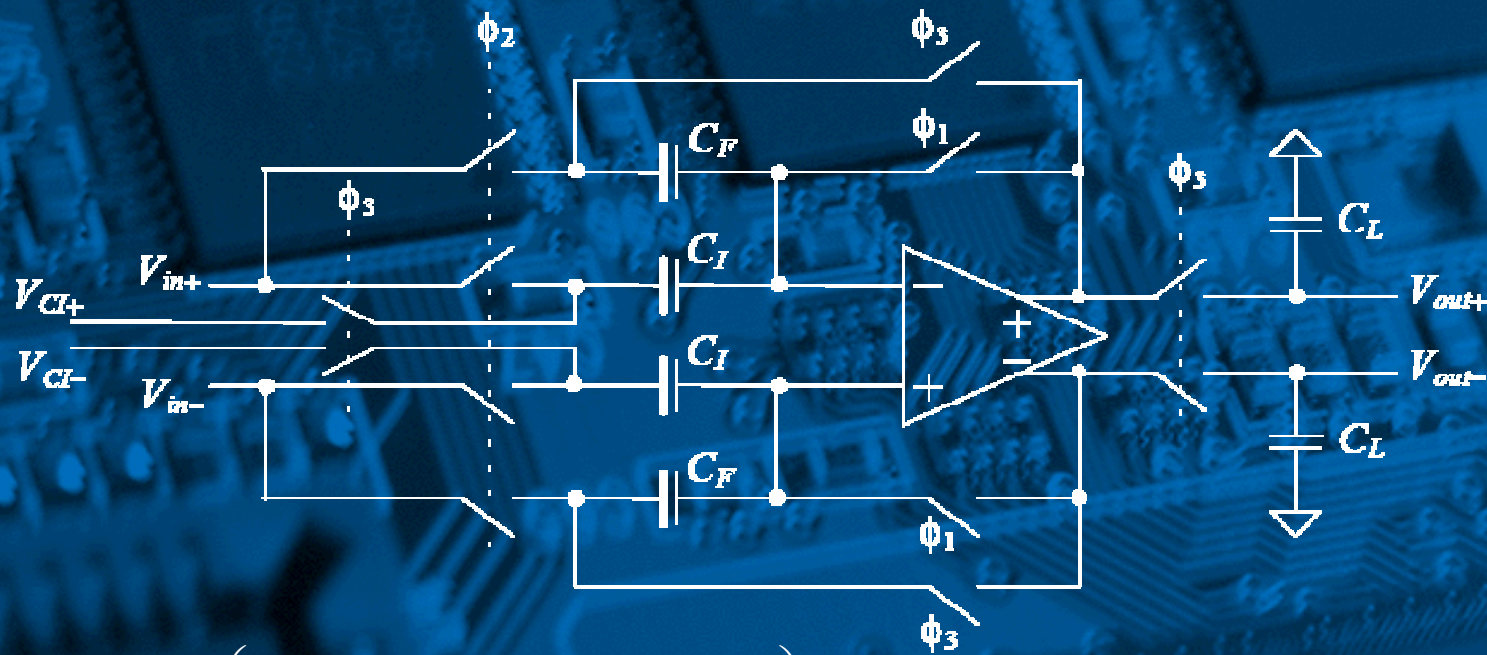

# 1.5 Bits/Stage




$$V_{OUT} = \left(1 + \frac{C_I}{C_F}\right) \left( (V_{in+} - V_{in-}) - \frac{(V_{CI+} - V_{CI-})}{\frac{C_F}{C_I} + 1} \right)$$

$$V_{OUT} = 2 \left( (V_{IN+} - V_{IN-}) - \frac{(V_{CI+} - V_{CI-})}{2} \right)$$

Figure 34.42




# 1.5 Bits/Stage

 

al Value +  $\frac{1}{2}$  of the analog output must always equal the input for each stage, just like the standard implementation


# 1.5 Bits/Stage

 

$$V_{OUT} = 2 \left( V_{IN} + \bar{a}\bar{b} \frac{V_{CM}}{2} - a\bar{b} \frac{V_{CM}}{2} - ab \frac{3V_{CM}}{2} \right)$$



# 1.5 Bits/Stage

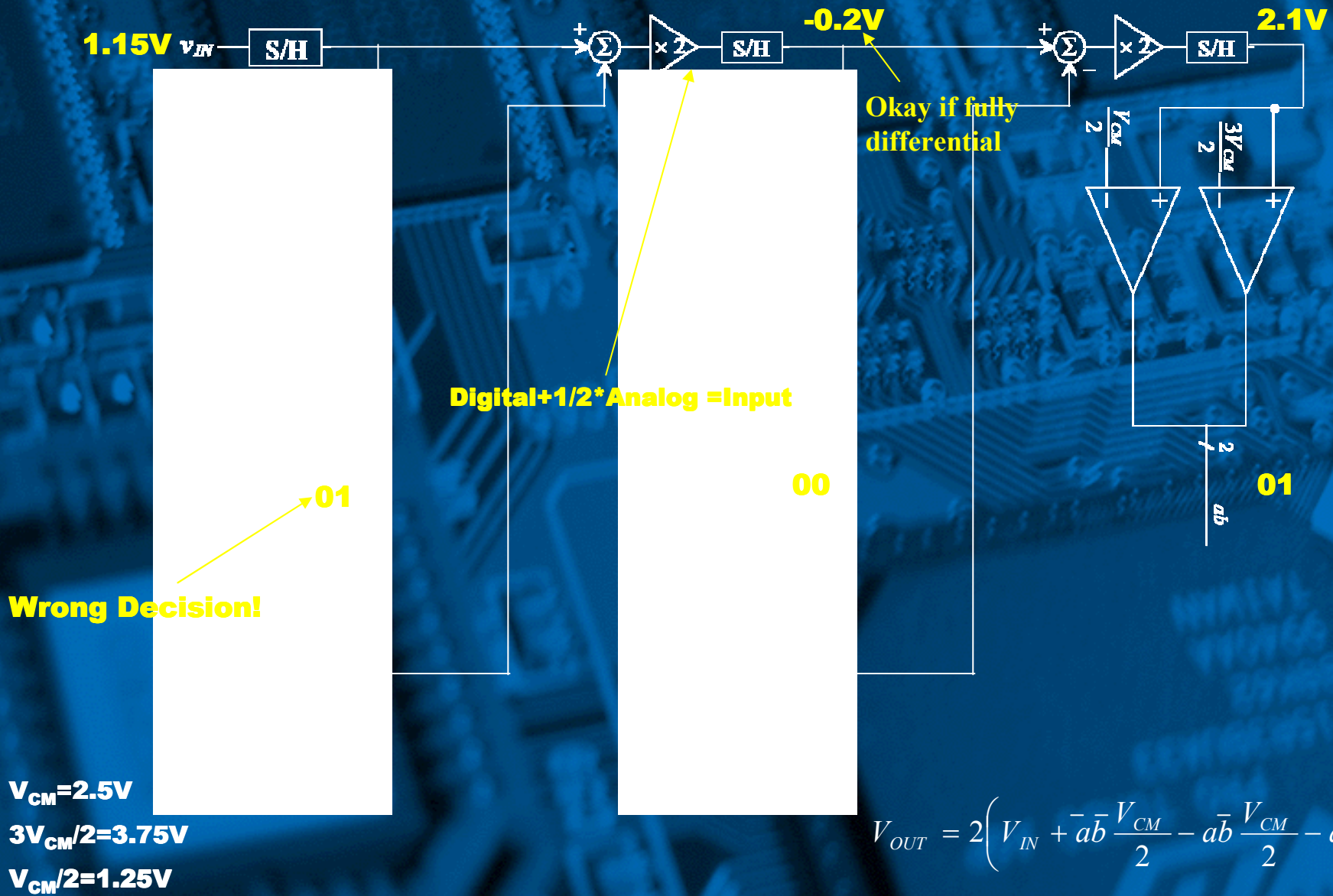



# 1.5 Bits/Stage

- **Advantage:**  
Comparators can be “sloppy” and can make mistakes without ruining the entire conversion
- **Disadvantage:**  
Requires  $2N$  comparators instead of  $N$  comparators  
Requires extra logic overhead to convert 2 bit output to single bit output



# Summary

- **Basic Operation**
  - Pipeline with a S/H, comparator, subtractor, and x2 amplifier
  - Each stage operates on residue of previous stage
- **Advantages/Disadvantages**
  - N comparators, one computation per clock cycle
  - Latency of N clock cycles, errors propagate
- **Ideal/Non-Ideal Switching Points**
- **INL/DNL**
  - Accuracy of early stages more important than later stages
- **S/H Design**
  - Integrate subtractor and x2 amplifier in S/H
- **1.5 Bits/Stage**
  - Increase accuracy at the cost of area



# References

- Baker, R.J., CMOS Circuit Design, Layout, and Simulation, Second Edition, Wiley-IEEE, 2008.
- Baker, R.J., CMOS Mixed-Signal Circuit Design, First Edition, Wiley-IEEE, 2002.





**Questions?**