



UiO : **Institutt for informatikk**

Det matematisk-naturvitenskapelige fakultet

Successive Approximation Register (SAR) Analog to Digital Converter (ADC)

By Espen Klein Nilsen
and Vegard Midtbøen



Content

- Introduction
- Requirements
- Solution
- Conclusion

Introduction

SAR ADC

- Sample-and-Hold
- Comparator
- Digital-to-Analog Converter
- SAR Logic

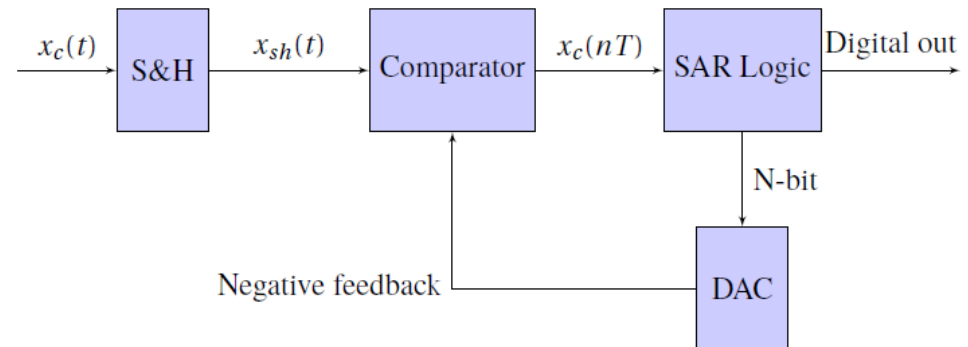


Figure 1.1: Block diagram

Introduction

SAR ADC

 


Figure 1.2: Example of 4-bit SAR ADC conversion

Introduction

Sample-and-Hold

- Snatches a value of a analog signal and holds it constant
- $\Phi 1$:on
→ C charges to V_{in}
- $\Phi 1$:off
→ $V_{out} = V_{in}$

 


Figure 1.3: Input signal and sampled signal

 


Figure 1.4: Sample and Hold

Introduction

Comparator

- Compares two input signals
- Outputs logic high or low

Introduction

Digital-to-Analog Converter

- R-2R ladder

$$V_{LSB} = V_{ref} \cdot \frac{1}{2^N}$$

$$BinVal = \sum_{i=0}^{N-1} 2^i \cdot b_i$$

$$V_{out} = V_{LSB} \cdot BinVal$$

$$V_{Max} = V_{ref} \cdot \frac{2^N - 1}{2^N}$$

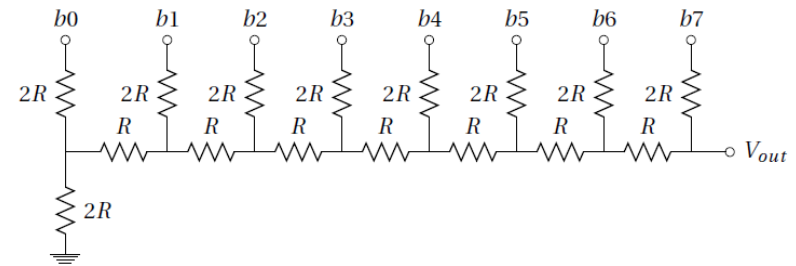


Figure 1.5: Example of 8-bit R-2R ladder

d7	d6	d5	d4	d3	d2	d1	d0	Voltage	Bit
0	0	0	0	0	0	0	1	4,687 mV	d0
0	0	0	0	0	0	1	0	9,375 mV	d1
0	0	0	0	0	1	0	0	18,75 mV	d2
0	0	0	0	1	0	0	0	37,50 mV	d3
0	0	0	1	0	0	0	0	75,00 mV	d4
0	0	1	0	0	0	0	0	150,0 mV	d5
0	1	0	0	0	0	0	0	300,0 mV	d6
1	0	0	0	0	0	0	0	600,0 mV	d7
1	1	1	1	1	1	1	1	1,195 mV	all

Table 3.2: Output voltage DAC

Introduction

SAR Logic

 


Figure 1.7: SAR logic block

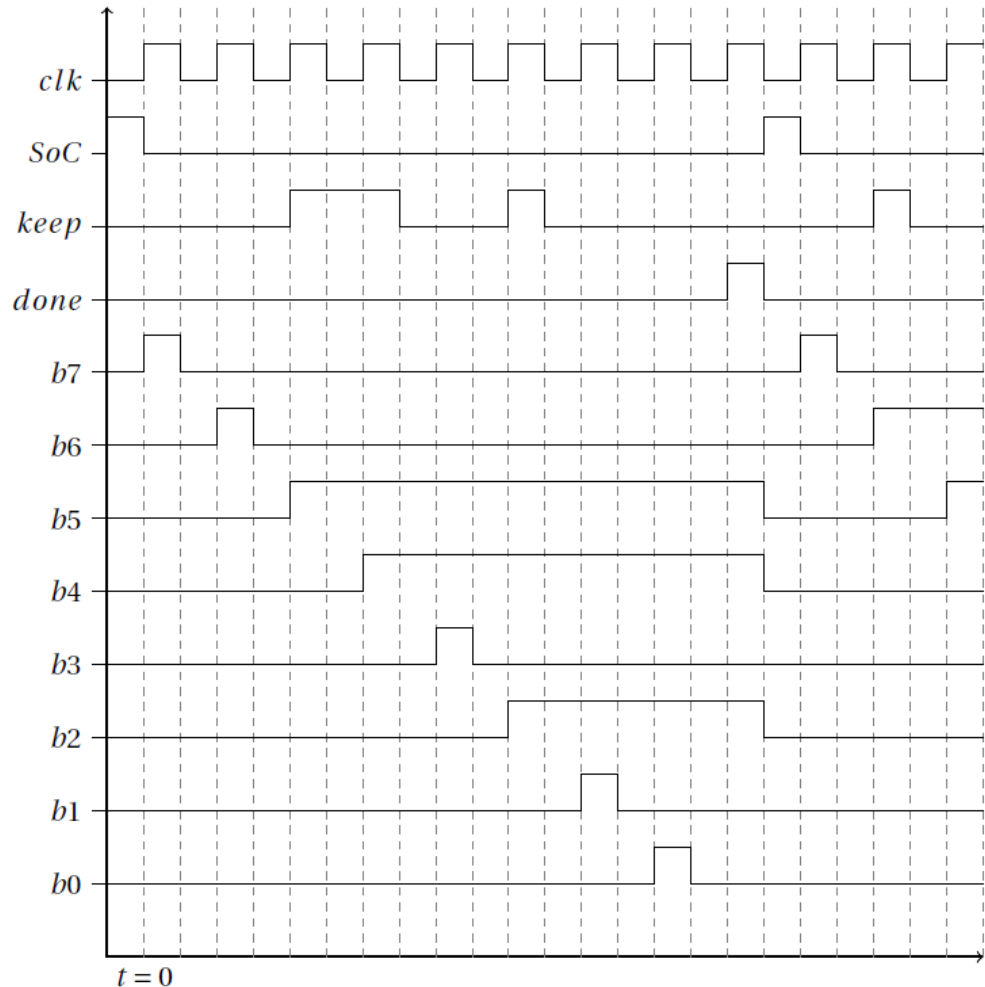


Figure 1.8: Typical timing diagram for the SAR logic block

Requirements

SAR ADC

- Input sampling rate: 1 M samples/s
- Output resolution: 8 bits
- Supply voltage: $VDD = 1.2 V$, and $VSS = 0 V$
- No missing codes

Requirements

DAC

- Sampling rate: 8 M samples/s
- Resolution: 8 bits
- Supply voltage: $V_{DD} = 1.2\text{ V}$, and $V_{SS} = 0\text{ V}$
- $\text{DNL} < \pm 0.5\text{ LSB}$
- $\text{INL} < \pm 0.5\text{ LSB}$
- $V_{OUT} (P-P) \geq 0.6\text{ V}$
- $C_{load} = 50\text{ fF}$

Requirements

Comparator

- Delay ≤ 0.5 clock cycle
- Supply Voltage: $V_{DD} = 1.2\text{ V}$ and $V_{SS} = 0\text{ V}$
- Offset < 0.5 LSB
- Gain $> V_{DD}/V_{ref}/2n$
- $C_{load} = 50\text{ fF}$

Results

- Sample-and-Hold
- Comparator
- Digital-to-Analog Converter
- SAR logic
- SR Latch
- Output buffers

Results

Sample-and-Hold Implementation and Layout

- Transmission gate
- Inverter

 


Figure 3.1: Sample and Hold design

 


Figure 3.3: Layout for Sample and hold without capacitor

Results

Sample-and-Hold Implementation and Layout

 


Figure 3.4: Layout for Sample and hold

Results

Sample-and-Hold Simulation

 


Figure 3.2: Sample and Hold simulation output

Results

Comparator Implementation and Layout

- Rail-to-rail input
- Large transistors

 


Figure 3.5: Comparator design

 


Figure 3.8: Layout for the Comparator

Results

Comparator Simulation

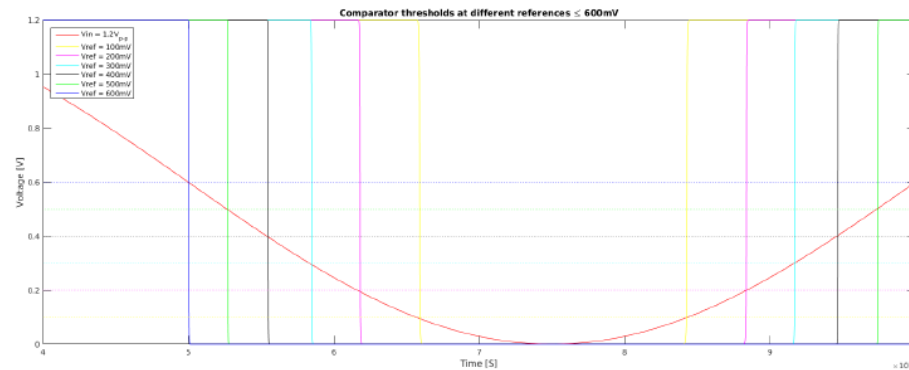


Figure 3.6: Comparator simulation output, $V_{ref} \leq 600mV$

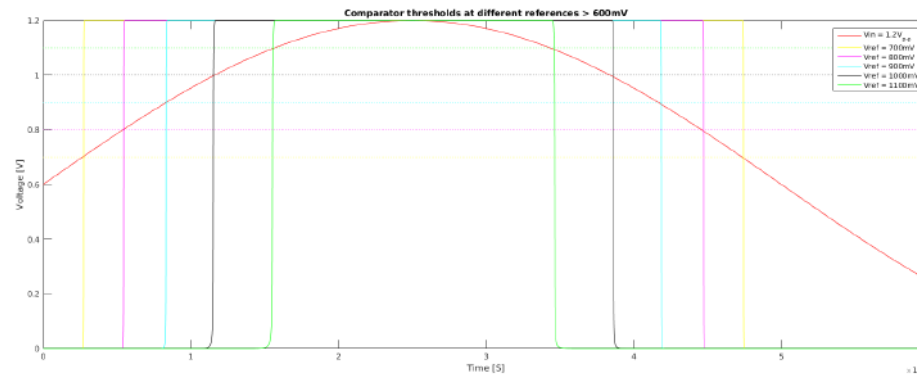


Figure 3.7: Sample and Hold simulation output, $V_{ref} > 600mV$

Results

Requirement fulfillment

- Achieved
 - Delay
 - Offset
 - Gain

Results

Digital-to-Analog Converter Implementation and Layout

- R-2R
- Buffers convert from 1V to 1.2V
- Each resistance divided in four
- $R = 320 \text{ k}\Omega$

 


Figure 3.16: Layout for DAC

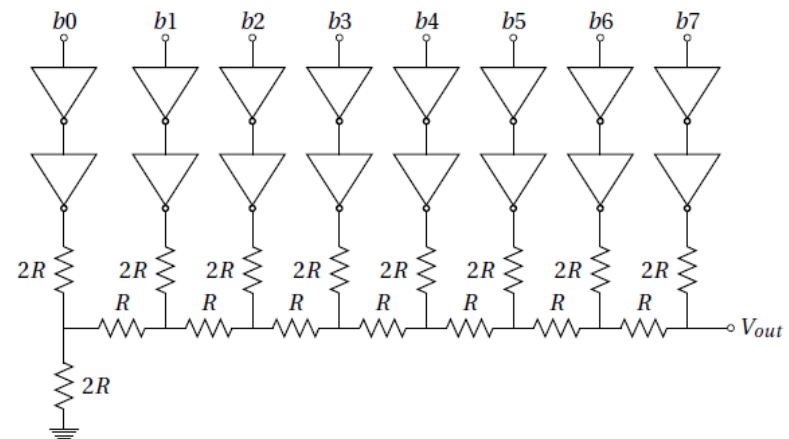


Figure 3.12: Implemented 8-bit R-2R ladder

Results

Digital-to-Analog Converter Simulation

$R = 10K$
 $2R = 20K$

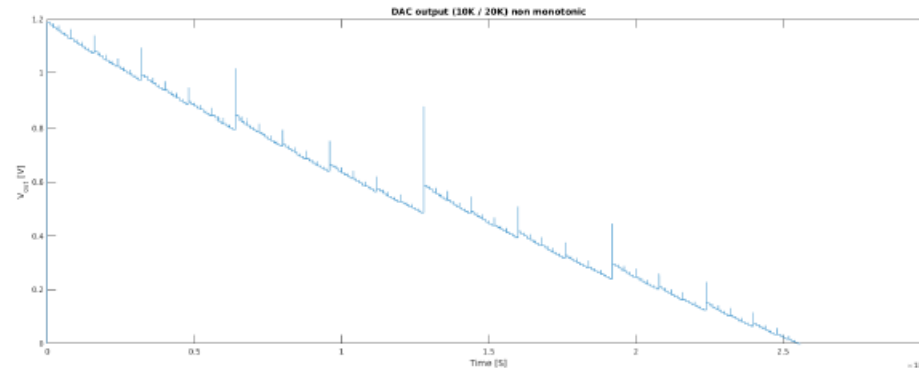


Figure 3.13: Simulation using 10k (20k) Ω

$R = 100K$
 $2R = 200K$

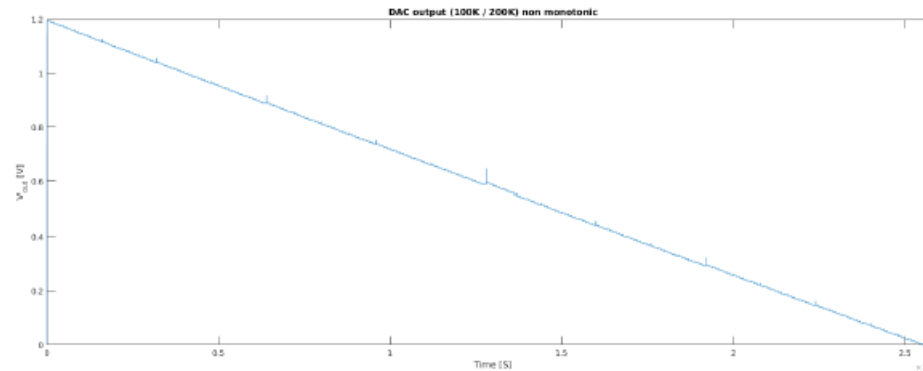


Figure 3.14: Simulation using 100k (200k) Ω

Results

Digital-to-Analog Converter Simulation

$R = 320K$
 $2R = 640K$

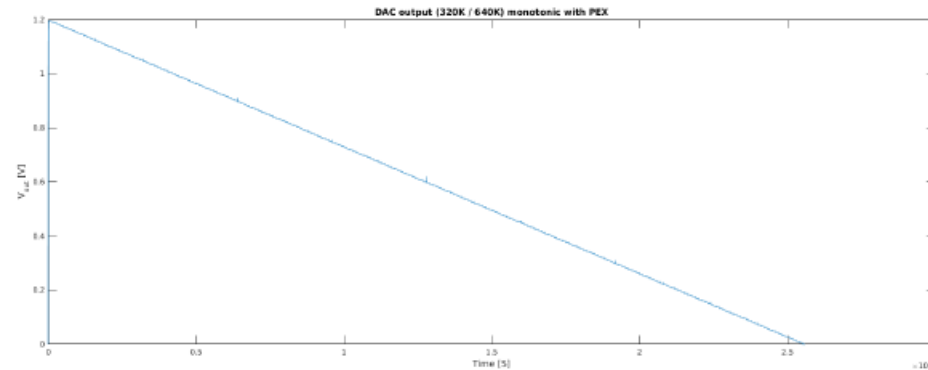


Figure 3.15: Simulation using 320k (640k) Ω

Results

Requirement fulfillment

- Achieved
 - Sampling rate of 8 M samples/s (10 M ok)
 - INL and DNL (software calculations)
 - Monotonic
 - Output voltage

Results

SAR logic

- Not simulated on its own
- Verified with the complete system

Results

SR Latch

- Needed to include SR Latch for control of sample-and-hold

S	R	Q	\bar{Q}
0	0	NC	NC
0	1	0	1
1	0	1	0
1	1	0	1

Table 3.3: SR latch function table

 


Figure 3.18: SR latch

 


Figure 3.19: Layout for the SR Latch

Results

Output buffers

- High impedance for the DAC
- Not simulated

 


Figure 3.20: Output buffers

 


Figure 3.21: Layout for the Output buffers

Results

SAR System Implementation and Layout

- The total area consumed:
 - $220\mu m \times 140\mu m$

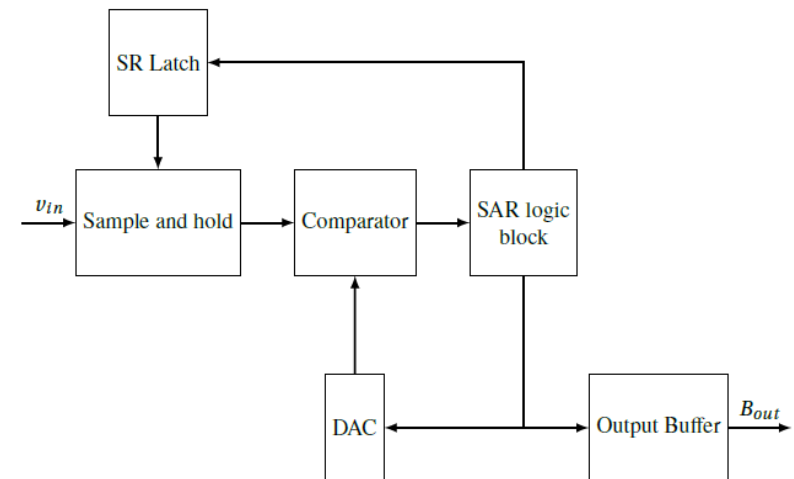


Figure 3.22: Block diagram representing the complete system

Results

SAR System Implementation and Layout

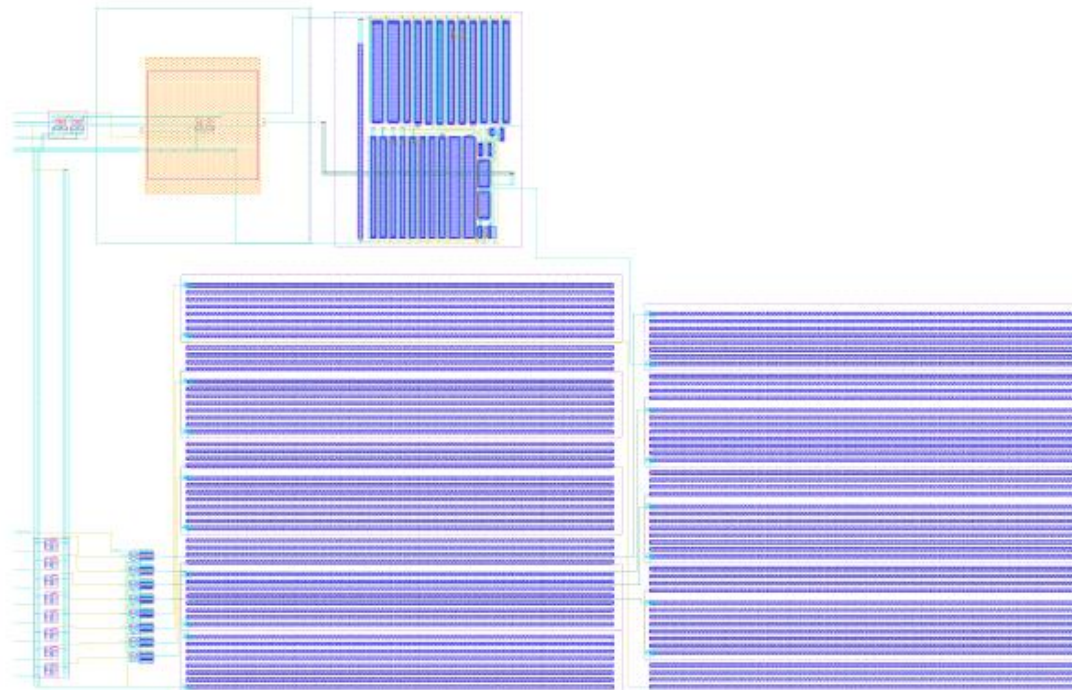


Figure 3.24: Implementation of the SAR system in layout

Results

SAR System Simulation

 


Figure 3.26: SAR system performance dynamics

Results

Requirement fulfillment

- Achieved
 - Input sampling rate of 1 M samples/s
 - Output resolution: 8 bits
- Not Verified
 - No missing codes

Conclusion

- Improvements
 - DAC design
 - SR latch
 - Layout
- Almost all requirements fulfilled