

CHAPTER 6 – CMOS OPERATIONAL AMPLIFIERS

INTRODUCTION

Chapter Outline

- 6.1 CMOS Op Amps
- 6.2 Compensation of Op Amps
- 6.3 Two-Stage Operational Amplifier Design
- 6.4 Cascode Op Amps
- 6.5 Simulation and Measurement of Op Amps
- 6.6 Macromodels for Op Amps
- 6.7 Summary

Hierarchical Perspective:

The op amps in this chapter represent an example of a reasonable complex circuit. The blocks and sub-blocks of the last two chapters will be used to implement the op amp in this chapter.

Chapter 6 →

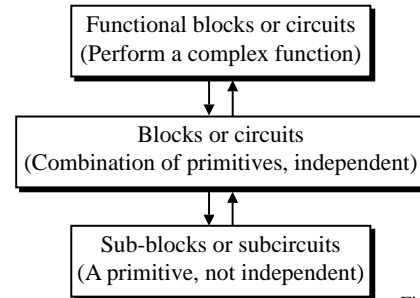


Fig. 6.0-1

What is an Op Amp?

The op amp (operational amplifier) is a high gain, dc coupled amplifier designed to be used with negative feedback to precisely define a closed loop transfer function.

The basic requirements for an op amp:


- Sufficiently large gain (the accuracy of the signal processing determines this)
- Differential inputs
- Frequency characteristics that permit stable operation when negative feedback is applied

Other requirements:

- High input impedance
- Low output impedance
- High speed/frequency

Why Op Amps?

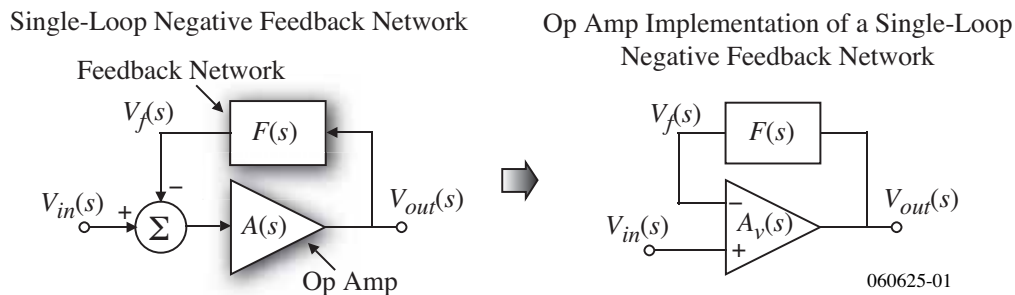The op amp is designed to be used with single-loop, negative feedback to accomplish precision signal processing as illustrated below.



The voltage gain, $\frac{V_{out}(s)}{V_{in}(s)}$, can be shown to be equal to,

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{A_v(s)}{1 + A_v(s)F(s)}$$

If the product of $A_v(s)F(s)$ is much greater than 1, then the voltage gain becomes,

$$\frac{V_{out}(s)}{V_{in}(s)} \approx \frac{1}{F(s)} \quad \Rightarrow \quad \text{The precision of the voltage gain is defined by } F(s).$$

SECTION 6.1 – CMOS OPERATIONAL AMPLIFIERS

APPLICATION OF THE OP AMP

Ideal Op Amp

Symbol:

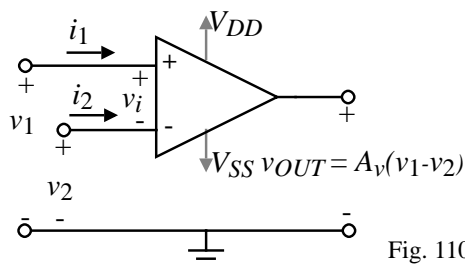


Fig. 110-02

Null port:

If the differential gain of the op amp is large enough then input terminal pair becomes a null port.

A null port is a pair of terminals where the voltage is zero and the current is zero.

I.e.,


$$v_1 - v_2 = v_i = 0$$

and

$$i_1 = 0 \text{ and } i_2 = 0$$

Therefore, ideal op amps can be analyzed by assuming the differential input voltage is zero and that no current flows into or out of the differential inputs.

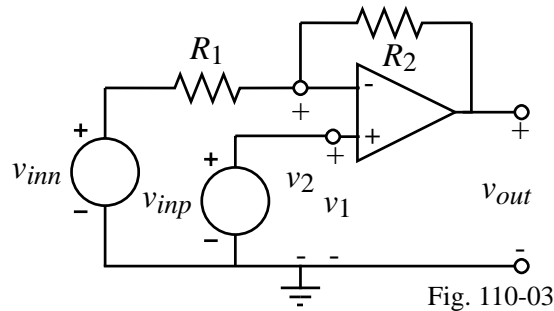General Configuration of the Op Amp as a Voltage Amplifier



Non-inverting voltage amplifier:


$$v_{inn} = 0 \quad \Rightarrow \quad v_{out} = \left(\frac{R_1 + R_2}{R_1} \right) v_{inp}$$

Inverting voltage amplifier:

$$v_{inn} = 0 \quad \Rightarrow \quad v_{out} = - \left(\frac{R_2}{R_1} \right) v_{inp}$$

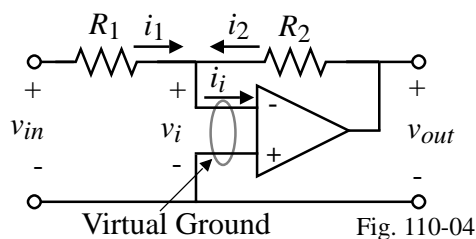Example 6.1-1 - Simplified Analysis of an Op Amp Circuit

The circuit shown below is an inverting voltage amplifier using an op amp. Find the voltage transfer function, v_{out}/v_{in} .



Solution

If $A_v \rightarrow \infty$, then $v_i \rightarrow 0$ because of the negative feedback path through R_2 .

(The op amp with $-fb.$ makes its input terminal voltages equal.)

$$v_i = 0 \text{ and } i_i = 0$$

Note that the null port becomes the familiar *virtual ground* if one of the op amp input terminals is on ground. If this is the case, then we can write that

$$i_1 = \frac{v_{in}}{R_1} \quad \text{and} \quad i_2 = \frac{v_{out}}{R_2}$$

Since, $i_i = 0$, then $i_1 + i_2 = 0$ giving the desired result as $\frac{v_{out}}{v_{in}} = - \frac{R_2}{R_1}$.

Example 6.1-2 – A More Challenging Example of Ideal Op Amp Analysis


Solve for Z_{in} of the op amp circuit shown assuming the op amps are ideal.

Solution

Relationships enforced
by the op amps:

- 1.) $I_{in} = I_1$
- 2.) $V_1 = V_2$
- 3.) $I_2 + I_3 = 0$
- 4.) $V_3 = V_4$
- 5.) $I_4 + I_5 = 0$
- 6.) $V_{in} = V_5$

$$Z_{in}(s) = \frac{V_{in}}{I_{in}}$$

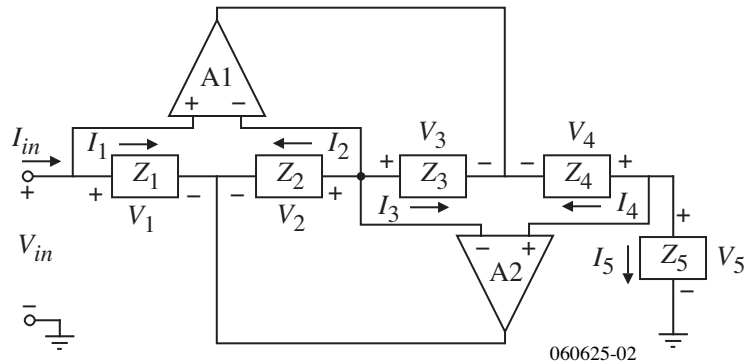

Therefore,


$$I_{in} = I_1 = \frac{V_1}{Z_1} = \frac{V_2}{Z_1} = \frac{I_2 Z_2}{Z_1} = \frac{-I_3 Z_2}{Z_1} = \frac{-V_3 Z_2}{Z_1 Z_3} = \frac{-V_4 Z_2}{Z_1 Z_3} = \frac{-I_4 Z_2 Z_4}{Z_1 Z_3} = \frac{I_5 Z_2 Z_4}{Z_1 Z_3}$$

Now, solve for Z_{in} ,

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_5}{I_{in}} = \frac{V_5 Z_1 Z_3}{I_5 Z_2 Z_4} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

OP AMP CHARACTERIZATION**Linear and Static Characterization of the CMOS Op Amp**

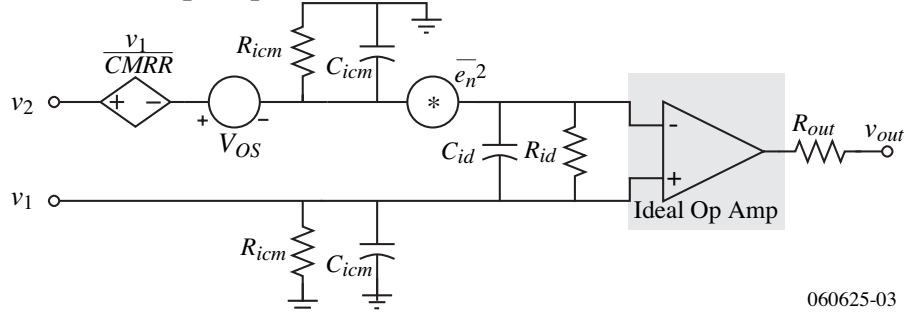A model for a nonideal op amp that includes some of the linear, static nonidealities:



where

R_{id} = differential input resistance

C_{id} = differential input capacitance

R_{icm} = common mode input resistance

C_{icm} = common mode input capacitance

V_{OS} = input-offset voltage

$CMRR$ = common-mode rejection ratio (when $v_1 = v_2$ an output results)

e_n^2 = voltage-noise spectral density (mean-square volts/Hertz)

Linear and Dynamic Characteristics of the Op Amp


Differential and common-mode frequency response:

$$V_{out}(s) = A_v(s)[V_1(s) - V_2(s)] \pm A_c(s) \left(\frac{V_1(s) + V_2(s)}{2} \right)$$

Differential-frequency response:

$$A_v(s) = \frac{A_{v0}}{\left(\frac{s}{p_1} - 1\right)\left(\frac{s}{p_2} - 1\right)\left(\frac{s}{p_3} - 1\right)\cdots} = \frac{A_{v0} p_1 p_2 p_3 \cdots}{(s - p_1)(s - p_2)(s - p_3) \cdots}$$

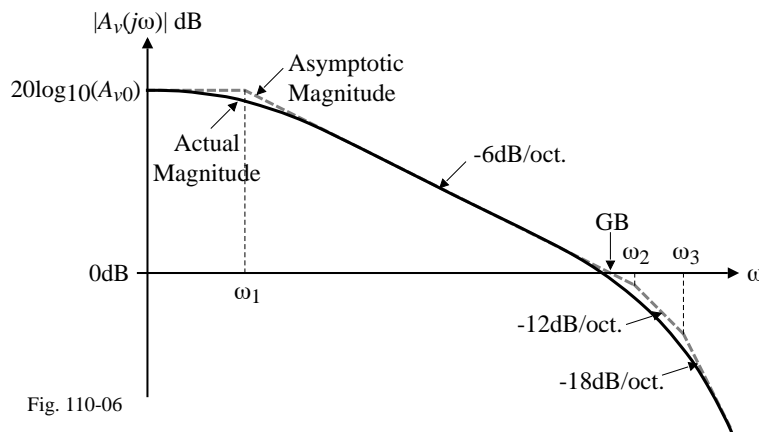where p_1, p_2, p_3, \dots are the poles of the differential-frequency response (ignoring zeros).



Other Characteristics of the Op Amp

Power supply rejection ratio ($PSRR$):

$$PSRR = \frac{\Delta V_{DD}}{\Delta V_{OUT}} A_v(s) = \frac{V_o/V_{in} (V_{dd} = 0)}{V_o/V_{dd} (V_{in} = 0)}$$


Input common mode range ($ICMR$):

$ICMR$ = the voltage range over which the input common-mode signal can vary without influence the differential performance

Slew rate (SR):

SR = output voltage rate limit of the op amp

Settling time (T_s):

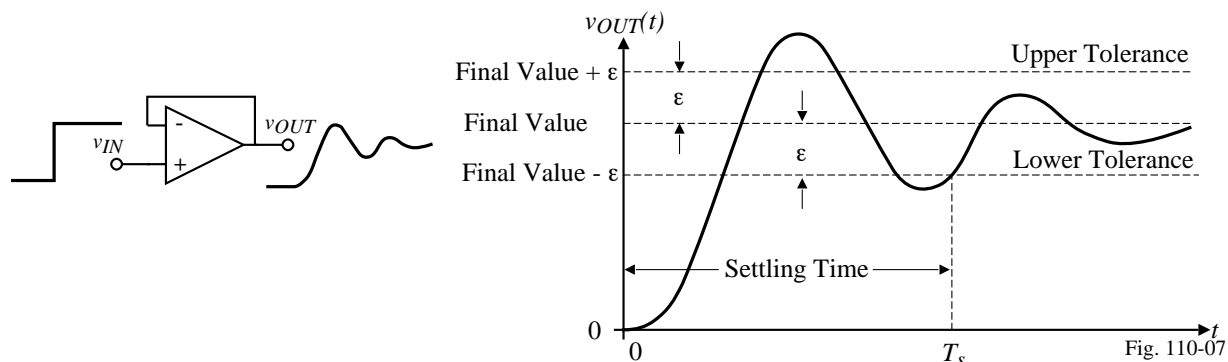

OP AMP CATEGORIZATION

Classification of CMOS Op Amps

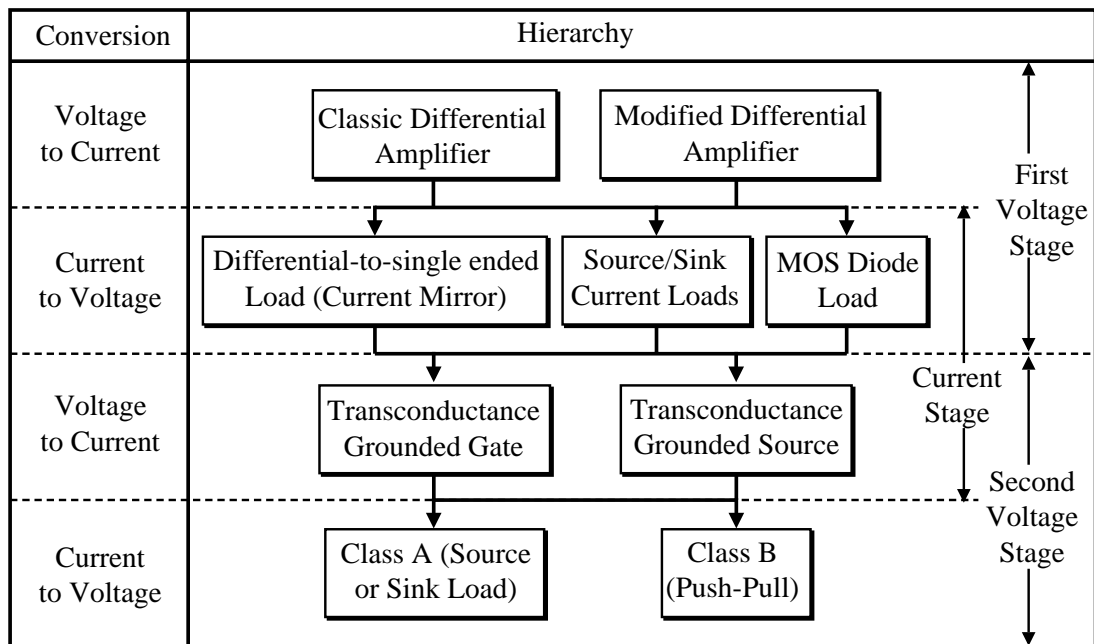


Table 110-01

Two-Stage CMOS Op Amp

Classical two-stage CMOS op amp broken into voltage-to-current and current-to-voltage stages:


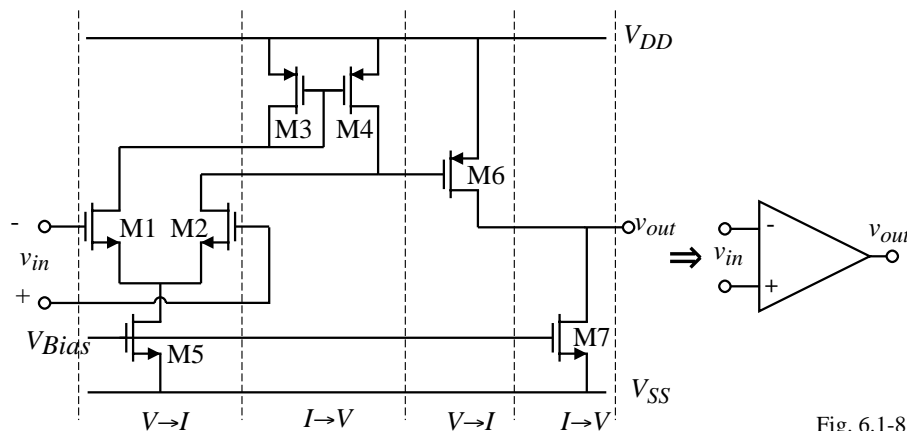


Fig. 6.1-8

Folded Cascode CMOS Op Amp

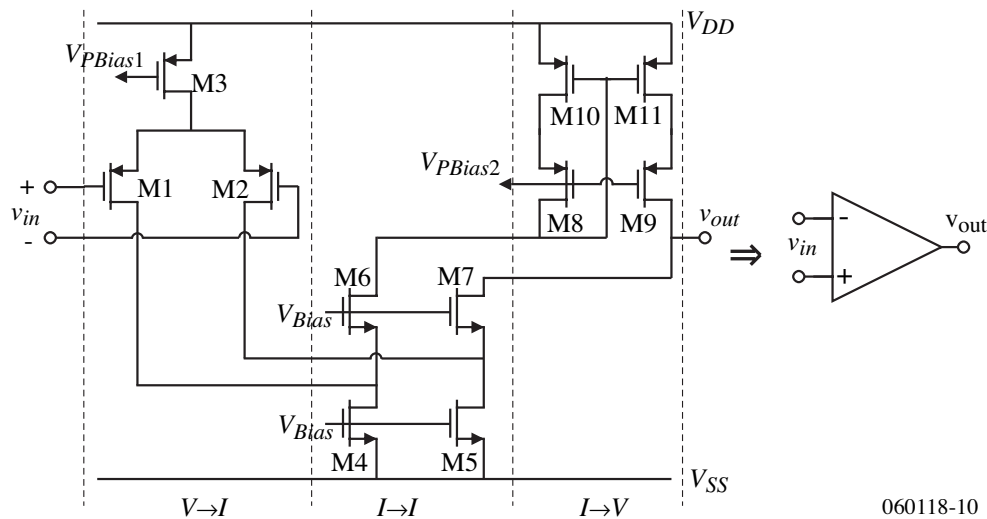Folded cascode CMOS op amp broken into stages.



DESIGN OF CMOS OP AMPS

Steps in Designing a CMOS Op Amp

Steps:

- 1.) Choosing or creating the basic structure of the op amp.
This step results in a schematic showing the transistors and their interconnections. This diagram does not change throughout the remainder of the design unless the specifications cannot be met, then a new or modified structure must be developed.
- 2.) Selection of the dc currents and transistor sizes.
Most of the effort of design is in this category.
Simulators are used to aid the designer in this phase.
- 3.) Physical implementation of the design.
Layout of the transistors
Floorplanning the connections, pin-outs, power supply buses and grounds
Extraction of the physical parasitics and re-simulation
Verification that the layout is a physical representation of the circuit.
- 4.) Fabrication
- 5.) Measurement
Verification of the specifications
Modification of the design as necessary

Design Inputs

Boundary conditions:

1. Process specification (V_T , K' , C_{ox} etc.)
2. Supply voltage and range
3. Supply current and range
4. Operating temperature and range

Requirements:

1. Gain
2. Gain bandwidth
3. Settling time
4. Slew rate
5. Common-mode input range, $ICMR$
6. Common-mode rejection ratio, $CMRR$
7. Power-supply rejection ratio, $PSRR$
8. Output-voltage swing
9. Output resistance
10. Offset
11. Noise
12. Layout area


Specifications for a Typical Unbuffered CMOS Op Amp

Boundary Conditions	Requirement
Process Specification	See Tables 3.1-1 and 3.1-2
Supply Voltage	$\pm 2.5\text{ V} \pm 10\%$
Supply Current	$100\text{ }\mu\text{A}$
Temperature Range	$0\text{ to }70^\circ\text{C}$
Specifications	Value
Gain	$\geq 70\text{ dB}$
Gainbandwidth	$\geq 5\text{ MHz}$
Settling Time	$\leq 1\text{ }\mu\text{sec}$
Slew Rate	$\geq 5\text{ V}/\mu\text{sec}$
Input CMR	$\geq \pm 1.5\text{ V}$
$CMRR$	$\geq 60\text{ dB}$
$PSRR$	$\geq 60\text{ dB}$
Output Swing	$\geq \pm 1.5\text{ V}$
Output Resistance	N/A, capacitive load only
Offset	$\leq \pm 10\text{ mV}$
Noise	$\leq 100\text{ nV}/\sqrt{\text{Hz}}$ at 1 KHz
Layout Area	$\leq 10,000\text{ min. channel length}^2$

Outputs of Op Amp Design

The basic outputs of design are:

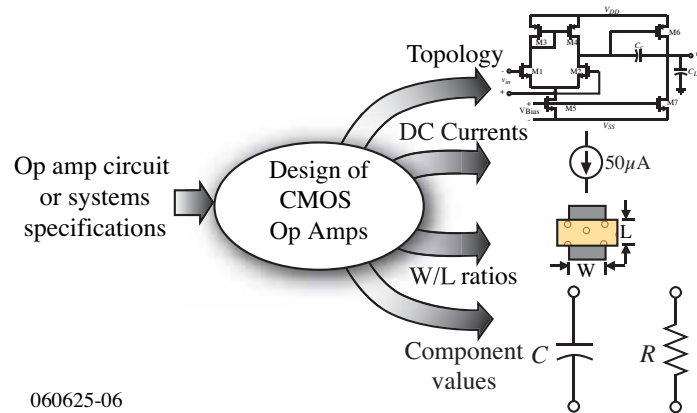- 1.) The topology
- 2.) The dc currents
- 3.) The W and L values of transistors
- 4.) The values of components



060625-06

Some Practical Thoughts on Op Amp Design

- 1.) Decide upon a suitable topology.
 - Experience is a great help
 - The topology should be the one capable of meeting most of the specifications
 - Try to avoid “inventing” a new topology but start with an existing topology
- 2.) Determine the type of compensation needed to meet the specifications.
 - Consider the load and stability requirements
 - Use some form of Miller compensation or a self-compensated approach
- 3.) Design dc currents and device sizes for proper dc, ac, and transient performance.
 - This begins with hand calculations based upon approximate design equations.
 - Compensation components are also sized in this step of the procedure.
 - After each device is sized by hand, a circuit simulator is used to fine tune the design

Two basic steps of design:

- 1.) “First-cut” - this step is to use hand calculations to propose a design that has potential of satisfying the specifications. Design robustness is developed in this step.
- 2.) Optimization - this step uses the computer to refine and optimize the design.

SECTION 6.2 - COMPENSATION OF OP AMPS

INTRODUCTION TO COMPENSATION

Compensation

Objective

Objective of compensation is to achieve stable operation when negative feedback is applied around the op amp.

Types of Compensation

1. Miller - Use of a capacitor feeding back around a high-gain, inverting stage.
 - Miller capacitor only
 - Miller capacitor with an unity-gain buffer to block the forward path through the compensation capacitor. Can eliminate the RHP zero.
 - Miller with a nulling resistor. Similar to Miller but with an added series resistance to gain control over the RHP zero.
2. Self compensating - Load capacitor compensates the op amp (later).
3. Feedforward - Bypassing a positive gain amplifier resulting in phase lead. Gain can be less than unity.

Because compensation plays such a strong role in design, it is considered before design.

Single-Loop, Negative Feedback Systems

Block diagram:

$A(s)$ = differential-mode voltage gain of the op amp

$F(s)$ = feedback transfer function from the output of op amp back to the input.

Definitions:

- Open-loop gain = $L(s) = -A(s)F(s)$
- Closed-loop gain = $\frac{V_{out}(s)}{V_{in}(s)} = \frac{A(s)}{1+A(s)F(s)}$

Stability Requirements:

The requirements for stability for a single-loop, negative feedback system is,

$$|A(j\omega_0^\circ)F(j\omega_0^\circ)| = |L(j\omega_0^\circ)| < 1$$

where $\omega_0^\circ = \omega_{360^\circ}$ is defined as

$$\text{Arg}[-A(j\omega_0^\circ)F(j\omega_0^\circ)] = \text{Arg}[L(j\omega_0^\circ)] = 0^\circ = 360^\circ$$

Another convenient way to express this requirement is

$$\text{Arg}[-A(j\omega_{0\text{dB}})F(j\omega_{0\text{dB}})] = \text{Arg}[L(j\omega_{0\text{dB}})] > 0^\circ$$

where $\omega_{0\text{dB}}$ is defined as

$$|A(j\omega_{0\text{dB}})F(j\omega_{0\text{dB}})| = |L(j\omega_{0\text{dB}})| = 1$$


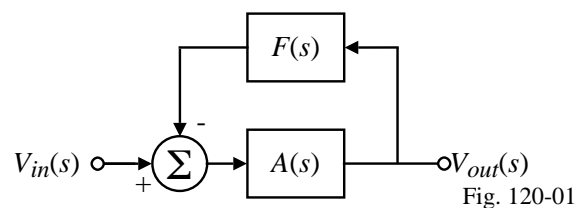


Illustration of the Stability Requirement using Bode Plots

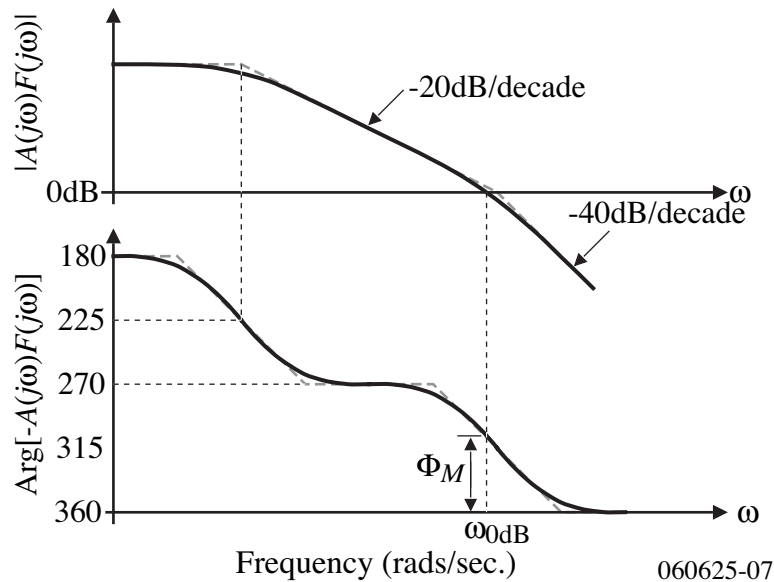


A measure of stability is given by the phase when $|A(j\omega)F(j\omega)| = 1$. This phase is called *phase margin*.

$$\text{Phase margin} = \Phi_M = 360^\circ - \text{Arg}[-A(j\omega_{0\text{dB}})F(j\omega_{0\text{dB}})] = 360^\circ - \text{Arg}[L(j\omega_{0\text{dB}})]$$

Why Do We Want Good Stability?

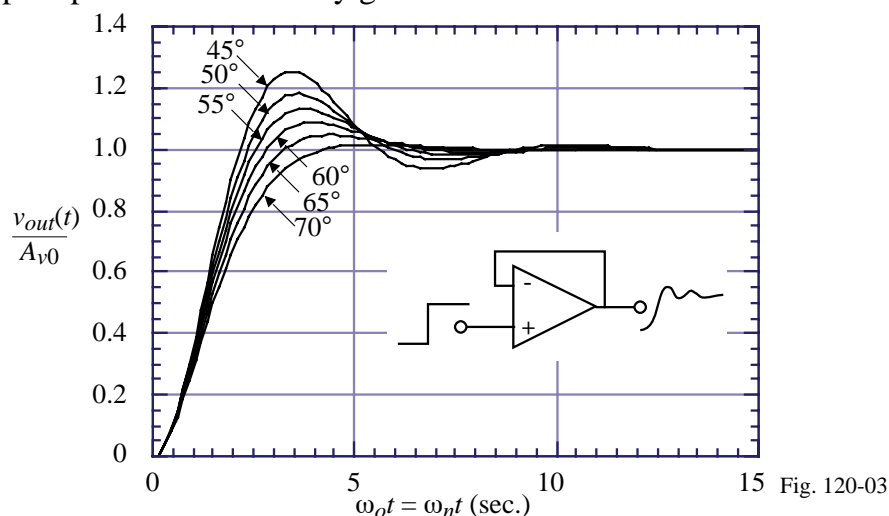Consider the step response of second-order system which closely models the closed-loop gain of the op amp connected in unity gain.



A “good” step response is one that quickly reaches its final value.

Therefore, we see that phase margin should be at least 45° and preferably 60° or larger. (A rule of thumb for satisfactory stability is that there should be less than three rings.)

Note that good stability is not necessarily the quickest risetime.

Uncompensated Frequency Response of Two-Stage Op Amps

Two-Stage Op Amps:

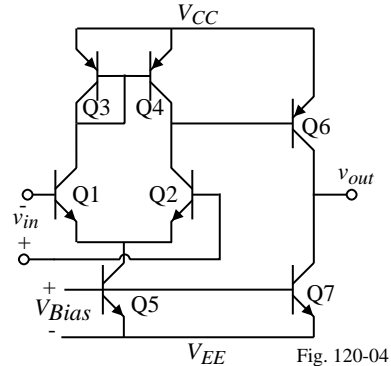
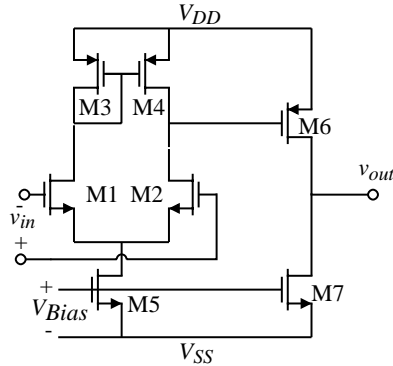


Fig. 120-04

Small-Signal Model:

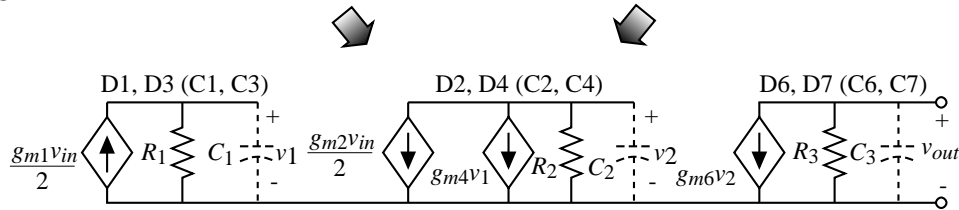


Fig. 120-05

Note that this model neglects the base-collector and gate-drain capacitances for purposes of simplification.

Uncompensated Frequency Response of Two-Stage Op Amps - Continued

For the MOS two-stage op amp:

$$R_1 \approx \frac{1}{g_{m3}} \parallel r_{ds3} \parallel r_{ds1} \approx \frac{1}{g_{m3}}$$

$$R_2 = r_{ds2} \parallel r_{ds4}$$

$$\text{and } R_3 = r_{ds6} \parallel r_{ds7}$$

$$C_1 = C_{gs3} + C_{gs4} + C_{bd1} + C_{bd3}$$

$$C_2 = C_{gs6} + C_{bd2} + C_{bd4}$$

$$\text{and } C_3 = C_L + C_{bd6} + C_{bd7}$$

For the BJT two-stage op amp:

$$R_1 = \frac{1}{g_{m3}} \parallel r_{\pi3} \parallel r_{\pi4} \parallel r_{o1} \parallel r_{o3} \approx \frac{1}{g_{m3}}$$

$$R_2 = r_{\pi6} \parallel r_{o2} \parallel r_{o4} \approx r_{\pi6}$$

$$\text{and } R_3 = r_{o6} \parallel r_{o7}$$

$$C_1 = C_{\pi3} + C_{\pi4} + C_{cs1} + C_{cs3}$$

$$C_2 = C_{\pi6} + C_{cs2} + C_{cs4}$$

$$\text{and } C_3 = C_L + C_{cs6} + C_{cs7}$$

Assuming the pole due to C_1 is much greater than the poles due to C_2 and C_3 gives,

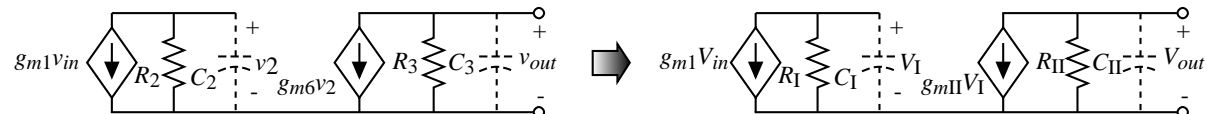



Fig. 120-06

The locations for the two poles are given by the following equations

$$p'_1 = \frac{-1}{R_I C_I} \quad \text{and} \quad p'_2 = \frac{-1}{R_{II} C_{II}}$$

where R_I (R_{II}) is the resistance to ground seen from the output of the first (second) stage and C_I (C_{II}) is the capacitance to ground seen from the output of the first (second) stage.

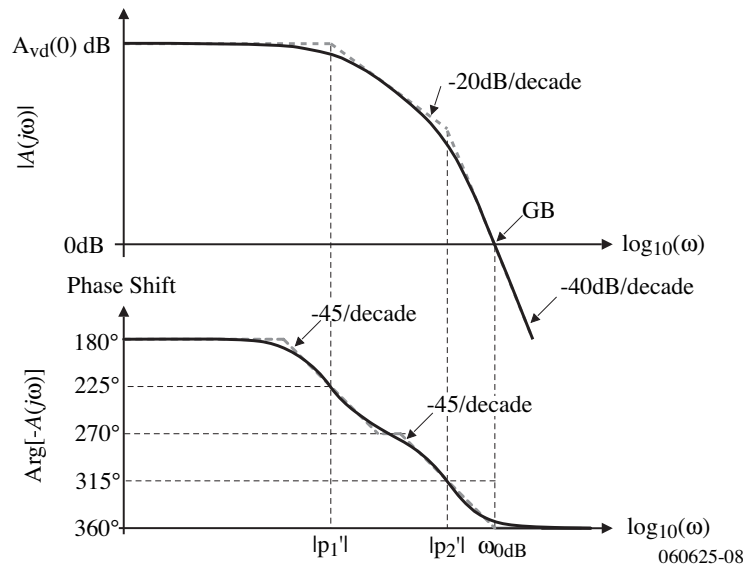Uncompensated Frequency Response of an Op Amp ($F(s) = 1$)



If we assume that $F(s) = 1$ (this is the worst case for stability considerations), then the above plot is the same as the loop gain.

Note that the phase margin is much less than 45° ($\approx 6^\circ$).

Therefore, the op amp must be compensated before using it in a closed-loop configuration.

MILLER COMPENSATION

Miller Compensation of the Two-Stage Op Amp

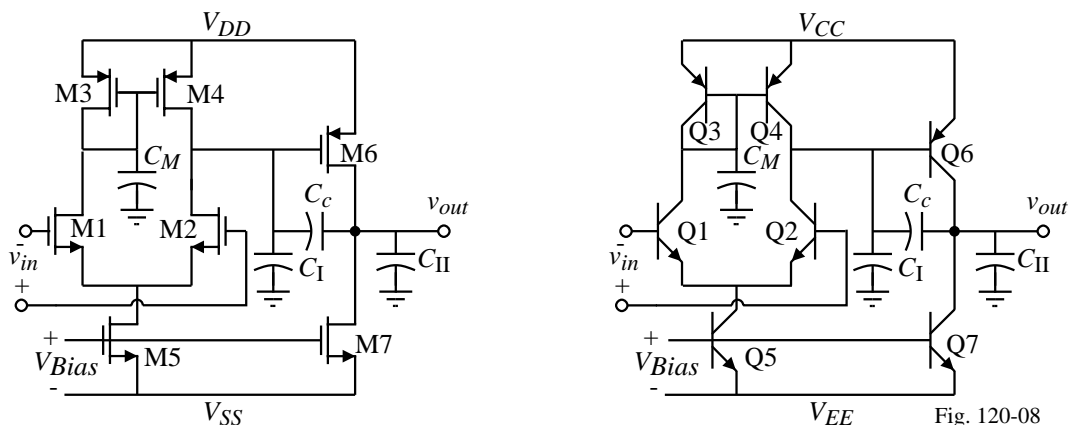


Fig. 120-08

The various capacitors are:

C_c = accomplishes the Miller compensation

C_M = capacitance associated with the first-stage mirror (mirror pole)

C_I = output capacitance to ground of the first-stage

C_{II} = output capacitance to ground of the second-stage

Compensated Two-Stage, Small-Signal Frequency Response Model Simplified

Use the CMOS op amp to illustrate:

1.) Assume that $g_{m3} \gg g_{ds3} + g_{ds1}$

2.) Assume that $\frac{g_{m3}}{C_M} \gg GB$

Therefore,


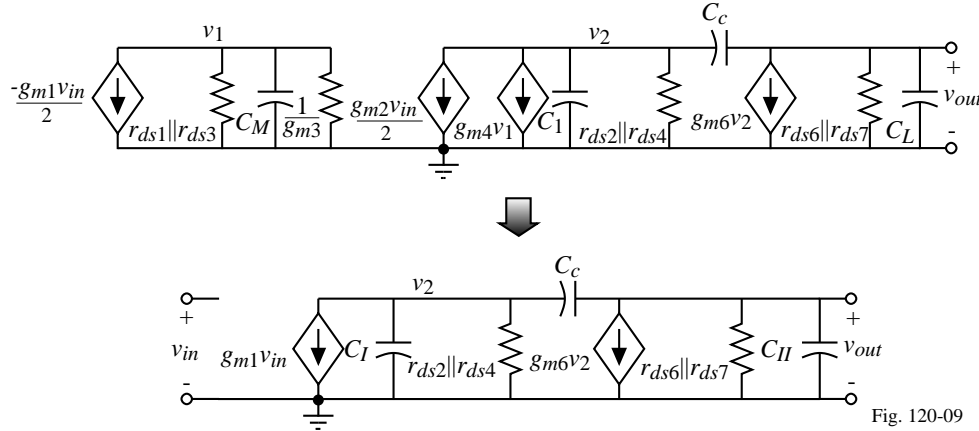


Fig. 120-09

Same circuit holds for the BJT op amp with different component relationships.

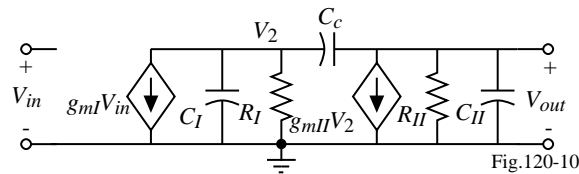General Two-Stage Frequency Response Analysis



where

$$g_{mI} = g_{m1} = g_{m2}, R_I = r_{ds2} || r_{ds4}, C_I = C_1$$

and

$$g_{mII} = g_{m6}, R_{II} = r_{ds6} || r_{ds7}, C_{II} = C_2 = C_L$$

Nodal Equations:

$$-g_{mI}V_{in} = [G_I + s(C_I + C_c)]V_2 - [sC_c]V_{out} \quad \text{and} \quad 0 = [g_{mII} - sC_c]V_2 + [G_{II} + sC_{II} + sC_c]V_{out}$$

Solving using Cramer's rule gives,

$$\begin{aligned} \frac{V_{out}(s)}{V_{in}(s)} &= \frac{g_{mI}(g_{mII} - sC_c)}{G_I G_{II} + s[G_{II}(C_I + C_{II}) + G_I(C_{II} + C_c) + g_{mII}C_c] + s^2[C_I C_{II} + C_c C_I + C_c C_{II}]} \\ &= \frac{A_o[1 - s(C_c/g_{mII})]}{1 + s[R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c] + s^2[R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II})]} \end{aligned}$$

where, $A_o = g_{mI}g_{mII}R_I R_{II}$

In general, $D(s) = \left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right) = 1 - s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2} \rightarrow D(s) \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$, if $|p_2| \gg |p_1|$

$$\therefore \quad p_1 = \frac{-1}{R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c} \approx \frac{-1}{g_{mII}R_I R_{II}C_c}, \quad z = \frac{g_{mII}}{C_c}$$

$$p_2 = \frac{-[R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c]}{R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II})} \approx \frac{-g_{mII}C_c}{C_I C_{II} + C_c C_I + C_c C_{II}} \approx \frac{-g_{mII}}{C_{II}}, \quad C_{II} > C_c > C_I$$

Summary of Results for Miller Compensation of the Two-Stage Op Amp

There are three roots of importance:

1.) Right-half plane zero:

$$z_1 = \frac{g_{mII}}{C_c} = \frac{g_{m6}}{C_c}$$

This root is very undesirable- it boosts the magnitude while decreasing the phase.

2.) Dominant left-half plane pole (the Miller pole):

$$p_1 \approx \frac{-1}{g_{mII}R_I R_{II} C_c} = \frac{-(g_{ds2} + g_{ds4})(g_{ds6} + g_{ds7})}{g_{m6} C_c}$$


This root accomplishes the desired compensation.

3.) Left-half plane output pole:

$$p_2 \approx \frac{-g_{mII}}{C_{II}} \approx \frac{-g_{m6}}{C_L}$$

This pole must be \geq unity-gainbandwidth or the phase margin will not be satisfied.

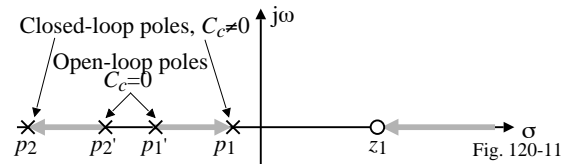
Root locus plot of the Miller compensation:



CMOS Analog Circuit Design

© P.E. Allen - 2006

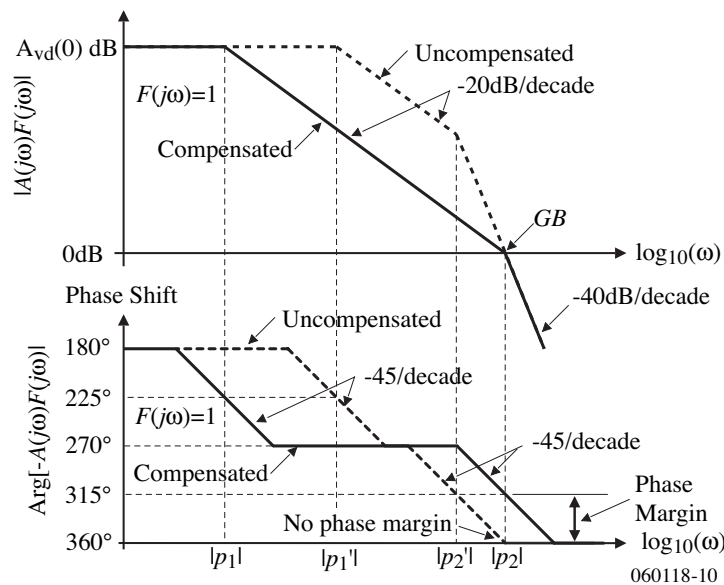Compensated Open-Loop Frequency Response of the Two-Stage Op Amp




Note that the unity-gainbandwidth, GB , is

$$GB = A_{vd}(0) \cdot |p_1| = (g_{mI} g_{mII} R_I R_{II}) \frac{1}{g_{mII} R_I R_{II} C_c} = \frac{g_{mI}}{C_c} = \frac{g_{m1}}{C_c} = \frac{g_{m2}}{C_c}$$

Conceptually, where do these roots come from?


1.) The Miller pole:

$$|p_1| \approx \frac{1}{R_I(g_{m6}R_{II}C_c)}$$

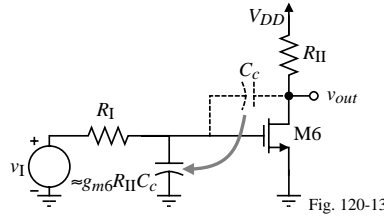

2.) The left-half plane output pole:


$$|p_2| \approx \frac{g_{m6}}{C_{II}}$$

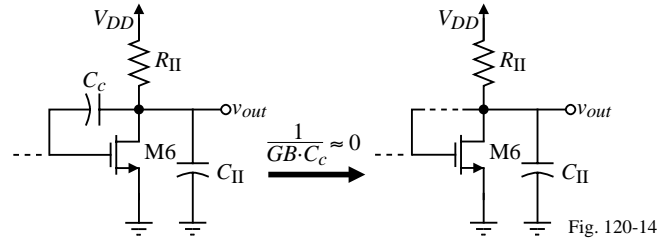

3.) Right-half plane zero (*One source of zeros is from multiple paths from the input to output*):

$$v_{out} = \left(\frac{-g_{m6}R_{II}(1/sC_c)}{R_{II} + 1/sC_c} \right) v' + \left(\frac{R_{II}}{R_{II} + 1/sC_c} \right) v'' = \frac{-R_{II} \left(\frac{g_{m6}}{sC_c} - 1 \right)}{R_{II} + 1/sC_c} v$$


where $v = v' = v''$.

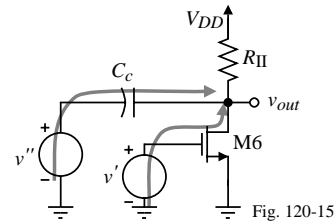

Further Comments on p_2

The previous observations on p_2 can be proved as follows:

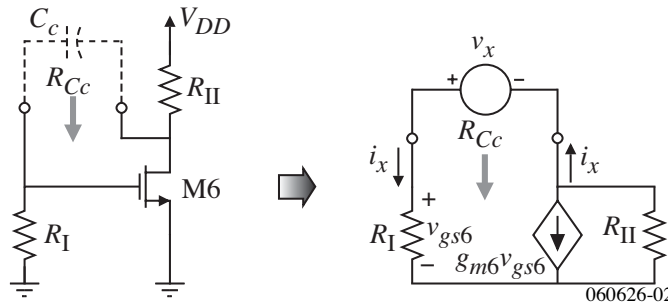Find the resistance R_{Cc} seen by the compensation capacitor, C_c .



$$v_x = i_x R_I + (i_x + g_{m6}v_{gs6})R_{II} = i_x R_I + (i_x + g_{m6}i_x R_I)R_{II}$$

Therefore,

$$R_{Cc} = \frac{v_x}{i_x} = R_I + (1 + g_{m6}R_I)R_{II} \approx g_{m6}R_I R_{II}$$

The frequency at which C_c begins to become a short is,

$$\frac{1}{\omega C_c} < g_{m6}R_I R_{II} \quad \text{or} \quad \omega > \frac{1}{g_{m6}R_I R_{II} C_c} \approx |p_1|$$

Thus, at the frequency where C_{II} begins to short the output, C_c is acting as a short.

Influence of the Mirror Pole

Up to this point, we have neglected the influence of the pole, p_3 , associated with the current mirror of the input stage. A small-signal model for the input stage that includes C_3 is shown below:

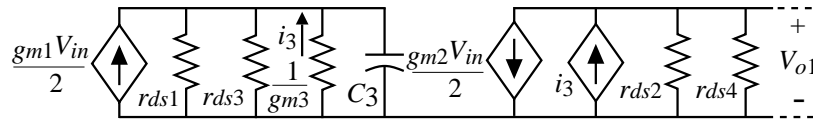


Fig. 120-16

The transfer function from the input to the output voltage of the first stage, $V_{o1}(s)$, can be written as

$$\frac{V_{o1}(s)}{V_{in}(s)} = \frac{-g_{m1}}{2(g_{ds2} + g_{ds4})} \left[\frac{g_{m3} + g_{ds1} + g_{ds3}}{g_{m3} + g_{ds1} + g_{ds3} + sC_3} + 1 \right] \approx \frac{-g_{m1}}{2(g_{ds2} + g_{ds4})} \left[\frac{sC_3 + 2g_{m3}}{sC_3 + g_{m3}} \right]$$

We see that there is a pole and a zero given as

$$p_3 = -\frac{g_{m3}}{C_3} \quad \text{and} \quad z_3 = -\frac{2g_{m3}}{C_3}$$

Summary of the Conditions for Stability of the Two-Stage Op Amp

- Unity-gainbandwidth is given as:

$$GB = A_v(0) \cdot |p_1| = (g_{mI} g_{mII} R_I R_{II}) \cdot \left(\frac{1}{g_{mII} R_I R_{II} C_c} \right) = \frac{g_{mI}}{C_c} = (g_{m1} g_{m2} R_1 R_2) \cdot \left(\frac{1}{g_{m2} R_1 R_2 C_c} \right) = \frac{g_{m1}}{C_c}$$

- The requirement for 45° phase margin is:

$$\pm 180^\circ - \text{Arg}[\text{Loop Gain}] = \pm 180^\circ - \tan^{-1} \left(\frac{\omega}{|p_1|} \right) - \tan^{-1} \left(\frac{\omega}{|p_2|} \right) - \tan^{-1} \left(\frac{\omega}{z} \right) = 45^\circ$$

Let $\omega = GB$ and assume that $z \geq 10GB$, therefore we get,

$$\pm 180^\circ - \tan^{-1} \left(\frac{GB}{|p_1|} \right) - \tan^{-1} \left(\frac{GB}{|p_2|} \right) - \tan^{-1} \left(\frac{GB}{z} \right) = 45^\circ$$

$$135^\circ \approx \tan^{-1}(A_v(0)) + \tan^{-1} \left(\frac{GB}{|p_2|} \right) + \tan^{-1}(0.1) = 90^\circ + \tan^{-1} \left(\frac{GB}{|p_2|} \right) + 5.7^\circ$$

$$39.3^\circ \approx \tan^{-1} \left(\frac{GB}{|p_2|} \right) \Rightarrow \frac{GB}{|p_2|} = 0.818 \Rightarrow |p_2| \geq 1.22GB$$

- The requirement for 60° phase margin:

$$|p_2| \geq 2.2GB \text{ if } z \geq 10GB$$

- If 60° phase margin is required, then the following relationships apply:


$$\frac{g_{m6}}{C_c} > \frac{10g_{m1}}{C_c} \Rightarrow g_{m6} > 10g_{m1} \quad \text{and} \quad \frac{g_{m6}}{C_2} > \frac{2.2g_{m1}}{C_c} \Rightarrow C_c > 0.22C_2$$

RIGHT-HALF PLANE ZERO

Controlling the Right-Half Plane Zero

Why is the RHP zero a problem?

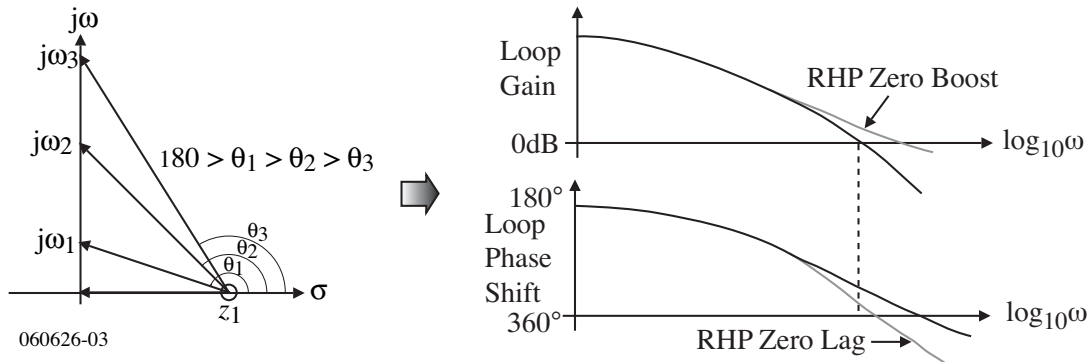Because it boosts the magnitude but lags the phase - the worst possible combination for stability.



Solution of the problem:

The compensation comes from the *feedback path* through C_C , but the RHP zero comes from the *feedforward path* through C_C so eliminate the feedforward path!

Use of Buffer to Eliminate the Feedforward Path through the Miller Capacitor

Model:

The transfer function is given by the following equation,

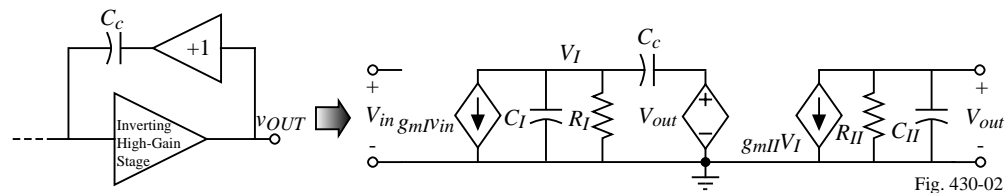


Fig. 430-02

$$\frac{V_o(s)}{V_{in}(s)} = \frac{(g_{mI})(g_{mII})(R_I)(R_{II})}{1 + s[R_IC_I + R_{II}C_{II} + R_IC_c + g_{mII}R_IR_{II}C_c] + s^2[R_IR_{II}C_{II}(C_I + C_c)]}$$

Using the technique as before to approximate p_1 and p_2 results in the following

$$p_1 \approx \frac{-1}{R_IC_I + R_{II}C_{II} + R_IC_c + g_{mII}R_IR_{II}C_c} \approx \frac{-1}{g_{mII}R_IR_{II}C_c}$$

and

$$p_2 \approx \frac{-g_{mII}C_c}{C_{II}(C_I + C_c)}$$

Comments:

Poles are approximately what they were before with the zero removed.

For 45° phase margin, $|p_2|$ must be greater than GB

For 60° phase margin, $|p_2|$ must be greater than $1.73GB$

Use of Buffer with Finite Output Resistance to Eliminate the RHP Zero

Assume that the unity-gain buffer has an output resistance of R_o .

Model:

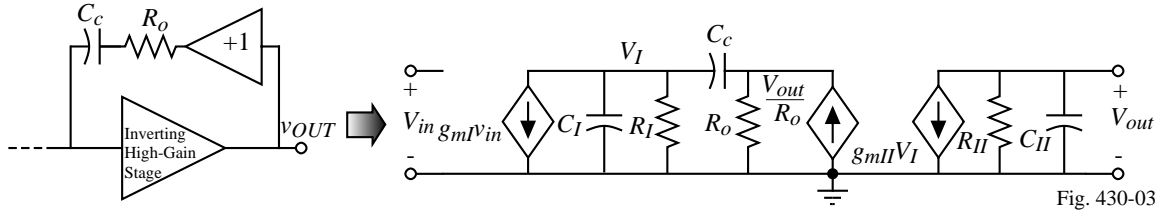


Fig. 430-03

It can be shown that if the output resistance of the buffer amplifier, R_o , is not neglected that another pole occurs at,

$$p_4 \approx \frac{-1}{R_o[C_I C_c / (C_I + C_c)]}$$

and a LHP zero at

$$z_2 \approx \frac{-1}{R_o C_c}$$

Closer examination shows that if a resistor, called a *nulling resistor*, is placed in series with C_c that the RHP zero can be eliminated or moved to the LHP.

Use of Nulling Resistor to Eliminate the RHP Zero (or turn it into a LHP zero)[†]

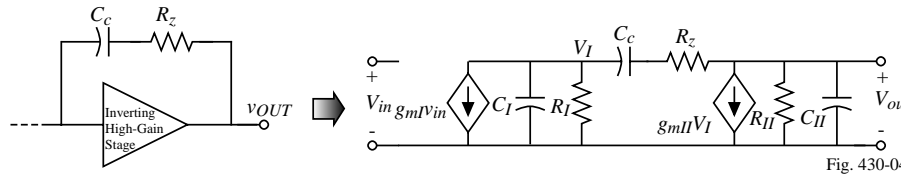


Fig. 430-04

Nodal equations:

$$g_{mI}V_{in} + \frac{V_I}{R_I} + sC_I V_I + \left(\frac{sC_c}{1 + sC_c R_z} \right) (V_I - V_{out}) = 0$$

$$g_{mII}V_I + \frac{V_o}{R_{II}} + sC_{II}V_{out} + \left(\frac{sC_c}{1 + sC_c R_z} \right) (V_{out} - V_I) = 0$$

Solution:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{a\{1 - s[(C_c/g_{mII}) - R_z C_c]\}}{1 + bs + cs^2 + ds^3}$$

where

$$a = g_{mI}g_{mII}R_I R_{II}$$

$$b = (C_{II} + C_c)R_{II} + (C_I + C_c)R_I + g_{mII}R_I R_{II}C_c + R_z C_c$$

$$c = [R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II}) + R_z C_c(R_I C_I + R_{II} C_{II})]$$

$$d = R_I R_{II} R_z C_I C_{II} C_c$$

[†] W.J. Parrish, "An Ion Implanted CMOS Amplifier for High Performance Active Filters", Ph.D. Dissertation, 1976, Univ. of CA., Santa Barbara.

Use of Nulling Resistor to Eliminate the RHP - Continued

If R_z is assumed to be less than R_I or R_{II} and the poles widely spaced, then the roots of the above transfer function can be approximated as

$$p_1 \approx \frac{-1}{(1 + g_{mII}R_{II})R_IC_c} \approx \frac{-1}{g_{mII}R_{II}R_IC_c}$$

$$p_2 \approx \frac{-g_{mII}C_c}{C_IC_{II} + C_cC_I + C_cC_{II}} \approx \frac{-g_{mII}}{C_{II}}$$

$$p_4 = \frac{-1}{R_zC_I}$$

and

$$z_1 = \frac{1}{C_c(1/g_{mII} - R_z)}$$

Note that the zero can be placed anywhere on the real axis.

Conceptual Illustration of the Nulling Resistor Approach

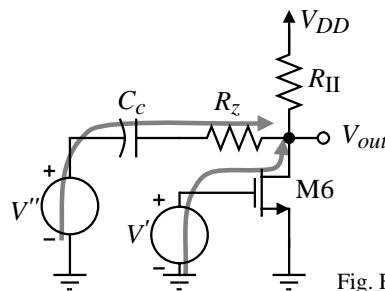


Fig. Fig. 430-05

The output voltage, V_{out} , can be written as

$$V_{out} = \frac{-g_{m6}R_{II}\left(R_z + \frac{1}{sC_c}\right)}{R_{II} + R_z + \frac{1}{sC_c}} V' + \frac{R_{II}}{R_{II} + R_z + \frac{1}{sC_c}} V'' = \frac{-R_{II}\left[g_{m6}R_z + \frac{g_{m6}}{sC_c} - 1\right]}{R_{II} + R_z + \frac{1}{sC_c}} V$$

when $V = V' = V''$.

Setting the numerator equal to zero and assuming $g_{m6} = g_{mII}$ gives,

$$z_1 = \frac{1}{C_c(1/g_{mII} - R_z)}$$

A Design Procedure that Allows the RHP Zero to Cancel the Output Pole, p_2

We desire that $z_1 = p_2$ in terms of the previous notation.

Therefore,

$$\frac{1}{C_c(1/g_{mII} - R_z)} = \frac{-g_{mII}}{C_{II}}$$

The value of R_z can be found as

$$R_z = \left(\frac{C_c + C_{II}}{C_c} \right) (1/g_{mII})$$

With p_2 canceled, the remaining roots are p_1 and p_4 (the pole due to R_z). For unity-gain stability, all that is required is that

$$|p_4| > A_v(0)|p_1| = \frac{A_v(0)}{g_{mII}R_{II}R_I C_c} = \frac{g_{mI}}{C_c}$$


and $(1/R_z C_I) > (g_{mI}/C_c) = GB$

Substituting R_z into the above inequality and assuming $C_{II} \gg C_c$ results in

$$C_c > \sqrt{\frac{g_{mI}}{g_{mII}}} C_I C_{II}$$

This procedure gives excellent stability for a fixed value of $C_{II} (\approx C_L)$.

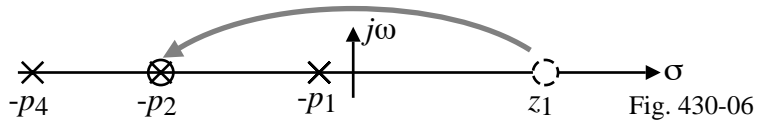Unfortunately, as C_L changes, p_2 changes and the zero must be readjusted to cancel p_2 .



Increasing the Magnitude of the Output Pole[†]

The magnitude of the output pole, p_2 , can be increased by introducing gain in the Miller capacitor feedback path. For example,

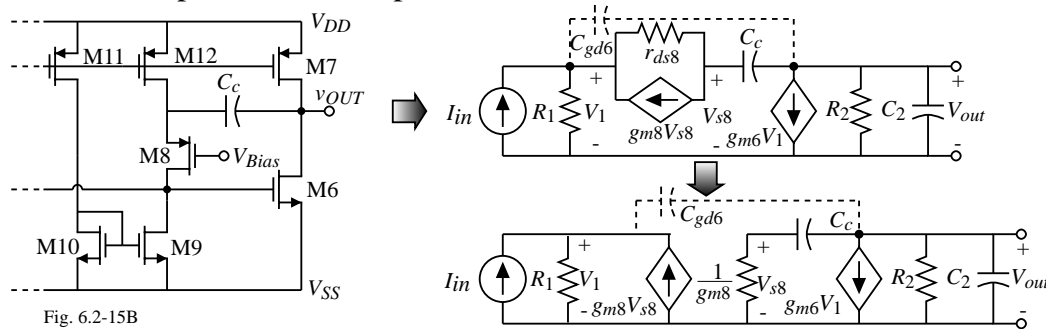


Fig. 6.2-15B

The resistors R_1 and R_2 are defined as

$$R_1 = \frac{1}{g_{ds2} + g_{ds4} + g_{ds9}} \quad \text{and} \quad R_2 = \frac{1}{g_{ds6} + g_{ds7}}$$

where transistors M2 and M4 are the output transistors of the first stage.

Nodal equations:

$$I_{in} = G_1 V_1 - g_{m8} V_{s8} = G_1 V_1 - \left(\frac{g_{m8} s C_c}{g_{m8} + s C_c} \right) V_{out} \quad \text{and} \quad 0 = g_{m6} V_1 + \left[G_2 + s C_2 + \frac{g_{m8} s C_c}{g_{m8} + s C_c} \right] V_{out}$$

[†] B.K. Ahuja, "An Improved Frequency Compensation Technique for CMOS Operational Amplifiers," *IEEE J. of Solid-State Circuits*, Vol. SC-18, No. 6 (Dec. 1983) pp. 629-633.

Increasing the Magnitude of the Output Pole - Continued

Solving for the transfer function V_{out}/I_{in} gives,

$$\frac{V_{out}}{I_{in}} = \left(\frac{-g_{m6}}{G_1 G_2} \right) \left[\frac{\left(1 + \frac{s C_c}{g_{m8}} \right)}{1 + s \left[\frac{C_c}{g_{m8}} + \frac{C_2}{G_2} + \frac{C_c}{G_2} + \frac{g_{m6} C_c}{G_1 G_2} \right] + s^2 \left(\frac{C_c C_2}{g_{m8} G_2} \right)} \right]$$

Using the approximate method of solving for the roots of the denominator gives

$$p_1 = \frac{-1}{\frac{C_c}{g_{m8}} + \frac{C_c}{G_2} + \frac{C_2}{G_2} + \frac{g_{m6} C_c}{G_1 G_2}} \approx \frac{-6}{g_{m6} r_{ds}^2 C_c}$$

$$\text{and } p_2 \approx \frac{-\frac{g_{m6} r_{ds}^2 C_c}{6}}{\frac{C_c C_2}{g_{m8} G_2}} = \frac{g_{m8} r_{ds}^2 G_2}{6} \left(\frac{g_{m6}}{C_2} \right) = \left(\frac{g_{m8} r_{ds}}{3} \right) |p_2'|$$

where all the various channel resistance have been assumed to equal r_{ds} and p_2' is the output pole for normal Miller compensation.


Result:

Dominant pole is approximately the same and the output pole is increased by $\approx g_{m6} r_{ds}$.

Increasing the Magnitude of the Output Pole - Continued

In addition there is a LHP zero at $-g_{m8}/s C_c$ and a RHP zero due to C_{gd6} (shown dashed in the model on Page 6.2-24) at g_{m6}/C_{gd6} .

Roots are:

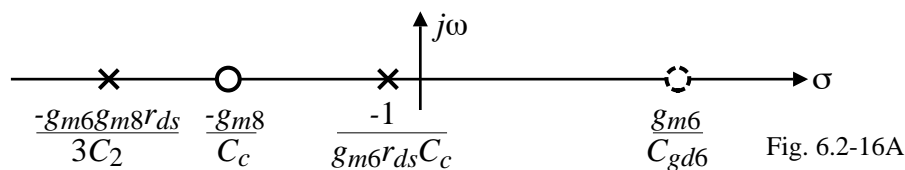

Concept Behind the Increasing of the Magnitude of the Output Pole

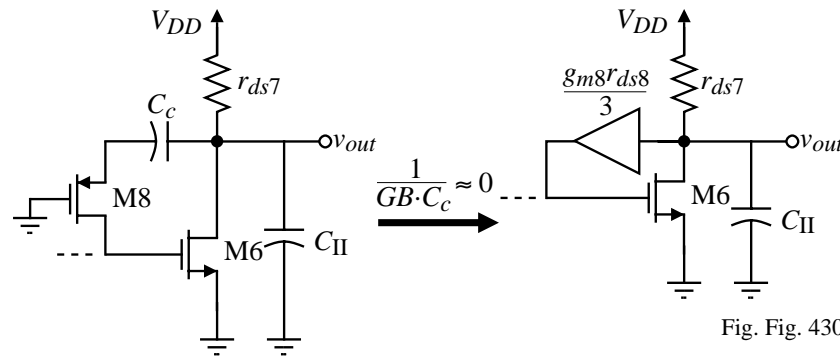


Fig. Fig. 430-08

$$R_{out} = r_{ds7} \parallel \left(\frac{3}{g_{m6}g_{m8}r_{ds8}} \right) \approx \frac{3}{g_{m6}g_{m8}r_{ds8}}$$

Therefore, the output pole is approximately,


$$|p_2| \approx \frac{g_{m6}g_{m8}r_{ds8}}{3C_{II}}$$

FINDING ROOTS BY INSPECTION


Identification of Poles from a Schematic

- 1.) Most poles are equal to the reciprocal product of the resistance from a node to ground and the capacitance connected to that node.
- 2.) Exceptions (generally due to feedback):

a.) Negative feedback:

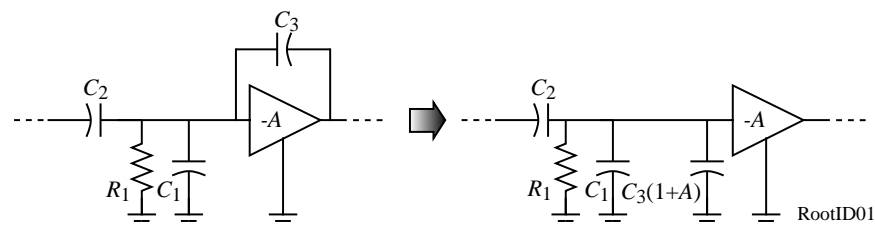


b.) Positive feedback ($A < 1$):

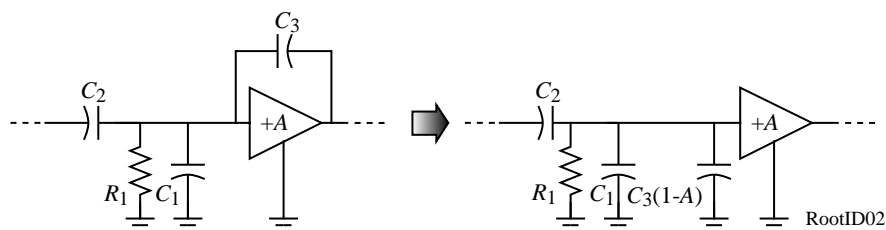


Identification of Zeros from a Schematic

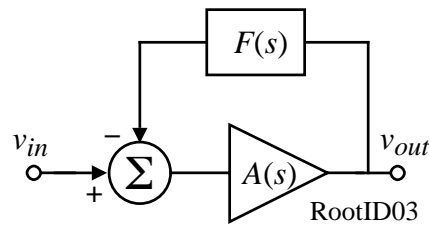1.) Zeros arise from poles in the feedback path.



$$\text{If } F(s) = \frac{1}{\frac{s}{p_1} + 1}, \text{ then } \frac{V_{out}}{V_{in}} = \frac{A(s)}{1 + A(s)F(s)} = \frac{A(s)}{1 + A(s)\frac{1}{\frac{s}{p_1} + 1}} = \frac{A(s)\left(\frac{s}{p_1} + 1\right)}{\frac{s}{p_1} + 1 + A(s)}$$

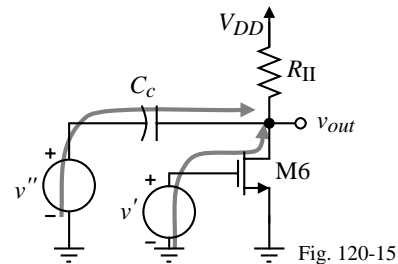2.) Zeros are also created by two paths from the input to the output and one of more of the paths is frequency dependent.



OTHER FORMS OF COMPENSATION

Feedforward Compensation

Use two parallel paths to achieve a LHP zero for lead compensation purposes.

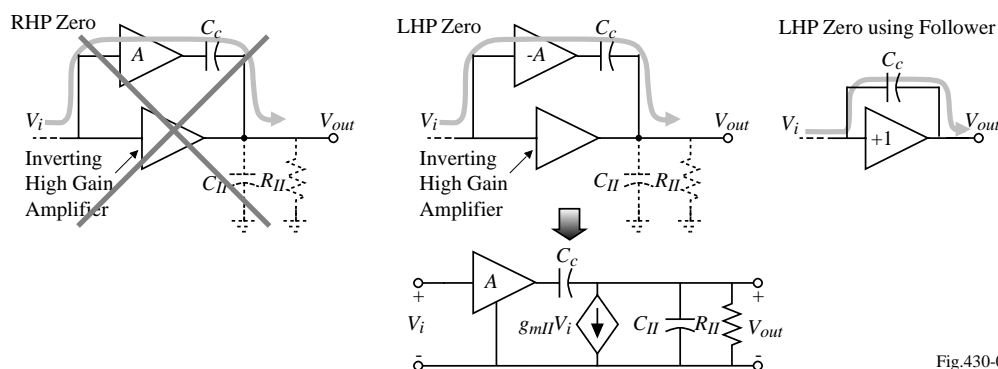


Fig.430-09

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{AC_c}{C_c + C_{II}} \left(\frac{s + g_{mII}/AC_c}{s + 1/[R_{II}(C_c + C_{II})]} \right)$$

To use the LHP zero for compensation, a compromise must be observed.

- Placing the zero below GB will lead to boosting of the loop gain that could deteriorate the phase margin.
- Placing the zero above GB will have less influence on the leading phase caused by the zero.

Note that a source follower is a good candidate for the use of feedforward compensation.

Self-Compensated Op Amps

Self compensation occurs when the load capacitor is the compensation capacitor (can never be unstable for resistive feedback)

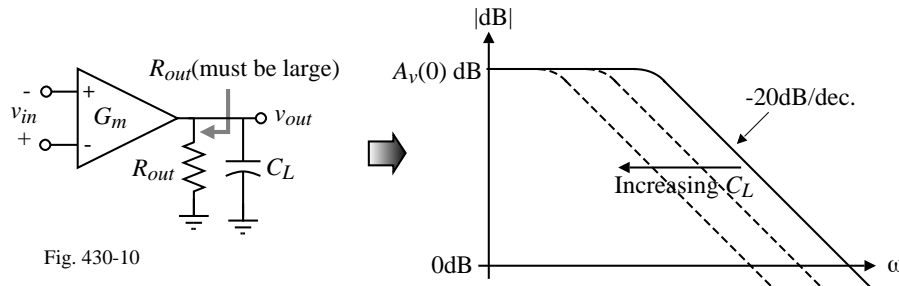


Fig. 430-10

Voltage gain:

$$\frac{v_{out}}{v_{in}} = A_v(0) = G_m R_{out}$$

Dominant pole:

$$p_1 = \frac{-1}{R_{out} C_L}$$

Unity-gainbandwidth:

$$GB = A_v(0) \cdot |p_1| = \frac{G_m}{C_L}$$

Stability:

Large load capacitors simply reduce GB but the phase is still 90° at GB .

CMOS OP AMP SLEW RATE

Slew Rate of a Two-Stage CMOS Op Amp

Remember that slew rate occurs when currents flowing in a capacitor become limited and is given as

$$I_{lim} = C \frac{dv_C}{dt} \text{ where } v_C \text{ is the voltage across the capacitor } C.$$

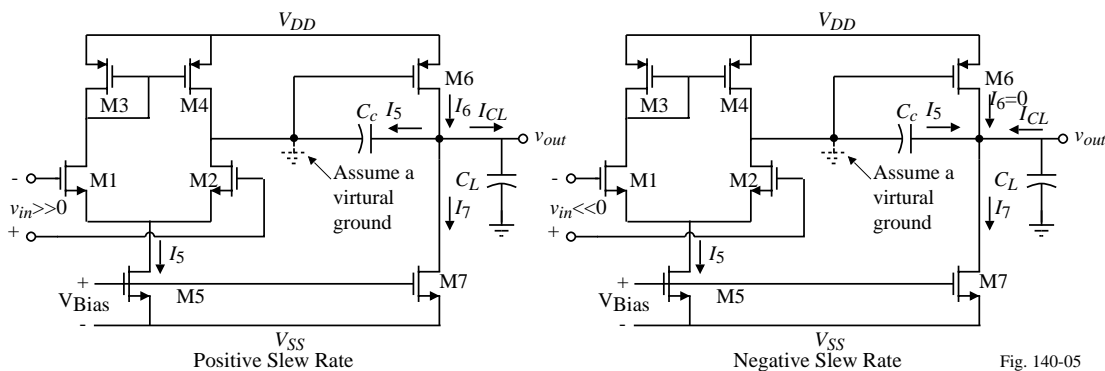


Fig. 140-05

$$SR^+ = \min \left[\frac{I_5}{C_c}, \frac{I_6 - I_5 - I_7}{C_L} \right] = \frac{I_5}{C_c} \text{ because } I_6 \gg I_5 \quad SR^- = \min \left[\frac{I_5}{C_c}, \frac{I_7 - I_5}{C_L} \right] = \frac{I_5}{C_c} \text{ if } I_7 \gg I_5.$$

Therefore, if C_L is not too large and if I_7 is significantly greater than I_5 , then the slew rate of the two-stage op amp should be, I_5/C_c .

SECTION 6.3 - TWO-STAGE OP AMP DESIGN

A DESIGN PROCEDURE FOR THE TWO-STAGE CMOS OP AMP

Unbuffered, Two-Stage CMOS Op Amp

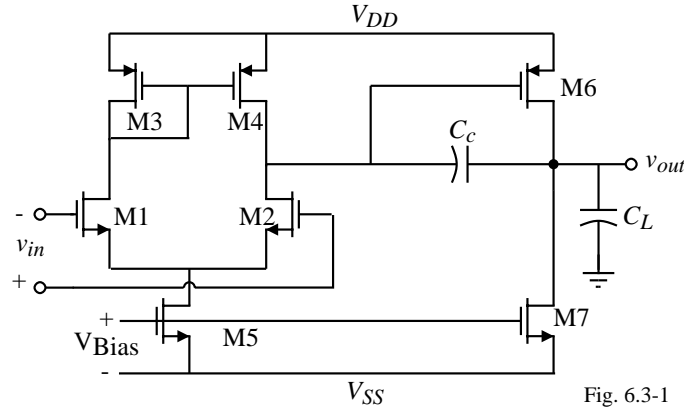


Fig. 6.3-1

Notation:

$$S_i = \frac{W_i}{L_i} = W/L \text{ of the } i\text{th transistor}$$

DC Balance Conditions for the Two-Stage Op Amp

For best performance, keep all transistors in saturation.

M4 is the only transistor that cannot be forced into saturation by internal connections or external voltages.

Therefore, we develop conditions to force M4 to be in saturation.

1.) First assume that $V_{SG4} = V_{SG6}$. This will cause “proper mirroring” in the M3-M4 mirror. Also, the gate and drain of M4 are at the same potential so that M4 is “guaranteed” to be in saturation.

2.) If $V_{SG4} = V_{SG6}$, then $I_6 = \left(\frac{S_6}{S_4}\right)I_4$

3.) However, $I_7 = \left(\frac{S_7}{S_5}\right)I_5 = \left(\frac{S_7}{S_5}\right)(2I_4)$

4.) For balance, I_6 must equal $I_7 \Rightarrow \boxed{\frac{S_6}{S_4} = \frac{2S_7}{S_5}}$ called the “balance conditions”

5.) So if the balance conditions are satisfied, then $V_{DG4} = 0$ and M4 is saturated.

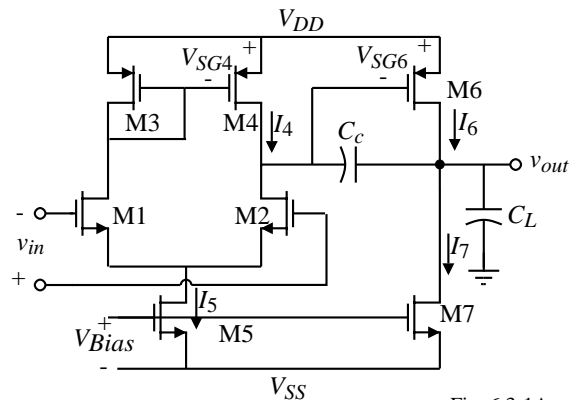


Fig. 6.3-1A

Design Relationships for the Two-Stage Op Amp

$$\text{Slew rate } SR = \frac{I_5}{C_c} \text{ (Assuming } I_7 \gg I_5 \text{ and } C_L > C_c)$$

$$\text{First-stage gain } A_{v1} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{2g_{m1}}{I_5(\lambda_2 + \lambda_4)}$$

$$\text{Second-stage gain } A_{v2} = \frac{g_{m6}}{g_{ds6} + g_{ds7}} = \frac{g_{m6}}{I_6(\lambda_6 + \lambda_7)}$$

$$\text{Gain-bandwidth } GB = \frac{g_{m1}}{C_c}$$

$$\text{Output pole } p_2 = \frac{-g_{m6}}{C_L}$$

$$\text{RHP zero } z_1 = \frac{g_{m6}}{C_c}$$

60° phase margin requires that $g_{m6} = 2.2g_{m2}(C_L/C_c)$ if all other roots are $\geq 10GB$.

$$\text{Positive ICMR } V_{in(max)} = V_{DD} - \sqrt{\frac{I_5}{\beta_3}} - |V_{T03}|_{(max)} + V_{T1(min)}$$

$$\text{Negative ICMR } V_{in(min)} = V_{SS} + \sqrt{\frac{I_5}{\beta_1}} + V_{T1(max)} + V_{DS5(sat)}$$

Op Amp Specifications

The following design procedure assumes that specifications for the following parameters are given.

1. Gain at dc, $A_v(0)$
2. Gain-bandwidth, GB
3. Phase margin (or settling time)
4. Input common-mode range, ICMR
5. Load Capacitance, C_L
6. Slew-rate, SR
7. Output voltage swing
8. Power dissipation, P_{diss}

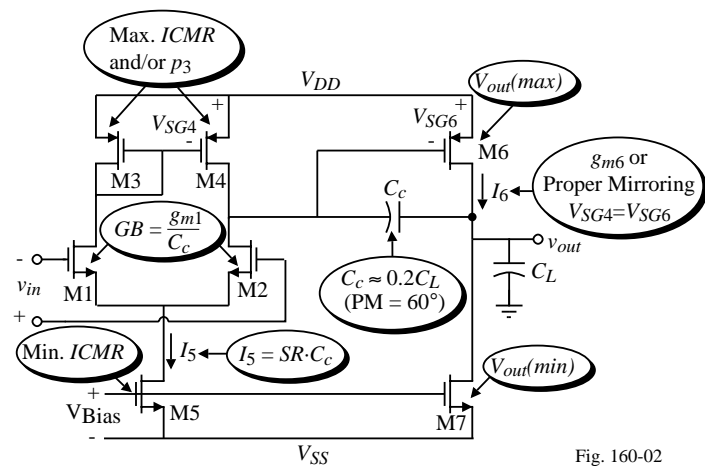


Fig. 160-02

Unbuffered Op Amp Design Procedure

This design procedure assumes that the gain at dc (A_v), unity gain bandwidth (GB), input common mode range ($V_{in}(\min)$ and $V_{in}(\max)$), load capacitance (C_L), slew rate (SR), settling time (T_s), output voltage swing ($V_{out}(\max)$ and $V_{out}(\min)$), and power dissipation (P_{diss}) are given. Choose the smallest device length which will keep the channel modulation parameter constant and give good matching for current mirrors.

1. From the desired phase margin, choose the minimum value for C_c , i.e. for a 60° phase margin we use the following relationship. This assumes that $z \geq 10GB$.

$$C_c > 0.22C_L$$

2. Determine the minimum value for the “tail current” (I_5) from the largest of the two values.

$$I_5 = SR \cdot C_c \quad \text{or} \quad I_5 \cong 10 \left(\frac{V_{DD} + |V_{SS}|}{2 \cdot T_s} \right)$$

3. Design for S_3 from the maximum input voltage specification.

$$S_3 = \frac{I_5}{K'_3[V_{DD} - V_{in}(\max) - |V_{T03}|(\max) + V_{T1}(\min)]^2}$$

4. Verify that the pole of M3 due to C_{gs3} and C_{gs4} ($= 0.67W_3L_3C_{ox}$) will not be dominant by assuming it to be greater than $10GB$

$$\frac{gm_3}{2C_{gs3}} > 10GB.$$

Unbuffered Op Amp Design Procedure - Continued

5. Design for S_1 (S_2) to achieve the desired GB .

$$gm_1 = GB \cdot C_c \rightarrow S_2 = \frac{gm_1^2}{K'_1 I_5}$$

6. Design for S_5 from the minimum input voltage. First calculate $V_{DS5}(\text{sat})$ then find S_5 .

$$V_{DS5}(\text{sat}) = V_{in}(\min) - V_{SS} - \sqrt{\frac{I_5}{\beta_1}} - V_{T1}(\max) \geq 100 \text{ mV} \rightarrow S_5 = \frac{2I_5}{K'_5[V_{DS5}(\text{sat})]^2}$$

7. Find S_6 by letting the second pole (p_2) be equal to 2.2 times GB and assuming that $V_{SG4} = V_{SG6}$.

$$gm_6 = 2.2gm_2(C_L/C_c) \quad \text{and} \quad \frac{gm_6}{gm_4} = \frac{\sqrt{2K_P'S_6I_6}}{\sqrt{2K_P'S_4I_4}} = \sqrt{\frac{S_6I_6}{S_4I_4}} = \frac{S_6}{S_4} \rightarrow S_6 = \frac{gm_6}{gm_4}S_4$$

8. Calculate I_6 from

$$I_6 = \frac{gm_6^2}{2K'_6S_6}$$

Check to make sure that S_6 satisfies the $V_{out}(\max)$ requirement and adjust as necessary.

9. Design S_7 to achieve the desired current ratios between I_5 and I_6 .

$$S_7 = (I_6/I_5)S_5 \quad (\text{Check the minimum output voltage requirements})$$

Unbuffered Op Amp Design Procedure - Continued

10. Check gain and power dissipation specifications.

$$A_v = \frac{2g_{m2}g_{m6}}{I_5(\lambda_2 + \lambda_4)I_6(\lambda_6 + \lambda_7)} \quad P_{diss} = (I_5 + I_6)(V_{DD} + |V_{SS}|)$$

11. If the gain specification is not met, then the currents, I_5 and I_6 , can be decreased or the W/L ratios of M2 and/or M6 increased. The previous calculations must be rechecked to insure that they are satisfied. If the power dissipation is too high, then one can only reduce the currents I_5 and I_6 . Reduction of currents will probably necessitate increase of some of the W/L ratios in order to satisfy input and output swings.

12. Simulate the circuit to check to see that all specifications are met.

DESIGN EXAMPLE

Example 6.3-1 - Design of a Two-Stage Op Amp

Using the material and device parameters given in Tables 3.1-1 and 3.1-2, design an amplifier similar to that shown in Fig. 6.3-1 that meets the following specifications. Assume the channel length is to be $1\mu\text{m}$ and the load capacitor is $C_L = 10\text{pF}$.

$A_v > 3000\text{V/V}$	$V_{DD} = 2.5\text{V}$	$V_{SS} = -2.5\text{V}$
$GB = 5\text{MHz}$	$SR > 10\text{V}/\mu\text{s}$	60° phase margin
V_{out} range = $\pm 2\text{V}$	$ICMR = -1$ to 2V	$P_{diss} \leq 2\text{mW}$

Solution

1.) The first step is to calculate the minimum value of the compensation capacitor C_c ,

$$C_c > (2.2/10)(10\text{ pF}) = 2.2\text{ pF}$$

2.) Choose C_c as 3pF . Using the slew-rate specification and C_c calculate I_5 .

$$I_5 = (3 \times 10^{-12})(10 \times 10^6) = 30\text{ }\mu\text{A}$$

3.) Next calculate $(W/L)_3$ using ICMR requirements.

$$(W/L)_3 = \frac{30 \times 10^{-6}}{(50 \times 10^{-6})[2.5 - 2 - .85 + 0.55]^2} = 15 \quad \rightarrow \quad \boxed{(W/L)_3 = (W/L)_4 = 15}$$

Example 6.3-1 - Continued

4.) Now we can check the value of the mirror pole, p_3 , to make sure that it is in fact greater than $10GB$. Assume the $C_{ox} = 0.4\text{fF}/\mu\text{m}^2$. The mirror pole can be found as

$$p_3 \approx \frac{-g_{m3}}{2C_{gs3}} = \frac{-\sqrt{2K'_p S_3 I_3}}{2(0.667)W_3 L_3 C_{ox}} = -2.81 \times 10^9 (\text{rads/sec})$$

or 448 MHz. Thus, p_3 , is not of concern in this design because $p_3 \gg 10GB$.

5.) The next step in the design is to calculate g_{m1} to get

$$g_{m1} = (5 \times 10^6)(2\pi)(3 \times 10^{-12}) = 94.25 \mu\text{S}$$

Therefore, $(W/L)_1$ is

$$(W/L)_1 = (W/L)_2 = \frac{g_{m1}^2}{2K'_N I_1} = \frac{(94.25)^2}{2 \cdot 110 \cdot 15} = 2.79 \approx 3.0 \Rightarrow \boxed{(W/L)_1 = (W/L)_2 = 3}$$

6.) Next calculate V_{DS5} ,

$$V_{DS5} = (-1) - (-2.5) - \sqrt{\frac{30 \times 10^{-6}}{110 \times 10^{-6} \cdot 3}} \cdot .85 = 0.35\text{V}$$

Using V_{DS5} calculate $(W/L)_5$ from the saturation relationship.

$$(W/L)_5 = \frac{2(30 \times 10^{-6})}{(110 \times 10^{-6})(0.35)^2} = 4.49 \approx 4.5 \rightarrow \boxed{(W/L)_5 = 4.5}$$

Example 6.3-1 - Continued

7.) For 60° phase margin, we know that

$$g_{m6} \geq 10g_{m1} \geq 942.5 \mu\text{S}$$

Assuming that $g_{m6} = 942.5 \mu\text{S}$ and knowing that $g_{m4} = 150 \mu\text{S}$, we calculate $(W/L)_6$ as

$$(W/L)_6 = 15 \frac{942.5 \times 10^{-6}}{(150 \times 10^{-6})} = 94.25 \approx 94$$

8.) Calculate I_6 using the small-signal g_m expression:

$$I_6 = \frac{(942.5 \times 10^{-6})^2}{(2)(50 \times 10^{-6})(94.25)} = 94.5 \mu\text{A} \approx 95 \mu\text{A}$$

If we calculate $(W/L)_6$ based on $V_{out}(\text{max})$, the value is approximately 15. Since 94 exceeds the specification and maintains better phase margin, we will stay with $(W/L)_6 = 94$ and $I_6 = 95 \mu\text{A}$.

With $I_6 = 95 \mu\text{A}$ the power dissipation is

$$P_{diss} = 5\text{V} \cdot (30 \mu\text{A} + 95 \mu\text{A}) = 0.625\text{mW}.$$

Example 6.3-1 - Continued

9.) Finally, calculate $(W/L)_7$

$$(W/L)_7 = 4.5 \left(\frac{95 \times 10^{-6}}{30 \times 10^{-6}} \right) = 14.25 \approx 14 \quad \rightarrow \quad \boxed{(W/L)_7 = 14}$$

Let us check the $V_{out}(\min)$ specification although the W/L of M7 is so large that this is probably not necessary. The value of $V_{out}(\min)$ is

$$V_{out}(\min) = V_{DS7}(\text{sat}) = \sqrt{\frac{2 \cdot 95}{110 \cdot 14}} = 0.351 \text{ V}$$

which is less than required. At this point, the first-cut design is complete.

10.) Now check to see that the gain specification has been met

$$A_v = \frac{(92.45 \times 10^{-6})(942.5 \times 10^{-6})}{15 \times 10^{-6}(.04 + .05)95 \times 10^{-6}(.04 + .05)} = 7,697 \text{ V/V}$$

which exceeds the specifications by a factor of two. An easy way to achieve more gain would be to increase the W and L values by a factor of two which because of the decreased value of λ would multiply the above gain by a factor of 20.

11.) The final step in the hand design is to establish true electrical widths and lengths based upon ΔL and ΔW variations. In this example ΔL will be due to lateral diffusion only. Unless otherwise noted, ΔW will not be taken into account. All dimensions will be rounded to integer values. Assume that $\Delta L = 0.2 \mu\text{m}$.

Example 6.3-1 – Continued

Therefore, we have,

$$W_1 = W_2 = 3(1 - 0.4) = 1.8 \mu\text{m} \approx 2 \mu\text{m}$$

$$W_3 = W_4 = 15(1 - 0.4) = 9 \mu\text{m}$$

$$W_5 = 4.5(1 - 0.4) = 2.7 \mu\text{m} \approx 3 \mu\text{m}$$

$$W_6 = 94(1 - 0.4) = 56.4 \mu\text{m} \approx 56 \mu\text{m}$$

$$W_7 = 14(1 - 0.4) = 8.4 \approx 8 \mu\text{m}$$

The figure below shows the results of the first-cut design. The W/L ratios shown do not account for the lateral diffusion discussed above. The next phase requires simulation.

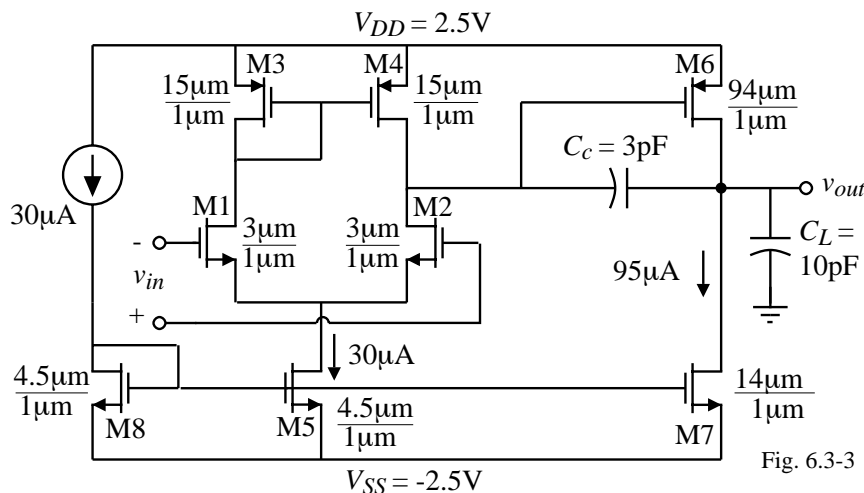


Fig. 6.3-3

ELIMINATING THE RHP ZERO

Incorporating the Nulling Resistor into the Miller Compensated Two-Stage Op Amp

Circuit:

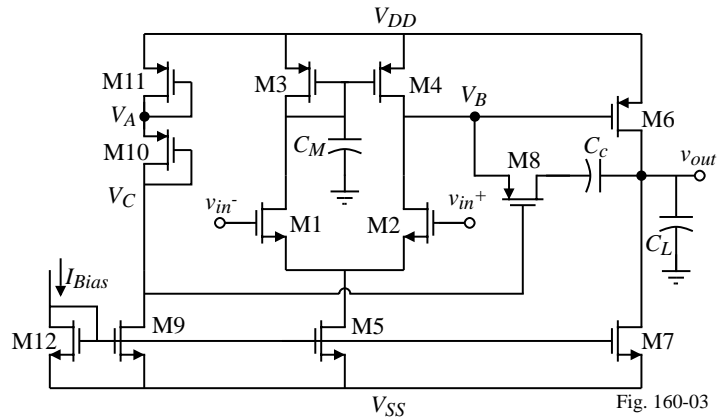


Fig. 160-03

We saw earlier that the roots were:

$$p_1 = -\frac{g_{m2}}{A_v C_c} = -\frac{g_{m1}}{A_v C_c} \quad p_2 = -\frac{g_{m6}}{C_L}$$

$$p_4 = -\frac{1}{R_z C_I} \quad z_1 = \frac{-1}{R_z C_c - C_c / g_{m6}}$$

where $A_v = g_{m1} g_{m6} R_I R_{II}$.

(Note that p_4 is the pole resulting from the nulling resistor compensation technique.)

Design of the Nulling Resistor (M8)

For the zero to be on top of the second pole (p_2), the following relationship must hold

$$R_z = \frac{1}{g_{m6}} \left(\frac{C_L + C_c}{C_c} \right) = \left(\frac{C_c + C_L}{C_c} \right) \frac{1}{\sqrt{2K'_p S_6 I_6}}$$

The resistor, R_z , is realized by the transistor M8 which is operating in the active region because the dc current through it is zero. Therefore, R_z can be written as

$$R_z = \frac{\partial v_{DS8}}{\partial i_{D8}} \bigg|_{V_{DS8}=0} = \frac{1}{K'_p S_8 (V_{SG8} - |V_{TP}|)}$$

The bias circuit is designed so that voltage V_A is equal to V_B .

$$\therefore |V_{GS10}| - |V_T| = |V_{GS8}| - |V_T| \Rightarrow V_{SG11} = V_{SG6} \Rightarrow \left(\frac{W_{11}}{L_{11}} \right) = \left(\frac{I_{10}}{I_6} \right) \left(\frac{W_6}{L_6} \right)$$

In the saturation region

$$|V_{GS10}| - |V_T| = \sqrt{\frac{2(I_{10})}{K'_p (W_{10}/L_{10})}} = |V_{GS8}| - |V_T|$$

$$\therefore R_z = \frac{1}{K'_p S_8} \sqrt{\frac{K'_p S_{10}}{2I_{10}}} = \frac{1}{S_8} \sqrt{\frac{S_{10}}{2K'_p I_{10}}}$$

$$\text{Equating the two expressions for } R_z \text{ gives } \left(\frac{W_8}{L_8} \right) = \left(\frac{C_c}{C_L + C_c} \right) \sqrt{\frac{S_{10} S_6 I_6}{I_{10}}}$$

Example 6.3-2 - RHP Zero Compensation

Use results of Ex. 6.3-1 and design compensation circuitry so that the RHP zero is moved from the RHP to the LHP and placed on top of the output pole p_2 . Use device data given in Ex. 6.3-1.

Solution

The task at hand is the design of transistors M8, M9, M10, M11, and bias current I_{10} . The first step in this design is to establish the bias components. In order to set V_A equal to V_B , then V_{SG11} must equal V_{SG6} . Therefore,

$$S_{11} = (I_{11}/I_6)S_6$$

Choose $I_{11} = I_{10} = I_9 = 15\mu\text{A}$ which gives $S_{11} = (15\mu\text{A}/95\mu\text{A})94 = 14.8 \approx 15$.

The aspect ratio of M10 is essentially a free parameter, and will be set equal to 1. There must be sufficient supply voltage to support the sum of V_{SG11} , V_{SG10} , and V_{DS9} . The ratio of I_{10}/I_5 determines the (W/L) of M9. This ratio is

$$(W/L)_9 = (I_{10}/I_5)(W/L)_5 = (15/30)(4.5) = 2.25 \approx 2$$

Now $(W/L)_8$ is determined to be

$$(W/L)_8 = \left(\frac{3\text{pF}}{3\text{pF} + 10\text{pF}} \right) \sqrt{\frac{1.94 \cdot 95\mu\text{A}}{15\mu\text{A}}} = 5.63 \approx 6$$

Example 6.3-2 - Continued

It is worthwhile to check that the RHP zero has been moved on top of p_2 . To do this, first calculate the value of R_z . V_{SG8} must first be determined. It is equal to V_{SG10} , which is

$$V_{SG10} = \sqrt{\frac{2I_{10}}{K'_p S_{10}}} + |V_{TP}| = \sqrt{\frac{2 \cdot 15}{50 \cdot 1}} + 0.7 = 1.474\text{V}$$

Next determine R_z .

$$R_z = \frac{1}{K'_p S_8 (V_{SG10} - |V_{TP}|)} = \frac{10^6}{50 \cdot 5.63 (1.474 - 0.7)} = 4.590\text{k}\Omega$$

The location of z_1 is calculated as

$$z_1 = \frac{-1}{(4.590 \times 10^3)(3 \times 10^{-12}) - \frac{3 \times 10^{-12}}{942.5 \times 10^{-6}}} = -94.46 \times 10^6 \text{ rads/sec}$$

The output pole, p_2 , is

$$p_2 = -\frac{942.5 \times 10^{-6}}{10 \times 10^{-12}} = -94.25 \times 10^6 \text{ rads/sec}$$

Thus, we see that for all practical purposes, the output pole is canceled by the zero that has been moved from the RHP to the LHP.

The results of this design are summarized below.

$$W_8 = 6 \mu\text{m} \quad W_9 = 2 \mu\text{m} \quad W_{10} = 1 \mu\text{m} \quad W_{11} = 15 \mu\text{m}$$

An Alternate Form of Nulling Resistor

To cancel p_2 ,

$$z_1 = p_2 \rightarrow R_z = \frac{C_c + C_L}{g_{m6A} C_c} = \frac{1}{g_{m6B}}$$

Which gives

$$g_{m6B} = g_{m6A} \left(\frac{C_c}{C_c + C_L} \right)$$

In the previous example,

$$g_{m6A} = 942.5 \mu S, C_c = 3 \text{ pF}$$

and $C_L = 10 \text{ pF}$.

Choose $I_{6B} = 10 \mu A$ to get

$$g_{m6B} = \frac{g_{m6A} C_c}{C_c + C_L} \rightarrow \sqrt{\frac{2K_P W_{6B} I_{6B}}{L_{6B}}} = \left(\frac{C_c}{C_c + C_L} \right) \sqrt{\frac{2K_P W_{6A} I_{D6}}{L_{6A}}}$$

or

$$\frac{W_{6B}}{L_{6B}} = \left(\frac{3}{13} \right)^2 \frac{I_{6A}}{I_{6B}} \frac{W_{6A}}{L_{6A}} = \left(\frac{3}{13} \right)^2 \left(\frac{95}{10} \right) (94) = 47.6 \rightarrow W_{6B} = 48 \mu m$$

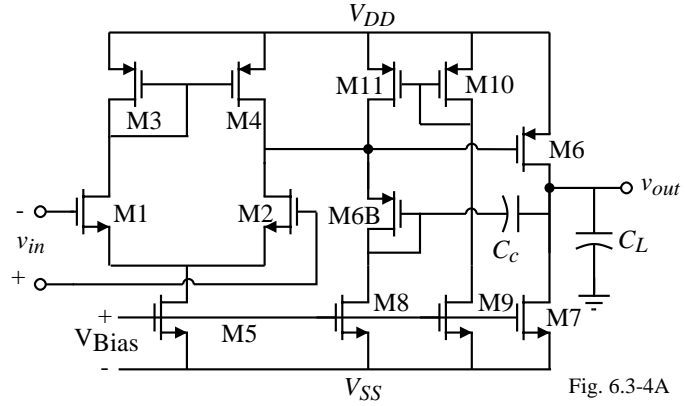


Fig. 6.3-4A

Programmability of the Two-Stage Op Amp

The following relationships depend on the bias current, I_{bias} , in the following manner and allow for programmability after fabrication.

$$A_v(0) = g_{mI} g_{mII} R_I R_{II} \propto \frac{1}{I_{Bias}}$$

$$GB = \frac{g_{mI}}{C_c} \propto \sqrt{I_{Bias}}$$

$$P_{diss} = (V_{DD} + |V_{SS}|)(1 + K_1 + K_2)I_{Bias} \propto I_{bias}$$

$$SR = \frac{K_1 I_{Bias}}{C_c} \propto I_{Bias}$$

$$R_{out} = \frac{1}{2\lambda K_2 I_{Bias}} \propto \frac{1}{I_{Bias}}$$

$$|p_1| = \frac{1}{g_{mII} R_I R_{II} C_c} \propto \frac{I_{Bias}^2}{\sqrt{I_{Bias}}} \propto I_{Bias}^{1.5}$$

$$|z| = \frac{g_{mII}}{C_c} \propto \sqrt{I_{Bias}}$$

Illustration of the I_{bias} dependence \rightarrow

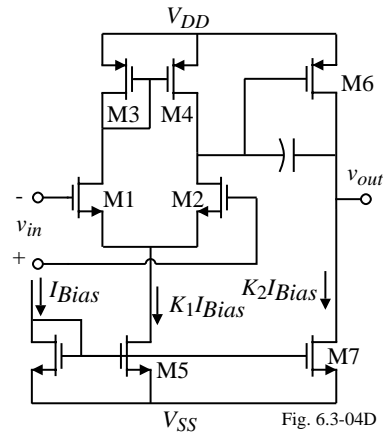


Fig. 6.3-04D

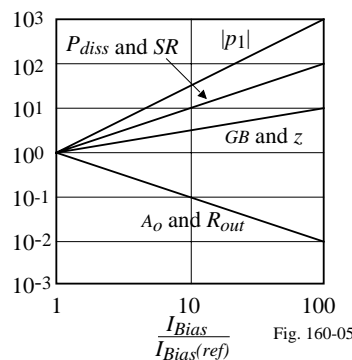


Fig. 160-05

Simulation of the Electrical Design

Area of source or drain = $AS = AD = W[L1 + L2 + L3]$

where

$L1$ = Minimum allowable distance between the contact in the S/D and the polysilicon ($5\mu\text{m}$)

$L2$ = Width of a minimum size contact ($5\mu\text{m}$)

$L3$ = Minimum allowable distance from contact in S/D to edge of S/D ($5\mu\text{m}$)

$$\therefore AS = AD = W \times 15\mu\text{m}$$

Perimeter of the source or drain = $PD = PS = 2W + 2(L1+L2+L3)$

$$\therefore PD = PS = 2W + 30\mu\text{m}$$

Illustration:

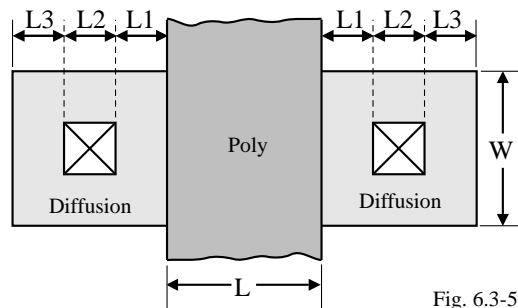


Fig. 6.3-5



POWER SUPPLY REJECTION RATIO OF THE TWO-STAGE OP AMP

What is PSRR?

$$PSRR = \frac{A_v(V_{dd}=0)}{A_{dd}(V_{in}=0)}$$

How do you calculate PSRR?

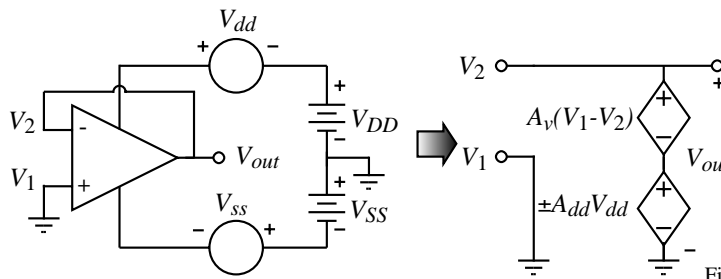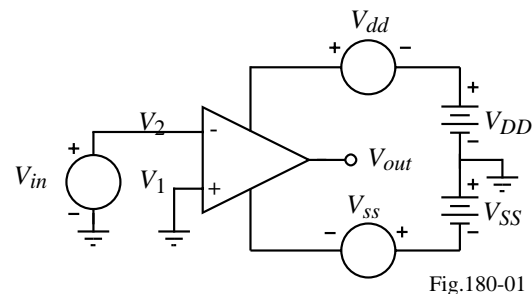You could calculate A_v and A_{dd} and divide, however



$$V_{out} = A_{dd}V_{dd} + A_v(V_1 - V_2) = A_{dd}V_{dd} - A_vV_{out} \rightarrow V_{out}(1 + A_v) = A_{dd}V_{dd}$$

$$\therefore \frac{V_{out}}{V_{dd}} = \frac{A_{dd}}{1 + A_v} \approx \frac{A_{dd}}{A_v} = \frac{1}{PSRR+} \quad (\text{Good for frequencies up to } GB)$$

Approximate Model for $PSRR^+$

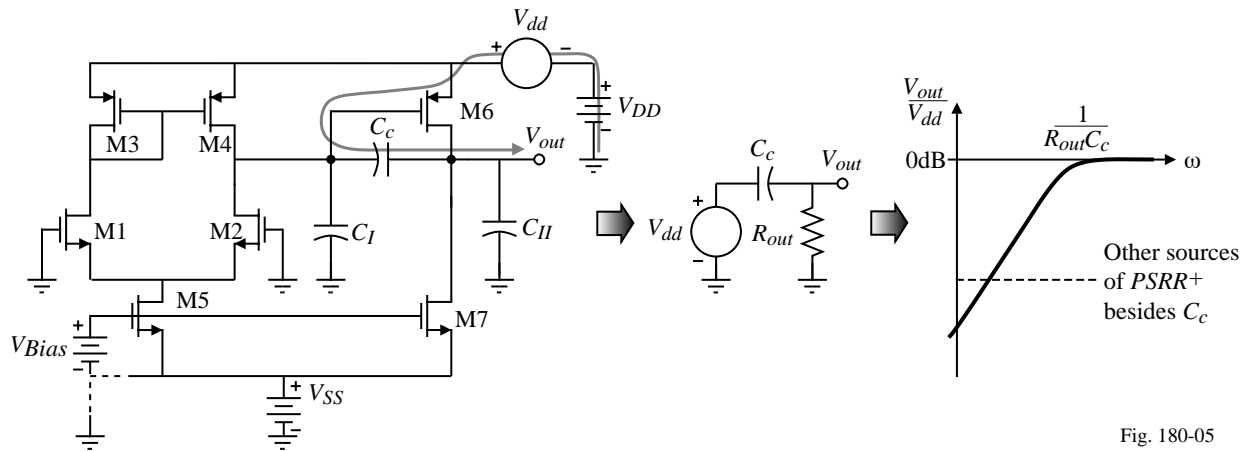


Fig. 180-05

- 1.) The M7 current sink causes V_{SG6} to act like a battery.
- 2.) Therefore, V_{dd} couples from the source to gate of M6.
- 3.) The path to the output is through any capacitance from gate to drain of M6.

Conclusion:

The Miller capacitor C_c couples the positive power supply ripple directly to the output.
Must reduce or eliminate C_c .

Approximate Model for $PSRR^-$

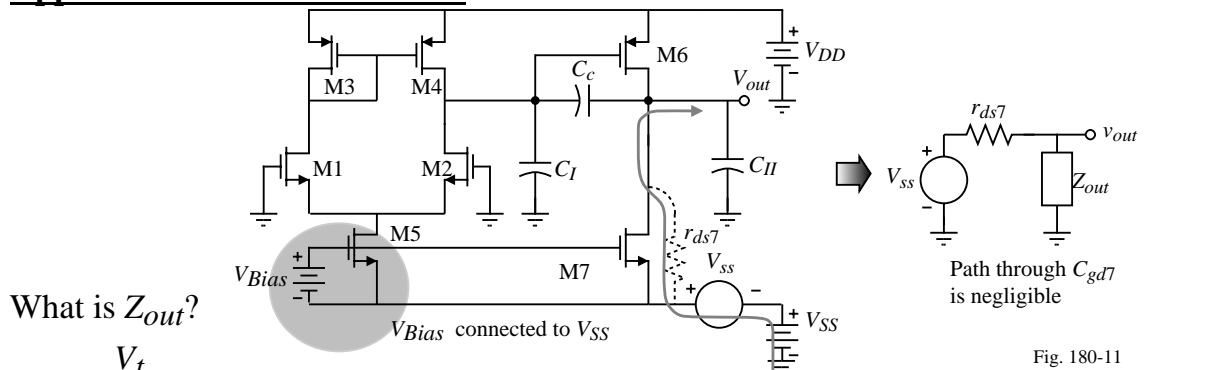


Fig. 180-11

$$I_t = g_{mII}V_1 = g_{mII} \left(\frac{g_{mI}V_t}{G_I + sC_I + sC_c} \right)$$

$$\text{Thus, } Z_{out} = \frac{G_I + s(C_I + C_c)}{g_{mI}g_{mII}}$$

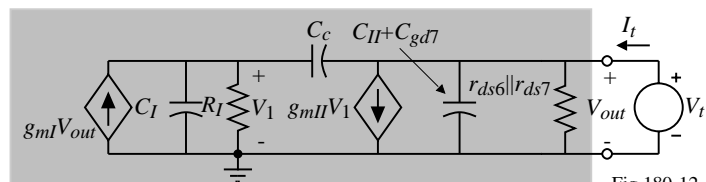


Fig.180-12

$$\therefore \frac{V_{out}}{V_{ss}} = \frac{1 + \frac{r_{ds7}}{Z_{out}}}{1} = \frac{s(C_c + C_I) + G_I + g_{mI}g_{mII}r_{ds7}}{s(C_c + C_I) + G_I} \Rightarrow \text{Pole at } \frac{-G_I}{C_c + C_I}$$

The negative $PSRR$ is much better than the positive $PSRR$.

SECTION 6.4 – CASCODE OP AMPS

INTRODUCTION

Why Cascode Op Amps?


- Control of the frequency behavior
- Can get more gain by increasing the output resistance of a stage
- In the past section, $PSRR$ of the two-stage op amp was insufficient for many applications
- A two-stage op amp can become unstable for large load capacitors (if nulling resistor is not used)
- The cascode op amp leads to wider $ICMR$ and/or smaller power supply requirements

Where Should the Cascode Technique be Used?

- First stage -
 - Good noise performance
 - Requires level translation to second stage
 - Degrades the Miller compensation
- Second stage -
 - Self compensating
 - Increases the efficiency of the Miller compensation
 - Increases $PSRR$

SINGLE STAGE CASCODE OP AMPS

Simple Single Stage Cascode Op Amp

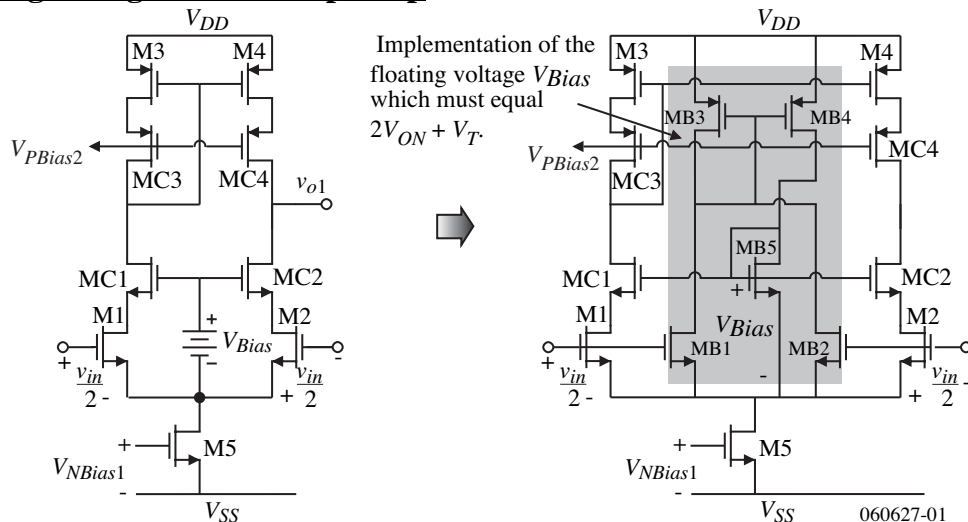

R_{out} of the first stage is $R_I \approx (g_{mC2}r_{dsC2}r_{ds2}) \parallel (g_{mC4}r_{dsC4}r_{ds4})$

Voltage gain $= \frac{v_{o1}}{v_{in}} = g_{m1}R_I$ [The gain is increased by approximately $0.5(g_{mC}r_{dsC})$]

As a single stage op amp, the compensation capacitor becomes the load capacitor.

Example 6.5-1 Single-Stage, Cascode Op Amp Performance

Assume that all W/L ratios are $10 \mu\text{m}/1 \mu\text{m}$, and that $I_{DS1} = I_{DS2} = 50 \mu\text{A}$ of single stage op amp. Find the voltage gain of this op amp and the value of C_I if $GB = 10 \text{ MHz}$. Use the model parameters of Table 3.1-2.

Solution

The device transconductances are

$$g_{m1} = g_{m2} = g_{mI} = 331.7 \mu\text{S}$$

$$g_{mC2} = 331.7 \mu\text{S}$$

$$g_{mC4} = 223.6 \mu\text{S}.$$

The output resistance of the NMOS and PMOS devices is $0.5 \text{ M}\Omega$ and $0.4 \text{ M}\Omega$, respectively.

$$\therefore R_I = 25 \text{ M}\Omega$$


$$A_v(0) = 8290 \text{ V/V}.$$

For a unity-gain bandwidth of 10 MHz , the value of C_I is 5.28 pF .

What happens if a 100pF capacitor is attached to this op amp?

GB goes from 10MHz to 0.53MHz .

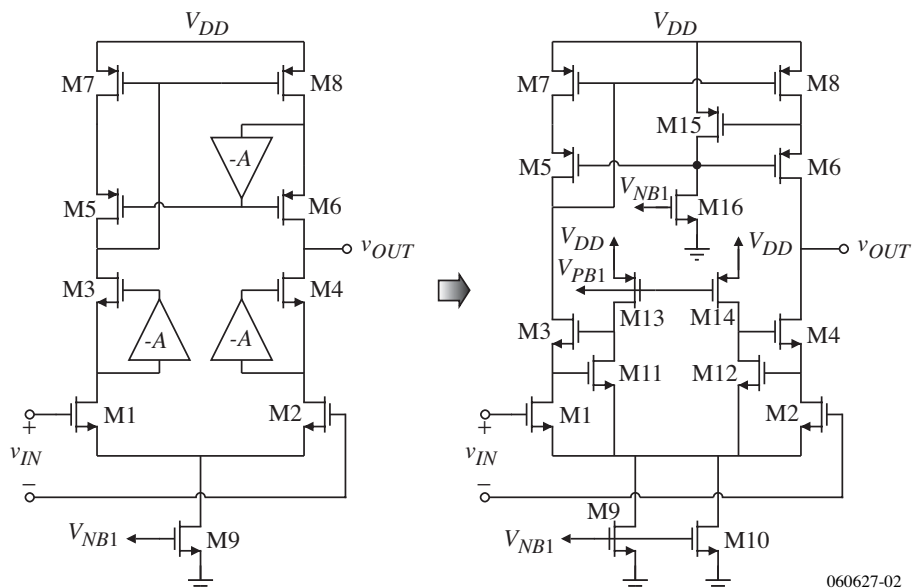Enhanced Gain, Single Stage, Cascode Op Amp




From inspection, we can write the voltage gain as,

$$A_v = \frac{v_{OUT}}{v_{IN}} = g_{m1} R_{out} \quad \text{where} \quad R_{out} = (A r_{ds6} g_{m6} r_{ds8}) \parallel (A r_{ds2} g_{m4} r_{ds4})$$


Since $A \approx g_m r_{ds}$ the voltage gain would be equal to $100,000$ to $500,000$.

TWO-STAGE, CASCODE OP AMPS

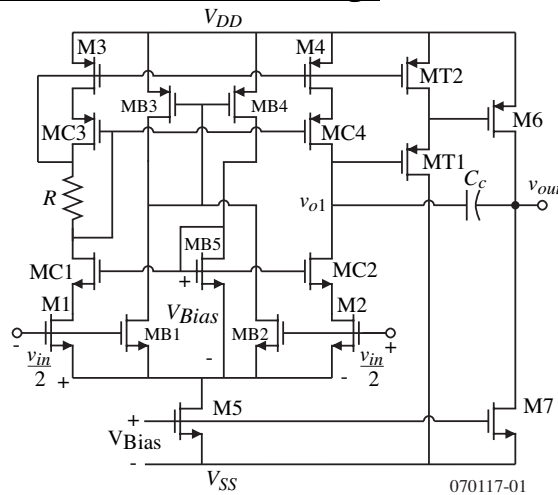Two-Stage Op Amp with a Cascoded First-Stage



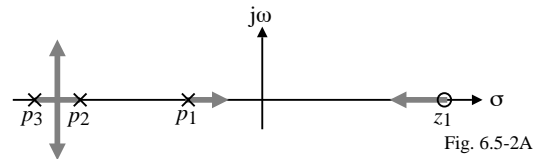- MT1 and MT2 are required for level shifting from the first-stage to the second.
- The $PSRR^+$ is improved by the presence of MT1
- Internal loop pole at the gate of M6 may cause the Miller compensation to fail.
- The voltage gain of this op amp could easily be 100,000V/V



Two-Stage Op Amp with a Cascode Second-Stage

$$A_v = g_{mI} g_{mII} R_I R_{II}$$

where $g_{mI} = g_{m1} = g_{m2}$, $g_{mII} = g_{m6}$,

$$R_I = \frac{1}{g_{ds2} + g_{ds4}} = \frac{2}{(\lambda_2 + \lambda_4) I_{D5}}$$

and

$$R_{II} = (g_{mC6} r_{dsC6} r_{ds6}) \parallel (g_{mC7} r_{dsC7} r_{ds7})$$


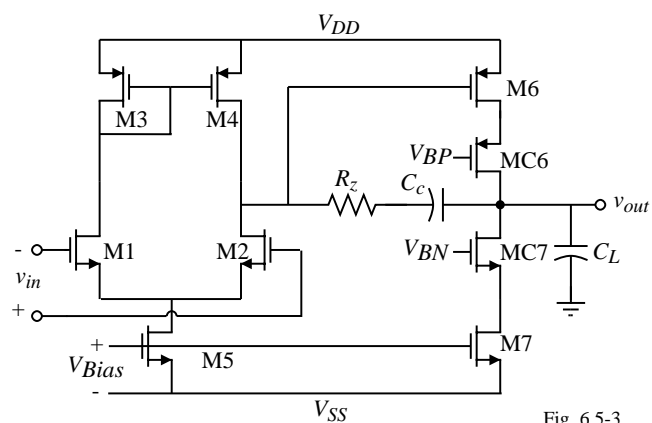


Fig. 6.5-3

Comments:

- The second-stage gain has greatly increased improving the Miller compensation
- The overall gain is approximately $(g_m r_{ds})^3$ or very large
- Output pole, p_2 , is approximately the same if C_c is constant
- The zero RHP is the same if C_c is constant
- PSRR is poor unless the Miller compensation is removed (then the op amp becomes self compensated)

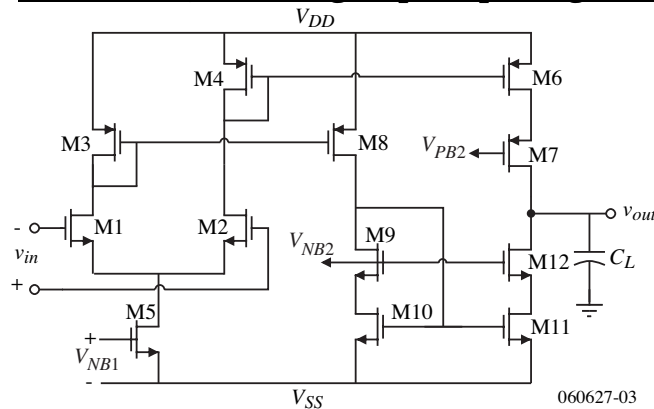A Balanced, Two-Stage Op Amp using a Cascode Output Stage



$$v_{out} = \left(\frac{g_{m1}g_{m8}}{g_{m3}} \frac{v_{in}}{2} + \frac{g_{m2}g_{m6}}{g_{m4}} \frac{v_{in}}{2} \right) R_{II}$$

$$= \left(\frac{g_{m1}}{2} + \frac{g_{m2}}{2} \right) k v_{in} R_{II} = g_{m1} \cdot k \cdot R_{II} v_{in}$$

where

$$R_{II} = (g_{m7}r_{ds7}r_{ds6}) \parallel (g_{m12}r_{ds12}r_{ds11})$$

and

$$k = \frac{g_{m8}}{g_{m3}} = \frac{g_{m6}}{g_{m4}}$$

This op amp is balanced because the drain-to-ground loads for M1 and M2 are identical.

TABLE 1 - Design Relationships for Balanced, Cascode Output Stage Op Amp.

$$\text{Slew rate} = \frac{I_{out}}{C_L} \quad GB = \frac{g_{m1}g_{m8}}{g_{m3}C_L} \quad A_v = \frac{1}{2} \left(\frac{g_{m1}g_{m8}}{g_{m3}} + \frac{g_{m2}g_{m6}}{g_{m4}} \right) R_{II}$$

$$V_{in}(\text{max}) = V_{DD} - \left[\frac{I_5}{\beta_3} \right]^{1/2} - |V_{TO3}|(\text{max}) + V_{T1}(\text{min}) \quad V_{in}(\text{min}) = V_{SS} + V_{DS5} + \left[\frac{I_5}{\beta_1} \right]^{1/2} + V_{T1}(\text{min})$$

Example 6.5-2 Design of Balanced, Cascoded Output Stage Op Amp

The balanced, cascoded output stage op amp is a useful alternative to the two-stage op amp. Its design will be illustrated by this example. The pertinent design equations for the op amp were given above. The specifications of the design are as follows:

$$V_{DD} = -V_{SS} = 2.5 \text{ V} \quad \text{Slew rate} = 5 \text{ V}/\mu\text{s} \text{ with a } 50 \text{ pF load}$$

$$GB = 10 \text{ MHz with a } 25 \text{ pF load} \quad A_v \geq 5000$$

$$\text{Input CMR} = -1 \text{ V to } +1.5 \text{ V} \quad \text{Output swing} = \pm 1.5 \text{ V}$$

Use the parameters of Table 3.1-2 and let all device lengths be $1 \mu\text{m}$.

Solution

While numerous approaches can be taken, we shall follow one based on the above specifications. The steps will be numbered to help illustrate the procedure.

1.) The first step will be to find the maximum source/sink current. This is found from the slew rate.

$$I_{source}/I_{sink} = C_L \times \text{slew rate} = 50 \text{ pF}(5 \text{ V}/\mu\text{s}) = 250 \mu\text{A}$$

2.) Next some W/L constraints based on the maximum output source/sink current are developed. Under dynamic conditions, all of I_5 will flow in M4; thus we can write

$$\text{Max. } I_{out}(\text{source}) = (S_6/S_4)I_5 \quad \text{and} \quad \text{Max. } I_{out}(\text{sink}) = (S_8/S_3)I_5$$

The maximum output sinking current is equal to the maximum output sourcing current if

$$S_3 = S_4, \quad S_6 = S_8, \quad \text{and} \quad S_{10} = S_{11}$$

Example 6.5-2 - Continued

3.) Choose I_5 as $100 \mu\text{A}$. This current (which can be changed later) gives

$$S_6 = 2.5S_4 \text{ and } S_8 = 2.5S_3$$

Note that S_8 could equal S_3 if $S_{11} = 2.5S_{10}$. This would minimize the power dissipation.

4.) Next design for $\pm 1.5 \text{ V}$ output capability. We shall assume that the output must source or sink the $250 \mu\text{A}$ at the peak values of output. First consider the negative output peak. Since there is 1 V difference between V_{SS} and the minimum output, let $V_{DS11}(\text{sat}) = V_{DS12}(\text{sat}) = 0.5 \text{ V}$ (we continue to ignore the bulk effects). Under the maximum negative peak assume that $I_{11} = I_{12} = 250 \mu\text{A}$. Therefore

$$0.5 = \sqrt{\frac{2I_{11}}{K'_N S_{11}}} = \sqrt{\frac{2I_{12}}{K'_N S_{12}}} = \sqrt{\frac{500 \mu\text{A}}{(110 \mu\text{A/V}^2)S_{11}}}$$

which gives $S_{11} = S_{12} = 18.2$ and $S_9 = S_{10} = 18.2$. For the positive peak, we get

$$0.5 = \sqrt{\frac{2I_6}{K'_P S_6}} = \sqrt{\frac{2I_7}{K'_P S_7}} = \sqrt{\frac{500 \mu\text{A}}{(50 \mu\text{A/V}^2)S_6}}$$

which gives $S_6 = S_7 = S_8 = 40$ and $S_3 = S_4 = (40/2.5) = 16$.

Example 6.5-2 - Continued

5.) Now we must consider the possibility of conflict among the specifications.

First consider the input CMR. S_3 has already been designed as 16. Using ICMR relationship, we find that S_3 should be at least 4.1. A larger value of S_3 will give a higher value of $V_{in}(\text{max})$ so that we continue to use $S_3 = 16$ which gives $V_{in}(\text{max}) = 1.95 \text{ V}$.

Next, check to see if the larger W/L causes a pole below the gainbandwidth. Assuming a C_{ox} of $0.4 \text{ fF}/\mu\text{m}^2$ gives the first-stage pole of

$$p_3 = \frac{-g_{m3}}{C_{gs3} + C_{gs8}} = \frac{-\sqrt{2K'_P S_3 I_3}}{(0.667)(W_3 L_3 + W_8 L_8)C_{ox}} = 33.15 \times 10^9 \text{ rads/sec or } 5.275 \text{ GHz}$$

which is much greater than 10 GB .

6.) Next we find g_{m1} (g_{m2}). There are two ways of calculating g_{m1} .

(a.) The first is from the A_v specification. The gain is

$$A_v = (g_{m1}/2g_{m4})(g_{m6} + g_{m8}) R_{II}$$

Note, a current gain of k could be introduced by making S_6/S_4 ($S_8/S_3 = S_{11}/S_3$) equal to k .

$$\frac{g_{m6}}{g_{m4}} = \frac{g_{m11}}{g_{m3}} = \sqrt{\frac{2K'_P \cdot S_6 \cdot I_6}{2K'_P \cdot S_4 \cdot I_4}} = k$$

Calculating the various transconductances we get $g_{m4} = 282.4 \mu\text{S}$, $g_{m6} = g_{m7} = g_{m8} = 707 \mu\text{S}$, $g_{m11} = g_{m12} = 707 \mu\text{S}$, $r_{ds6} = r_{d7} = 0.16 \text{ M}\Omega$, and $r_{ds11} = r_{ds12} = 0.2 \text{ M}\Omega$.

Assuming that the gain A_v must be greater than 5000 and $k = 2.5$ gives $g_{m1} > 72.43 \mu\text{S}$.

Example 6.5-2 - Continued

(b.) The second method of finding g_{m1} is from the GB specifications. Multiplying the gain by the dominant pole ($1/C_{II}R_{II}$) gives

$$GB = \frac{g_{m1}(g_{m6} + g_{m8})}{2g_{m4}C_L}$$

Assuming that $C_L = 25$ pF and using the specified GB gives $g_{m1} = 251 \mu S$.

Since this is greater than $72.43 \mu S$, we choose $g_{m1} = g_{m2} = 251 \mu S$. Knowing I_5 gives $S_1 = S_2 = 5.7 \approx 6$.

8.) The next step is to check that S_1 and S_2 are large enough to meet the $-1V$ input CMR specification. Use the saturation formula we find that V_{DS5} is 0.261 V. This gives $S_5 = 26.7 \approx 27$. The gain becomes $A_v = 6,925V/V$ and $GB = 10$ MHz for a 25 pF load. We shall assume that exceeding the specifications in this area is not detrimental to the performance of the op amp.

9.) Knowing the currents and W/L values, the bias voltages V_{NB1} , V_{NB2} and V_{PB2} can be designed.

The W/L values resulting from this design procedure are shown below. The power dissipation for this design is seen to be 2 mW. The next step would be simulation.

$$\begin{array}{lll} S_1 = S_2 = 6 & S_3 = S_4 = 16 & S_5 = 27 \\ S_6 = S_7 = S_8 = 40 & S_9 = S_{10} = S_{11} = S_{12} = 18.2 & \end{array}$$

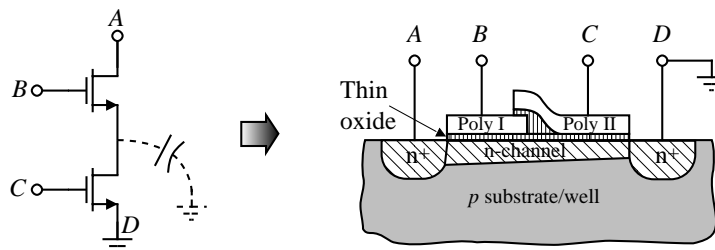
Technological Implications of the Cascode Configuration

Fig. 6.5-5

If a double poly CMOS process is available, internode parasitics can be minimized. As an alternative, one should keep the drain/source between the transistors to a minimum area.

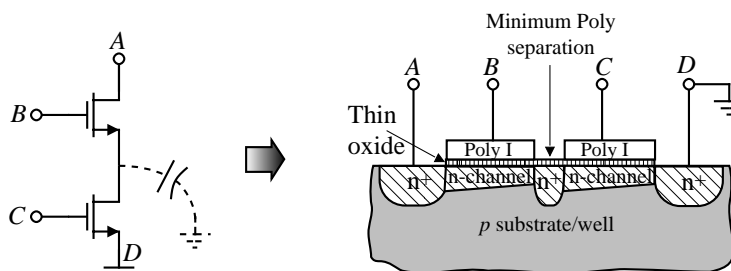


Fig. 6.5-5A

Input Common Mode Range for Two Types of Differential Amplifier Loads


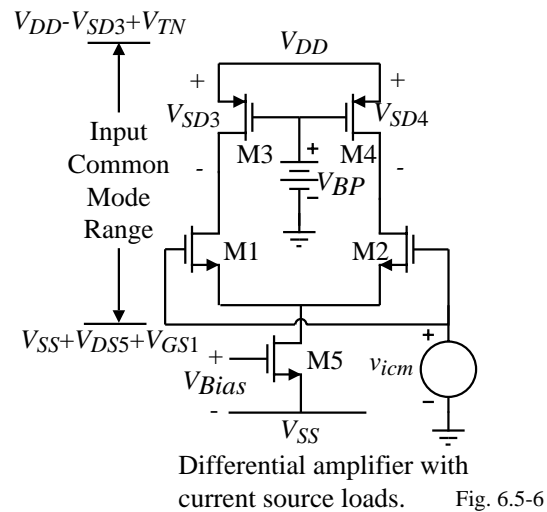
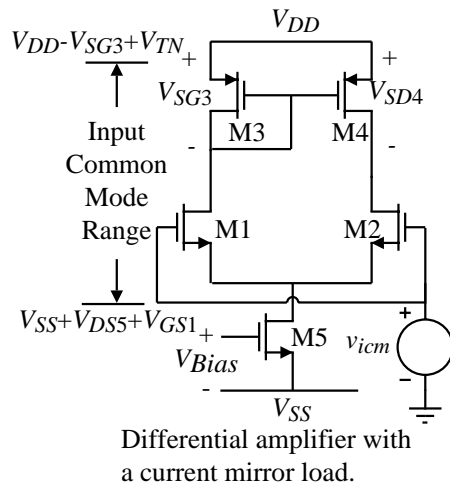


Fig. 6.5-6

In order to improve the ICMR, it is desirable to use current source (sink) loads without losing half the gain.

The resulting solution is the *folded cascode* op amp.

The Folded Cascode Op Amp

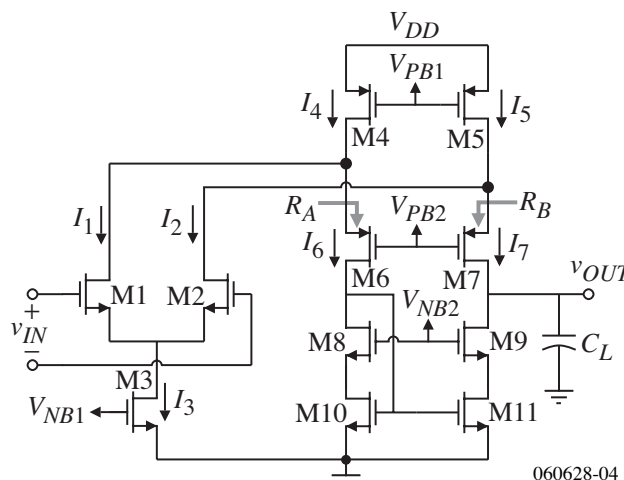

060628-04


Comments:

- I_4 and I_5 , should be designed so that I_6 and I_7 never become zero (i.e. $I_4 = I_5 = 1.5I_3$)
- This amplifier is nearly balanced (would be exactly if R_A was equal to R_B)
- Self compensating
- Poor noise performance, the gain occurs at the output so all intermediate transistors contribute to the noise along with the input transistors. (Some first stage gain can be achieved if R_A and R_B are greater than g_{m1} or g_{m2} .)

Small-Signal Analysis of the Folded Cascode Op Amp

Model:

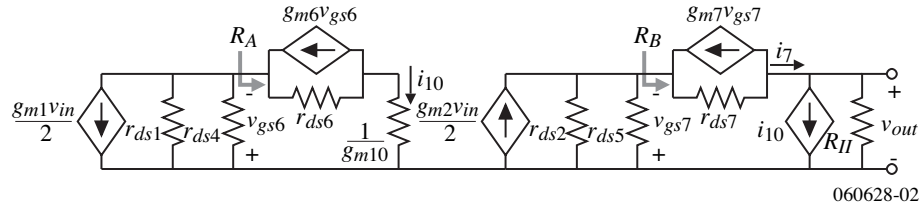Recalling what we learned about the resistance looking into the source of the cascode transistor;



$$R_A = \frac{r_{ds6} + (1/g_{m10})}{1 + g_{m6}r_{ds6}} \approx \frac{1}{g_{m6}} \quad \text{and} \quad R_B = \frac{r_{ds7} + R_{II}}{1 + g_{m7}r_{ds7}} \approx \frac{R_{II}}{g_{m7}r_{ds7}} \quad \text{where} \quad R_{II} \approx g_{m9}r_{ds9}r_{ds11}$$

The small-signal voltage transfer function can be found as follows. The current i_{10} is written as

$$i_{10} = \frac{-g_{m1}(r_{ds1} || r_{ds4})v_{in}}{2[R_A + (r_{ds1} || r_{ds4})]} \approx \frac{-g_{m1}v_{in}}{2}$$

and the current i_7 can be expressed as

$$i_7 = \frac{\frac{g_{m2}(r_{ds2} || r_{ds5})v_{in}}{2} \cdot \frac{R_{II}}{g_{m7}r_{ds7} + (r_{ds2} || r_{ds5})}}{2 \left[1 + \frac{R_{II}(g_{ds2} + g_{ds5})}{g_{m7}r_{ds7}} \right]} = \frac{g_{m2}v_{in}}{2 \left(1 + \frac{R_{II}(g_{ds2} + g_{ds5})}{g_{m7}r_{ds7}} \right)} = \frac{g_{m2}v_{in}}{2(1+k)} \quad \text{where} \quad k = \frac{R_{II}(g_{ds2} + g_{ds5})}{g_{m7}r_{ds7}}$$

The output voltage, v_{out} , is equal to the sum of i_7 and i_{10} flowing through R_{out} . Thus,

$$\frac{v_{out}}{v_{in}} = \left(\frac{g_{m1}}{2} + \frac{g_{m2}}{2(1+k)} \right) R_{out} = \left(\frac{2+k}{2+2k} \right) g_{m1} R_{out}$$

Frequency Response of the Folded Cascode Op Amp

The frequency response of the folded cascode op amp is determined primarily by the output pole which is given as

$$p_{out} = \frac{-1}{R_{out}C_{out}}$$

where C_{out} is all the capacitance connected from the output of the op amp to ground.

All other poles must be greater than $GB = g_{m1}/C_{out}$. The approximate expressions for each pole is

- 1.) Pole at node A: $p_A \approx -g_{m6}/C_A$
- 2.) Pole at node B: $p_B \approx -g_{m7}/C_B$
- 3.) Pole at drain of M6: $p_6 \approx -g_{m10}/C_6$
- 4.) Pole at source of M8: $p_8 \approx -(g_{m8}r_{ds8}g_{m10})/C_8$
- 5.) Pole at source of M9: $p_9 \approx -g_{m9}/C_9$

where the approximate expressions are found by the reciprocal product of the resistance and parasitic capacitance seen to ground from a given node. One might feel that because R_B is approximately r_{ds} that this pole might be too small. However, at frequencies where this pole has influence, C_{out} , causes R_{out} to be much smaller making p_B also non-dominant.

Example 6.5-3 - Folded Cascode, CMOS Op Amp

Assume that all $g_{mN} = g_{mP} = 100\mu\text{S}$, $r_{dsN} = 2\text{M}\Omega$, $r_{dsP} = 1\text{M}\Omega$, and $C_L = 10\text{pF}$. Find all of the small-signal performance values for the folded-cascode op amp.

$$R_{II} = 0.4\text{G}\Omega, R_A = 10\text{k}\Omega, \text{ and } R_B = 4\text{M}\Omega \quad \therefore k = \frac{0.4 \times 10^9 (0.3 \times 10^{-6})}{100} = 1.2$$

$$\frac{v_{out}}{v_{in}} = \left(\frac{2+1.2}{2+2.4} \right) (100)(57.143) = 4,156\text{V/V}$$

$$R_{out} = R_{II} \parallel [g_{m7}r_{ds7}(r_{ds5} \parallel r_{ds2})] = 400\text{M}\Omega \parallel [(100)(0.667\text{M}\Omega)] = 57.143\text{M}\Omega$$

$$|p_{out}| = \frac{1}{R_{out}C_{out}} = \frac{1}{57.143\text{M}\Omega \cdot 10\text{pF}} = 1,750 \text{ rads/sec.} \Rightarrow 278\text{Hz} \Rightarrow GB = 1.21\text{MHz}$$

PSRR of the Folded Cascode Op Amp

Consider the following circuit used to model the PSRR:-

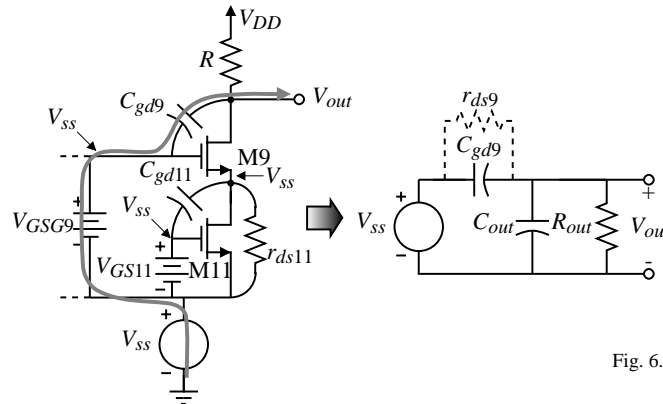


Fig. 6.5-9A

This model assumes that gate, source and drain of M11 and the gate and source of M9 all vary with V_{GS} .


We shall examine V_{out}/V_{SS} rather than $PSRR^-$. (Small V_{out}/V_{SS} will lead to large $PSRR^-$.)

The transfer function of V_{out}/V_{SS} can be found as

$$\frac{V_{out}}{V_{SS}} \approx \frac{sC_{gd9}R_{out}}{sC_{out}R_{out}+1} \quad \text{for } C_{gd9} < C_{out}$$

The approximate $PSRR^-$ is sketched on the next page.

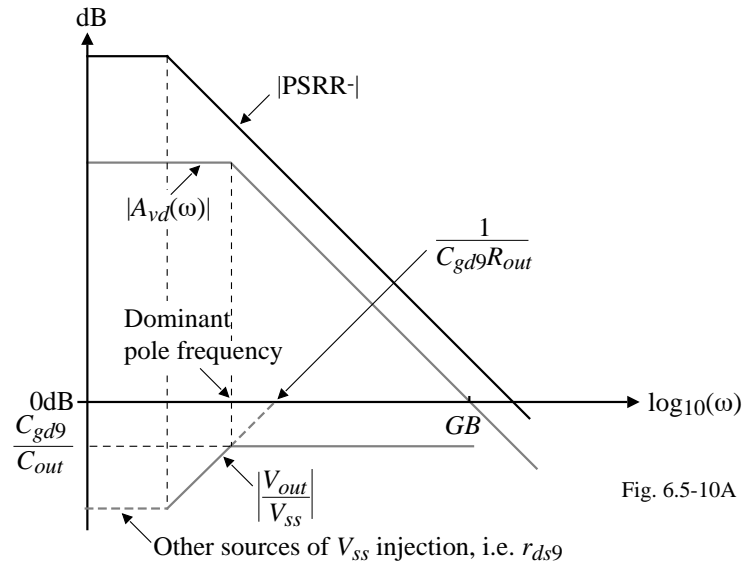Frequency Response of the PSRR- of the Folded Cascode Op Amp



We see that the PSRR of the cascode op amp is much better than the two-stage op amp.

Design Approach for the Folded-Cascode Op Amp

Step	Relationship	Design Equation/Constraint	Comments
1	Slew Rate	$I_3 = SR \cdot C_L$	
2	Bias currents in output cascodes	$I_4 = I_5 = 1.2I_3$ to $1.5I_3$	Avoid zero current in cascodes
3	Maximum output voltage, $v_{out(max)}$	$S_5 = \frac{2I_5}{K_P \cdot V_{SD5}^2}$, $S_7 = \frac{2I_7}{K_P \cdot V_{SD7}^2}$, ($S_4 = S_5$ and $S_6 = S_7$)	$V_{SD5(sat)} = V_{SD7(sat)} = 0.5[V_{DD} - V_{out(max)}]$
4	Minimum output voltage, $v_{out(min)}$	$S_{11} = \frac{2I_{11}}{K_N \cdot V_{DS11}^2}$, $S_9 = \frac{2I_9}{K_N \cdot V_{DS9}^2}$, ($S_{10} = S_{11}$ and $S_8 = S_9$)	$V_{DS9(sat)} = V_{DS11(sat)} = 0.5[V_{out(min)} - V_{SS}]$
5	$GB = \frac{gm1}{C_L}$	$S_1 = S_2 = \frac{gm1^2}{K_N \cdot I_3} = \frac{GB^2 C_L^2}{K_N \cdot I_3}$	
6	Minimum input CM	$S_3 = \frac{2I_3}{K_N \cdot (V_{in(min)} - V_{SS} - \sqrt{(I_3/K_N \cdot S_1)} - V_{T1})^2}$	
7	Maximum input CM	$S_4 = S_5 = \frac{2I_4}{K_P \cdot (V_{DD} - V_{in(max)} + V_{T1})^2}$	S_4 and S_5 must meet or exceed value in step 3
8	Differential Voltage Gain	$\frac{v_{out}}{v_{in}} = \left(\frac{gm1}{2} + \frac{gm2}{2(1+k)} \right) R_{out} = \left(\frac{2+k}{2+2k} \right) gm1 R_{out}$	$k = \frac{R_{II}(g_{ds2} + g_{ds4})}{gm7 r_{ds7}}$
9	Power dissipation	$P_{diss} = (V_{DD} - V_{SS})(I_3 + I_{10} + I_{11})$	

Example 6.5-3 Design of a Folded-Cascode Op Amp

Follow the procedure given to design the folded-cascode op amp when the slew rate is $10\text{V}/\mu\text{s}$, the load capacitor is 10pF , the maximum and minimum output voltages are $\pm 2\text{V}$ for $\pm 2.5\text{V}$ power supplies, the GB is 10MHz , the minimum input common mode voltage is -1.5V and the maximum input common mode voltage is 2.5V . The differential voltage gain should be greater than $5,000\text{V}/\text{V}$ and the power dissipation should be less than 5mW . Use channel lengths of $1\mu\text{m}$.

Solution

Following the approach outlined above we obtain the following results.

$$I_3 = SR \cdot C_L = 10 \times 10^6 \cdot 10^{-11} = 100\mu\text{A}$$

Select $I_4 = I_5 = 125\mu\text{A}$.

Next, we see that the value of $0.5(V_{DD} - V_{out}(\text{max}))$ is $0.5\text{V}/2$ or 0.25V . Thus,

$$S_4 = S_5 = \frac{2 \cdot 125\mu\text{A}}{50\mu\text{A}/\text{V}^2 \cdot (0.25\text{V})^2} = \frac{2 \cdot 125 \cdot 16}{50} = 80$$

and assuming worst case currents in M_6 and M_7 gives,

$$S_6 = S_7 = \frac{2 \cdot 125\mu\text{A}}{50\mu\text{A}/\text{V}^2 \cdot (0.25\text{V})^2} = \frac{2 \cdot 125 \cdot 16}{50} = 80$$

The value of $0.5(V_{out}(\text{min}) - |V_{SS}|)$ is also 0.25V which gives the value of S_8, S_9, S_{10} and

$$S_{11} \text{ as } S_8 = S_9 = S_{10} = S_{11} = \frac{2 \cdot I_8}{K_N' V_{DS8}^2} = \frac{2 \cdot 125}{110 \cdot (0.25)^2} = 36.36$$

Example 6.5-3 - Continued

In step 5, the value of GB gives S_1 and S_2 as

$$S_1 = S_2 = \frac{GB^2 \cdot C_L^2}{K_N' I_3} = \frac{(20\pi \times 10^6)^2 (10^{-11})^2}{110 \times 10^{-6} \cdot 100 \times 10^{-6}} = 35.9$$

The minimum input common mode voltage defines S_3 as

$$S_3 = \frac{2I_3}{K_N' \left(V_{in}(\text{min}) - V_{SS} - \sqrt{\frac{I_3}{K_N' S_1}} - V_{T1} \right)^2} = \frac{200 \times 10^{-6}}{110 \times 10^{-6} \left(-1.5 + 2.5 - \sqrt{\frac{100}{110 \cdot 35.9}} - 0.7 \right)^2} = 91.6$$

We need to check that the values of S_4 and S_5 are large enough to satisfy the maximum input common mode voltage. The maximum input common mode voltage of 2.5 requires

$$S_4 = S_5 \geq \frac{2I_4}{K_P' [V_{DD} - V_{in}(\text{max}) + V_{T1}]^2} = \frac{2 \cdot 125\mu\text{A}}{50 \times 10^{-6} \text{A}/\text{V}^2 [0.7\text{V}]^2} = 10.2$$

which is much less than 80 . In fact, with $S_4 = S_5 = 80$, the maximum input common mode voltage is 3V .

The power dissipation is found to be

$$P_{diss} = 5\text{V}(125\mu\text{A} + 125\mu\text{A}) = 1.25\text{mW}$$

Example 6.5-3 - Continued

The small-signal voltage gain requires the following values to evaluate:

$$S_4, S_5: \quad g_m = \sqrt{2 \cdot 125 \cdot 50 \cdot 80} = 1000 \mu\text{S} \quad \text{and} \quad g_{ds} = 125 \times 10^{-6} \cdot 0.05 = 6.25 \mu\text{S}$$

$$S_6, S_7: \quad g_m = \sqrt{2 \cdot 75 \cdot 50 \cdot 80} = 774.6 \mu\text{S} \quad \text{and} \quad g_{ds} = 75 \times 10^{-6} \cdot 0.05 = 3.75 \mu\text{S}$$

$$S_8, S_9, S_{10}, S_{11}: \quad g_m = \sqrt{2 \cdot 75 \cdot 110 \cdot 36.36} = 774.6 \mu\text{S} \quad \text{and} \quad g_{ds} = 75 \times 10^{-6} \cdot 0.04 = 3 \mu\text{S}$$

$$S_1, S_2: \quad g_{mI} = \sqrt{2 \cdot 50 \cdot 110 \cdot 35.9} = 628 \mu\text{S} \quad \text{and} \quad g_{ds} = 50 \times 10^{-6} (0.04) = 2 \mu\text{S}$$

Thus,

$$R_{II} \approx g_{m9} r_{ds9} r_{ds11} = (774.6 \mu\text{S}) \left(\frac{1}{3 \mu\text{S}} \right) \left(\frac{1}{3 \mu\text{S}} \right) = 86.07 \text{M}\Omega$$

$$R_{out} \approx 86.07 \text{M}\Omega \parallel (774.6 \mu\text{S}) \left(\frac{1}{3.75 \mu\text{S}} \right) \left(\frac{1}{2 \mu\text{S} + 6.25 \mu\text{S}} \right) = 19.40 \text{M}\Omega$$

$$k = \frac{R_{II}(g_{ds2} + g_{ds4})}{g_{m7} r_{ds7}} = \frac{86.07 \text{M}\Omega (2 \mu\text{S} + 6.25 \mu\text{S}) (3.75 \mu\text{S})}{774.6 \mu\text{S}} = 3.4375$$

The small-signal, differential-input, voltage gain is

$$A_{vd} = \left(\frac{2+k}{2+2k} \right) g_{mI} R_{out} = \left(\frac{2+3.4375}{2+6.875} \right) 0.628 \times 10^{-3} \cdot 19.40 \times 10^6 = 7,464 \text{ V/V}$$


The gain is larger than required by the specifications which should be okay.

Comments on Folded Cascode Op Amps

- Good PSRR
- Good ICMR
- Self compensated
- Can cascade an output stage to get extremely high gain with lower output resistance (use Miller compensation in this case)
- Need first stage gain for good noise performance
- Widely used in telecommunication circuits where large dynamic range is required

Enhanced-Gain, Folded Cascode Op Amps

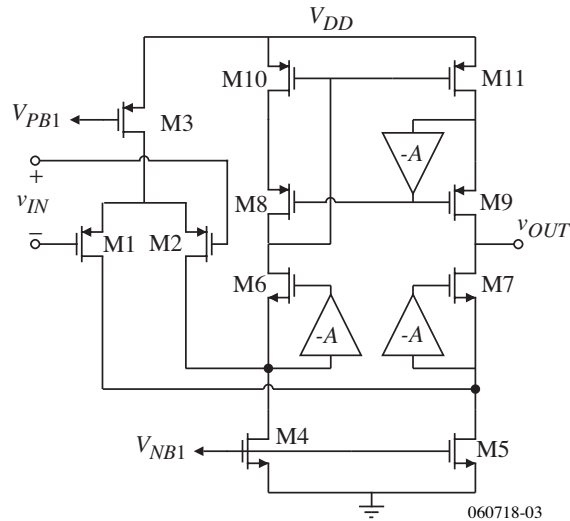If more gain is needed, the folded cascode op amp can be enhanced to boost the output impedance even higher as follows.



$$\text{Voltage gain} = g_{m1}R_{out},$$

where

$$R_{out} \approx [A r_{ds7} g_{m7} (r_{ds1} \parallel r_{ds5})] \parallel (A r_{ds9} g_{m9} r_{ds11})$$

Since $A \approx g_m r_{ds}$ the voltage gain would be in the range of 100,000 to 500,000.


Note that to achieve maximum output swing, it will be necessary to make sure that M5 and M11 are biased with $V_{DS} = V_{DS}(\text{sat})$.

What are the Enhancement Amplifiers?

Requirements:

- 1.) Need a gain of $g_m r_{ds}$.
- 2.) Must be able to set the dc voltage at its input to get wide-output voltage swing.

Possible Enhancement Amplifiers:

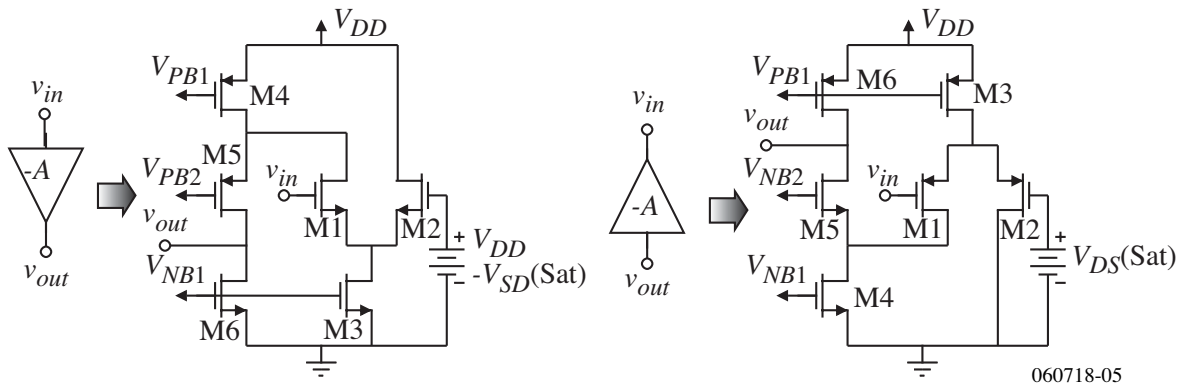


Frequency Response of the Enhanced Gain Cascode Op Amps

Normally, the frequency response of the cascode op amps would have one dominant pole at the output. The frequency response would be,

$$A_v(s) = g_{m1} \left(\frac{R_{out}(1/sC_{out})}{R_{out} + 1/sC_{out}} \right) = \frac{g_{m1}R_{out}}{sR_{out}C_{out} + 1} = \frac{g_{m1}R_{out}}{1 - \frac{s}{p_1}}$$

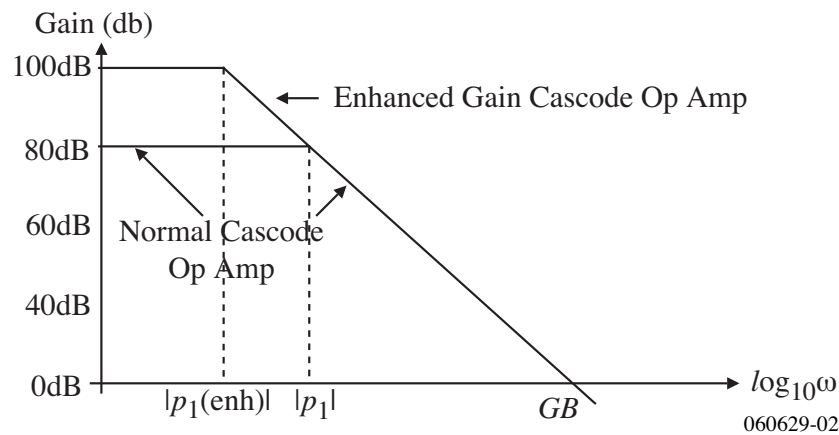If the amplifier used to boost the output resistance had no frequency dependence then the frequency response would be as follows.



Frequency Response of the Enhanced Gain Cascode Op Amp – Continued

- Does the pole in the feedback amplifier A have an influence?

Although the output resistance can be modeled as,

$$R_{out}' \approx R_{out} A_o \left(\frac{1 - \frac{s}{p_2 A_o}}{1 - \frac{s}{p_2}} \right)$$

it has no influence on the frequency response because C_{out} has shorted out any influence a change in R_{out} might have.

- Higher order poles come from a diversion of the current flow in the op amp to ground rather than the intended destination of the current to the output. These poles that divert the current are:
 - Pole at the source of M6 (A_{gm6}/C_6) - Pole at the source of M7 (A_{gm7}/C_7)
 - Pole at the drain of M8 (A_{gm10}/C_8) - Pole at the source of M9 (A_{gm9}/C_6)
 - Pole at the drain of M10 ($g_{m8}r_{ds8}g_{m10}/C_{10}$)

Note that the enhancement amplifiers cause all higher-order poles to be moved out by $|A|$. Therefore, the GB of the enhanced gain cascode op amp should be able to be increased by $|A|$.

SECTION 6.5 - SIMULATION AND MEASUREMENT OF OP AMPS

Simulation and Measurement Considerations

Objectives:

- The objective of simulation is to verify and optimize the design.
- The objective of measurement is to experimentally confirm the specifications.

Similarity Between Simulation and Measurement:

- Same goals
- Same approach or technique

Differences Between Simulation and Measurement:

- Simulation can idealize a circuit
- Measurement must consider all nonidealities

Simulating or Measuring the Open-Loop Transfer Function of the Op Amp

Circuit (Darkened op amp identifies the op amp under test):

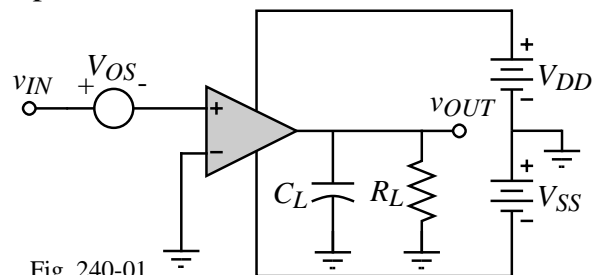


Fig. 240-01

Simulation:

This circuit will give the voltage transfer function curve. This curve should identify:

- 1.) The linear range of operation
- 2.) The gain in the linear range
- 3.) The output limits
- 4.) The systematic input offset voltage
- 5.) DC operating conditions, power dissipation
- 6.) When biased in the linear range, the small-signal frequency response can be obtained
- 7.) From the open-loop frequency response, the phase margin can be obtained ($F = 1$)

Measurement:

This circuit probably will not work unless the op amp gain is very low.

A More Robust Method of Measuring the Open-Loop Frequency Response

Circuit:

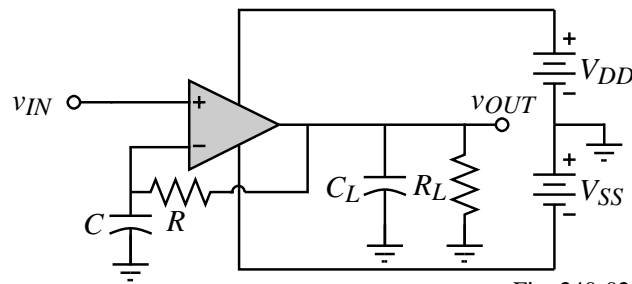


Fig. 240-02

Resulting Closed-Loop Frequency Response:

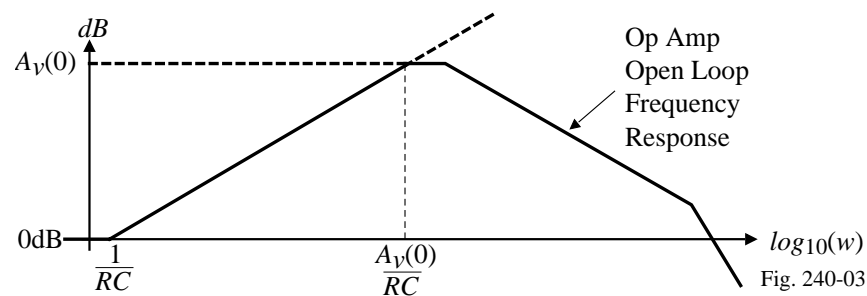


Fig. 240-03

Make the RC product as large as possible.

Simulation and Measurement of Open-Loop Frequency Response with Moderate Gain Op Amps


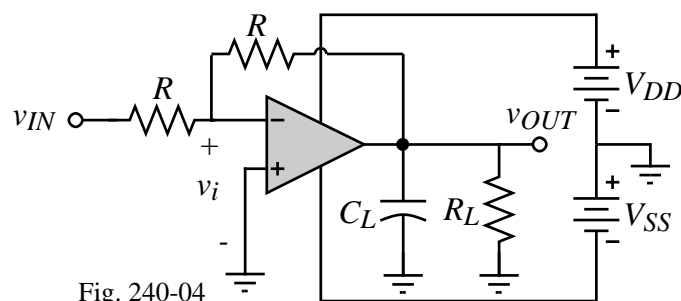


Fig. 240-04

Make R as large and measure v_{out} and v_i to get the open loop gain.

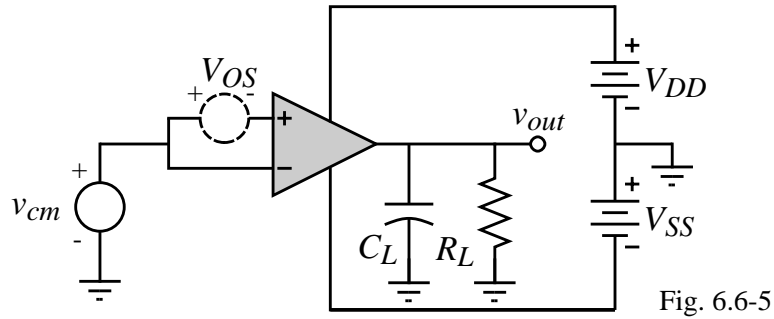
Simulation of the Common-Mode Voltage Gain



Make sure that the output voltage of the op amp is in the linear region.

Simulation of CMRR of an Op Amp

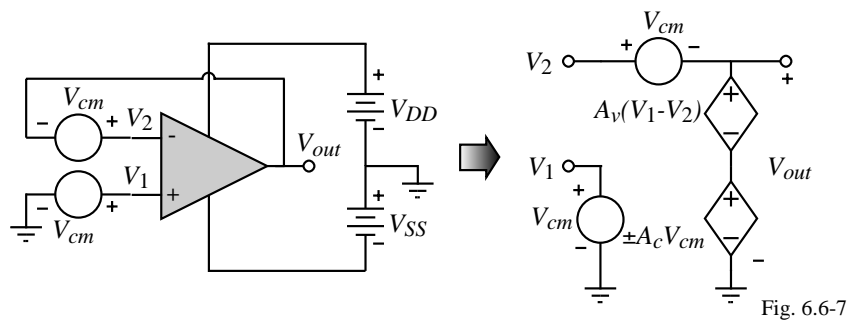None of the above methods are really suitable for simulation of *CMRR*. Consider the following:



$$V_{out} = A_v(V_1 - V_2) \pm A_{cm} \left(\frac{V_1 + V_2}{2} \right) = -A_v V_{out} \pm A_{cm} V_{cm}$$


$$V_{out} = \frac{\pm A_{cm}}{1 + A_v} V_{cm} \approx \frac{\pm A_{cm}}{A_v} V_{cm}$$

$$\therefore \boxed{|CMRR| = \frac{A_v}{A_{cm}} = \frac{V_{cm}}{V_{out}}}$$

(However, $PSRR^+$ must equal $PSRR^-$)

Direct Simulation of PSRR

Circuit:

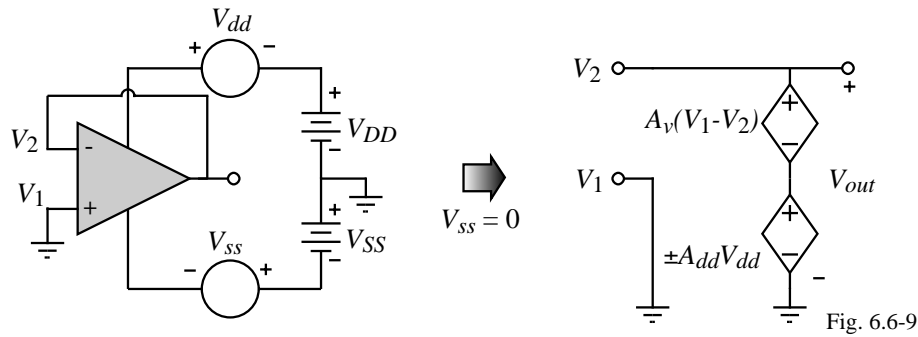

$$V_{out} = A_v(V_1 - V_2) \pm A_{dd}V_{dd} = -A_vV_{out} \pm A_{dd}V_{dd}$$

$$V_{out} = \frac{\pm A_{dd}}{1 + A_v} V_{dd} \approx \frac{\pm A_{dd}}{A_v} V_{dd}$$

$$\therefore PSRR^+ = \frac{A_v}{A_{dd}} = \frac{V_{dd}}{V_{out}} \quad \text{and} \quad PSRR^- = \frac{A_v}{A_{ss}} = \frac{V_{ss}}{V_{out}}$$

Works well as long as $CMRR$ is much greater than 1.

Measurement of A_v , $CMRR$ and $PSRR$

Configuration:

$$\text{Note that } v_I \approx \frac{v_{OS}}{1000} \quad \text{or} \quad v_{OS} \approx 1000v_I$$

How Does this Circuit Work?

$CMRR$:

1.) Set

$$V_{DD}' = V_{DD} + 1V$$

$$V_{SS}' = V_{SS} + 1V$$

$$v_{OUT}' = v_{OUT} + 1V$$

2.) Measure v_{OS} (v_{OS1})

3.) Set

$$V_{DD}' = V_{DD} - 1V$$

$$V_{SS}' = V_{SS} - 1V$$

$$v_{OUT}' = v_{OUT} - 1V$$

4.) Measure v_{OS} (v_{OS2})

5.)

$$CMRR = \frac{2000}{|v_{OS2} - v_{OS1}|}$$

$PSRR$:

1.) Set

$$V_{DD}' = V_{DD} + 1V$$

$$V_{SS}' = V_{SS}$$

$$v_{OUT}' = 0V$$

2.) Measure v_{OS} (v_{OS3})

3.) Set

$$V_{DD}' = V_{DD} - 1V$$


$$V_{SS}' = V_{SS}$$

$$v_{OUT}' = 0V$$

4.) Measure v_{OS} (v_{OS4})

5.)

$$PSRR^+ = \frac{2000}{|v_{OS4} - v_{OS3}|}$$

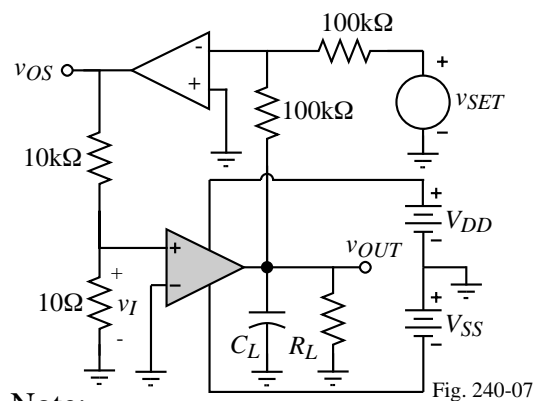

Note:

1.) $PSRR^-$ can be measured similar to $PSRR^+$ by changing only V_{SS} .

2.) The $\pm 1V$ perturbation can be replaced by a sinusoid to measure $CMRR$ or $PSRR$ as follows:

$$PSRR^+ = \frac{1000 \cdot v_{dd}}{v_{OS}}, \quad PSRR^- = \frac{1000 \cdot v_{ss}}{v_{OS}}$$

$$\text{and } CMRR = \frac{1000 \cdot v_{cm}}{v_{OS}}$$

How Does the Previous Idea Work?

A circuit is shown which is used to measure the $CMRR$ and $PSRR$ of an op amp. Prove that the $CMRR$ can be given as

$$CMRR = \frac{1000 v_{icm}}{v_{os}}$$

Solution

The definition of the common-mode rejection ratio is

$$CMRR = \left| \frac{A_{vd}}{A_{cm}} \right| = \frac{(v_{out}/v_{id})}{(v_{out}/v_{icm})}$$

However, in the above circuit the value of v_{out} is the same so that we get

$$CMRR = \frac{v_{icm}}{v_{id}}$$

But $v_{id} = v_i$ and $v_{os} \approx 1000v_i = 1000v_{id} \Rightarrow v_{id} = \frac{v_{os}}{1000}$

Substituting in the previous expression gives, $CMRR = \frac{v_{icm}}{\frac{v_{os}}{1000}} = \frac{1000 v_{icm}}{v_{os}}$


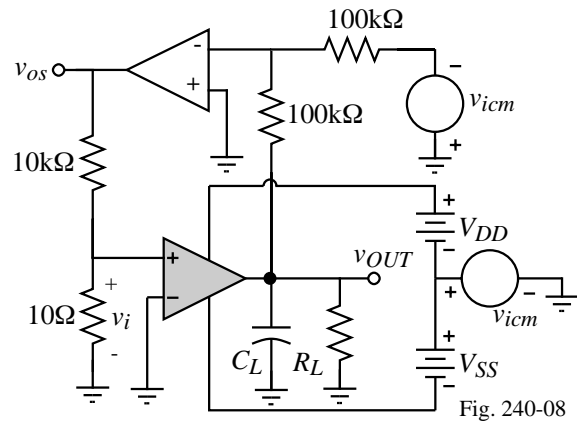


Fig. 240-08

Measurement of Open-Loop Gain

Measurement configuration:

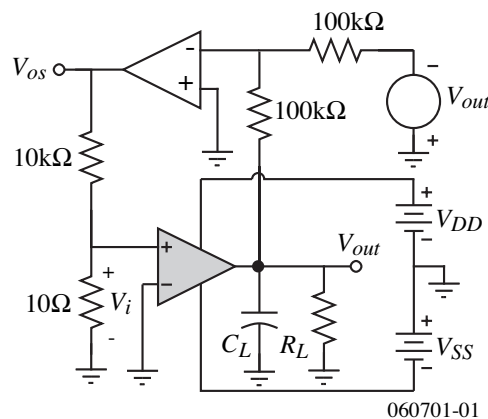


060701-01

$$A_{vd} = \frac{V_{out}}{V_{id}} = \frac{V_{out}}{V_i}$$

$$V_{os} \approx 1000V_i$$

Therefore, $A_{vd} = \frac{1000V_{out}}{V_{os}}$


Simulation or Measurement of *ICMR*

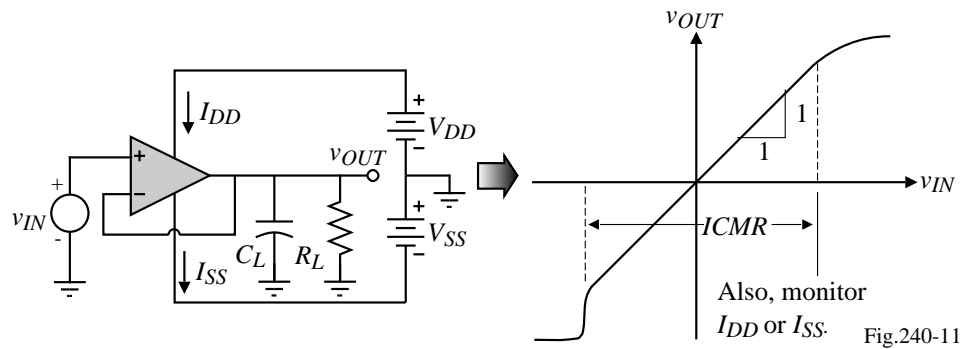

Initial jump in sweep is due to the turn-on of M5.

Should also plot the current in the input stage (or the power supply current).

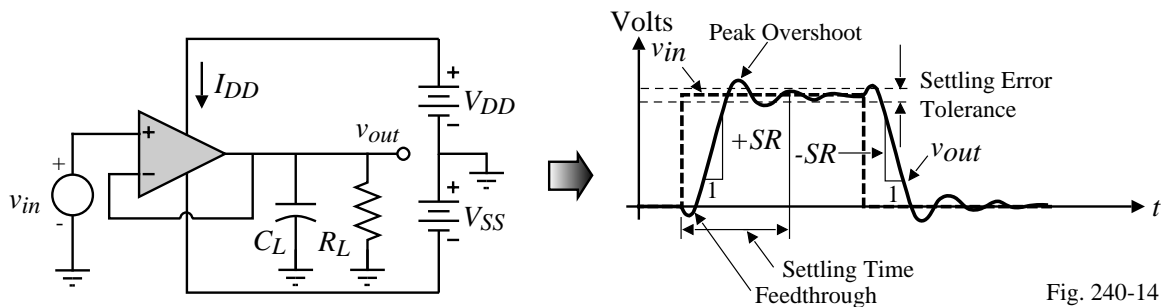Measurement or Simulation of Slew Rate and Settling Time



If the slew rate influences the small signal response, then make the input step size small enough to avoid slew rate (i.e. less than 0.5V for MOS).

Phase Margin and Peak Overshoot Relationship

It can be shown (Appendix C of the text) that:

$$\text{Phase Margin (Degrees)} = 57.2958 \cos^{-1}[\sqrt{4\zeta^4 + 1} - 2\zeta^2]$$

$$\text{Overshoot (\%)} = 100 \exp\left(\frac{-\pi\zeta}{\sqrt{1-\zeta^2}}\right)$$

For example, a 5% overshoot corresponds to a phase margin of approximately 64° .

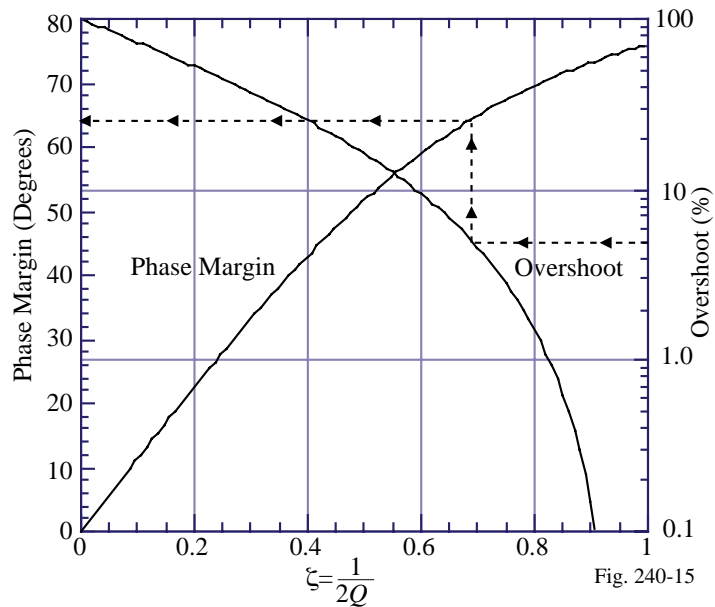


Fig. 240-15

Example 6.5-1 Simulation of the CMOS Op Amp of Ex. 6.3-1.

The op amp designed in Example 6.3-1 and shown in Fig. 6.3-3 is to be analyzed by SPICE to determine if the specifications are met. The device parameters to be used are those of Tables 3.1-2 and 3.2-1. In addition to verifying the specifications of Example 6.3-1, we will simulate PSRR+ and PSRR-.

Solution/Simulation

The op amp will be treated as a subcircuit in order to simplify the repeated analyses. The table on the next page gives the SPICE subcircuit description of Fig. 6.3-3. While the values of AD , AS , PD , and PS could be calculated if the physical layout was complete, we will make an educated estimate of these values by using the following approximations.

$$AS = AD \cong W[L1 + L2 + L3]$$

$$PS = PD \cong 2W + 2[L1 + L2 + L3]$$

where $L1$ is the minimum allowable distance between the polysilicon and a contact in the moat (Rule 5C of Table 2.6-1), $L2$ is the length of a minimum-size square contact to moat (Rule 5A of Table 2.6-1), and $L3$ is the minimum allowable distance between a contact to moat and the edge of the moat (Rule 5D of Table 2.6-1).


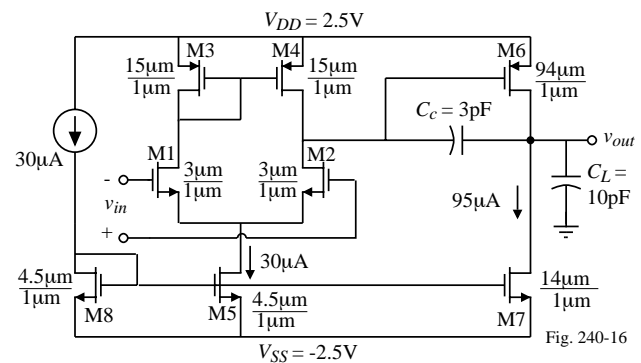


Fig. 240-16

Example 6.6-2 - Continued

Op Amp Subcircuit:

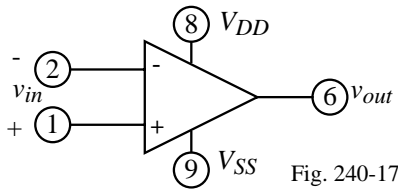

```

.SUBCKT OPAMP 1 2 6 8 9
M1 4 2 3 3 NMOS1 W=3U L=1U AD=18P AS=18P PD=18U PS=18U
M2 5 1 3 3 NMOS1 W=3U L=1U AD=18P AS=18P PD=18U PS=18U
M3 4 4 8 8 PMOS1 W=15U L=1U AD=90P AS=90P PD=42U PS=42U
M4 5 4 8 8 PMOS1 W=15U L=1U AD=90P AS=90P PD=42U PS=42U
M5 3 7 9 9 NMOS1 W=4.5U L=1U AD=27P AS=27P PD=21U PS=21U
M6 6 5 8 8 PMOS1 W=94U L=1U AD=564P AS=564P PD=200U PS=200U
M7 6 7 9 9 NMOS1 W=14U L=1U AD=84P AS=84P PD=40U PS=40U
M8 7 7 9 9 NMOS1 W=4.5U L=1U AD=27P AS=27P PD=21U PS=21U
CC 5 6 3.0P
.MODEL NMOS1 NMOS VTO=0.70 KP=110U GAMMA=0.4 LAMBDA=0.04 PHI=0.7
+MJ=0.5 MJSW=0.38 CGBO=700P CGSO=220P CGDO=220P CJ=770U CJSW=380P
+LD=0.016U TOX=14N
.MODEL PMOS1 PMOS VTO=-0.7 KP=50U GAMMA=0.57 LAMBDA=0.05 PHI=0.8
+MJ=0.5 MJSW=0.35 CGBO=700P CGSO=220P CGDO=220P CJ=560U CJSW=350P +LD=0.014U TOX=14N
IBIAS 8 7 30U
.ENDS

```

Example 6.6-2 - Continued

PSPICE Input File for the Open-Loop Configuration:

```

EXAMPLE 1 OPEN LOOP CONFIGURATION
.OPTION LIMPTS=1000
VIN+ 1 0 DC 0 AC 1.0
VDD 4 0 DC 2.5
VSS 0 5 DC 2.5
VIN - 2 0 DC 0
CL 3 0 10P
X1 1 2 3 4 5 OPAMP
:
:
(Subcircuit of previous slide)
:
:
.OP
.TF V(3) VIN+
.DC VIN+ -0.005 0.005 100U
.PRINT DC V(3)
.AC DEC 10 1 10MEG
.PRINT AC VDB(3) VP(3)
.PROBE (This entry is unique to PSPICE)
.END

```

Example 6.6-2 - Continued

Open-loop transfer characteristic of Example 6.3-1:

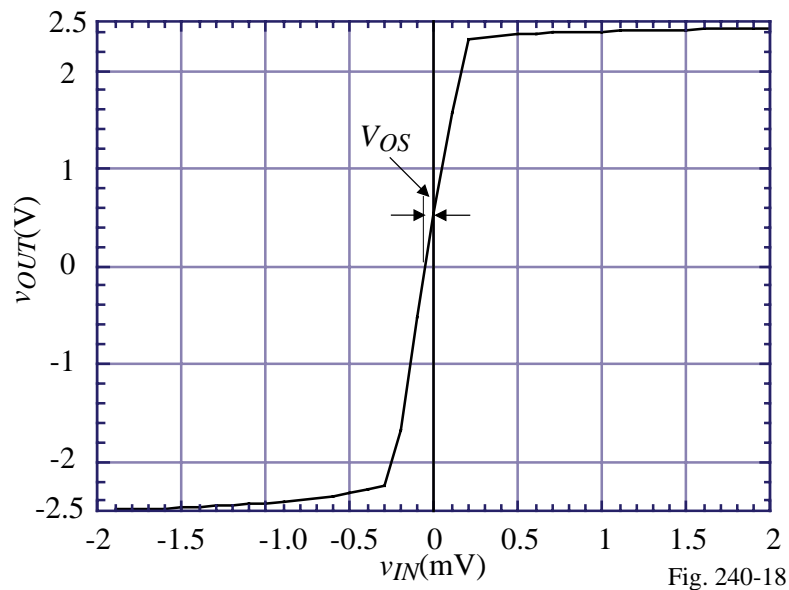


Fig. 240-18

Example 6.6-2 - Continued

Open-loop transfer frequency response of Example 6.3-1:

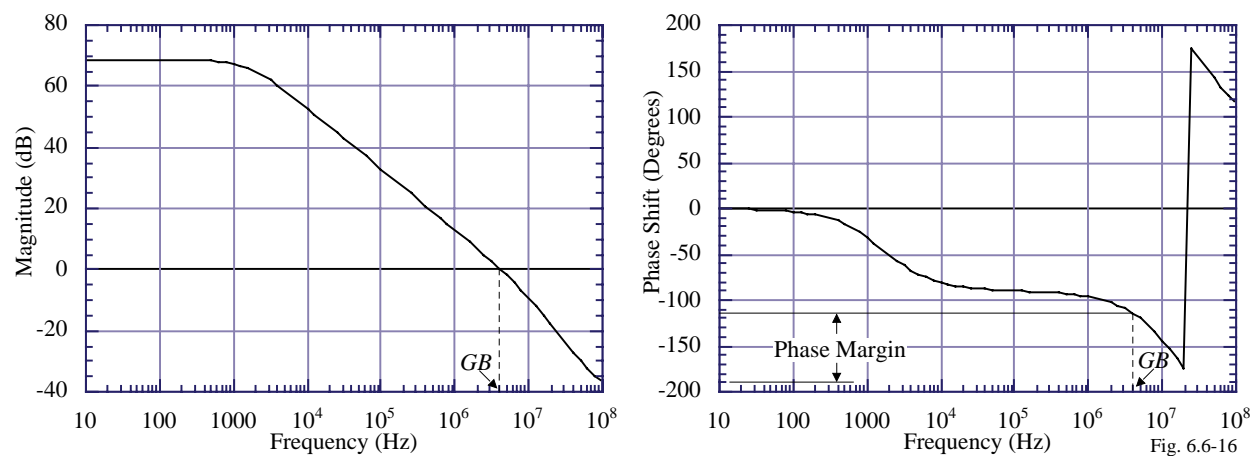


Fig. 6.6-16

Example 6.6-2 - Continued

Input common mode range of Example 6.3-1:

EXAMPLE 6.6-1 UNITY GAIN CONFIGURATION.

.OPTION LIMPTS=501

VIN+ 1 0 PWL(0 -2 10N -2 20N 2 2U 2 2.01U -2 4U -2 4.01U
+ -.1 6U -.1 6.0 1U .1 8U .1 8.01U -.1 10U -.1)

VDD 4 0 DC 2.5 AC 1.0

VSS 0 5 DC 2.5

CL 3 0 20P

X1 1 3 3 4 5 OPAMP

.....

(Subcircuit of Table 6.6-1)

.....

.DC VIN+ -2.5 2.5 0.1

.PRINT DC V(3)

.TRAN 0.05U 10U 0 10N

.PRINT TRAN V(3) V(1)

.AC DEC 10 1 10MEG

.PRINT AC VDB(3) VP(3)

.PROBE (This entry is unique to PSPICE)

.END

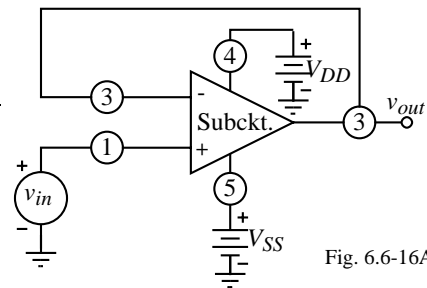


Fig. 6.6-16A

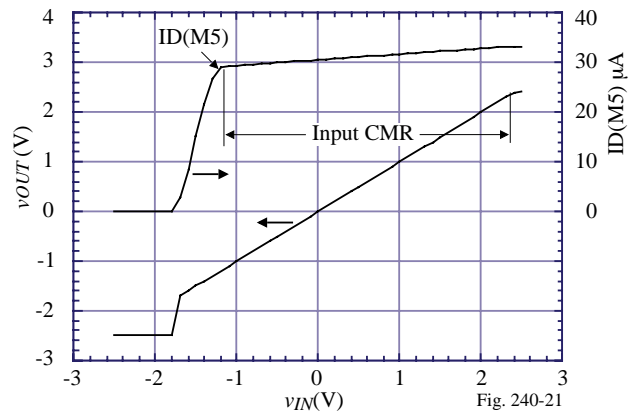


Fig. 240-21

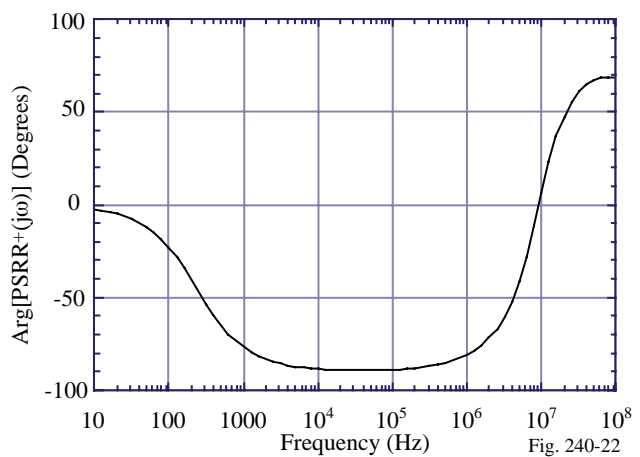
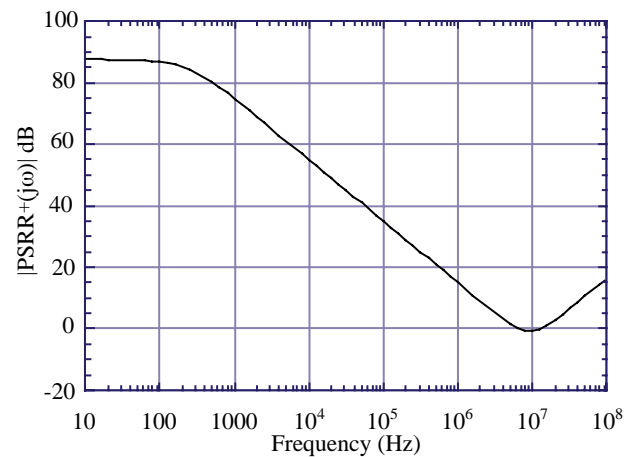
Example 6.6-2 - ContinuedPositive *PSRR* of Example 6.3-1:

Fig. 240-22

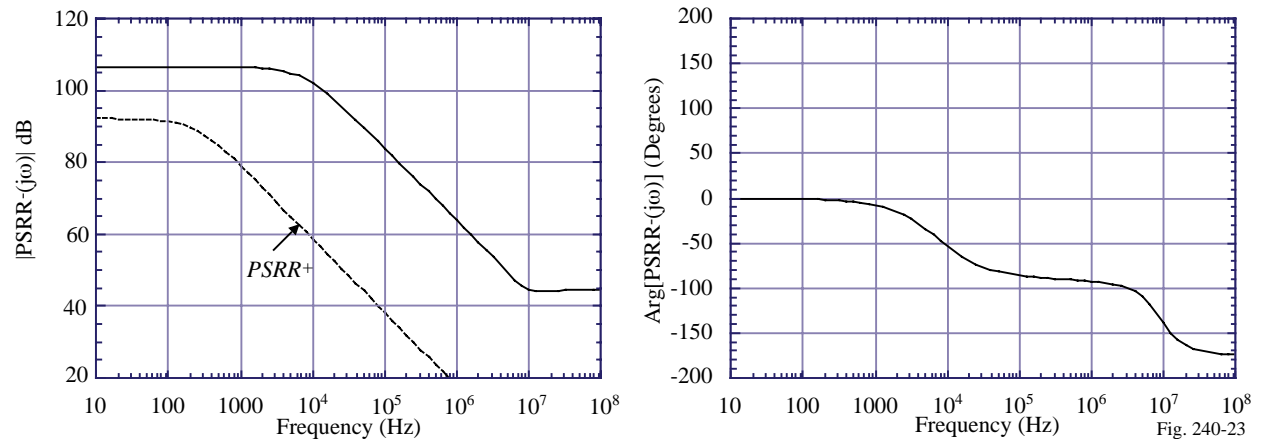
Example 6.6-2 - ContinuedNegative $PSRR$ of Example 6.3-1:

Fig. 240-23

Example 6.6-2 - Continued

Large-signal and small-signal transient response of Example 6.3-1:

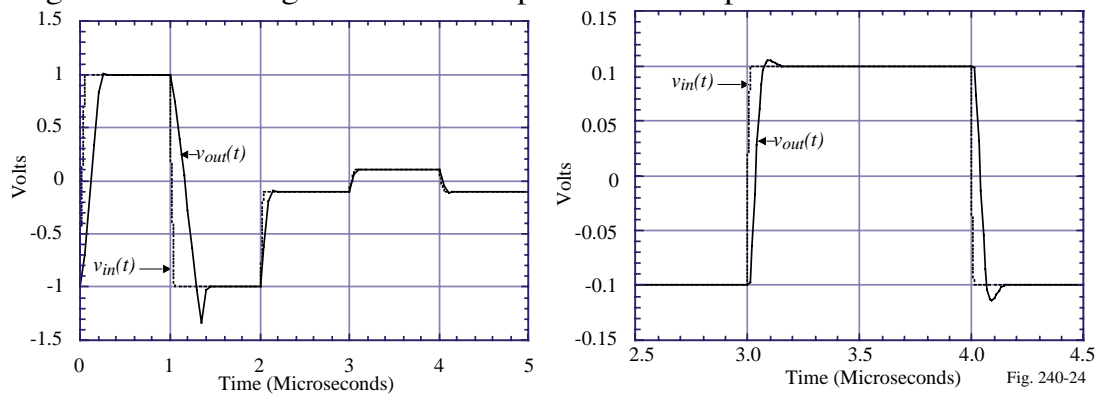


Fig. 240-24

Why the negative overshoot on the slew rate?

If M7 cannot sink sufficient current then the output stage slews and only responds to changes at the output via the feedback path which involves a delay.

Note that $-dv_{out}/dt \approx -2V/0.3\mu s = -6.67V/\mu s$. For a 10pF capacitor this requires $66.7\mu A$ and only $95\mu A - 66.7\mu A = 28\mu A$ is available for C_c . For the positive slew rate, M6 can provide whatever current is required by the capacitors and can immediately respond to changes at the output.

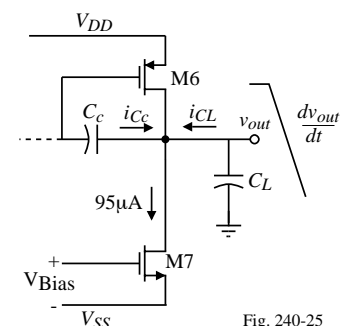


Fig. 240-25

Example 6.6-2 - Continued

Comparison of the Simulation Results with the Specifications of Example 6.3-1:

Specification (Power supply = $\pm 2.5\text{V}$)	Design (Ex. 6.3-1)	Simulation (Ex. 1)
Open Loop Gain	>5000	10,000
GB (MHz)	5 MHz	5 MHz
Input CMR (Volts)	-1V to 2V	-1.2 V to 2.4 V,
Slew Rate ($\text{V}/\mu\text{sec}$)	>10 ($\text{V}/\mu\text{sec}$)	+10, -7($\text{V}/\mu\text{sec}$)
P_{diss} (mW)	$< 2\text{mW}$	0.625mW
V_{out} range (V)	$\pm 2\text{V}$	+2.3V, -2.2V
PSRR+ (0) (dB)	-	87
PSRR- (0) (dB)	-	106
Phase margin (degrees)	60°	65°
Output Resistance ($\text{k}\Omega$)	-	122.5k Ω

Example 6.6-3

Why is the negative-going overshoot larger than the positive-going overshoot on the small-signal transient response of the last slide?

Consider the following circuit and waveform:

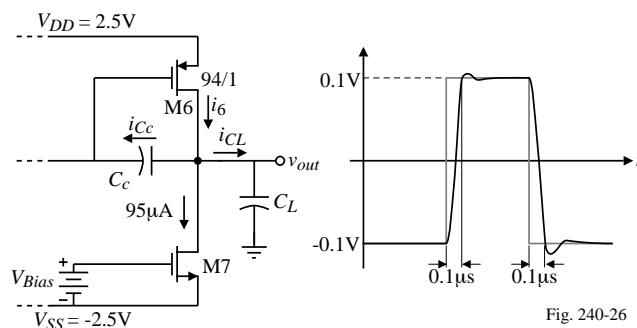


Fig. 240-26

During the rise time,

$$i_{CL} = C_L(dv_{out}/dt) = 10\text{pF}(0.2\text{V}/0.1\mu\text{s}) = 20\mu\text{A} \text{ and } i_{Cc} = 3\text{pF}(2\text{V}/\mu\text{s}) = 6\mu\text{A}$$

$$\therefore i_6 = 95\mu\text{A} + 20\mu\text{A} + 6\mu\text{A} = 121\mu\text{A} \Rightarrow g_{m6} = 1066\mu\text{S} \text{ (nominal was } 942.5\mu\text{S)}$$

$$\text{During the fall time, } i_{CL} = C_L(-dv_{out}/dt) = 10\text{pF}(-0.2\text{V}/0.1\mu\text{s}) = -20\mu\text{A}$$

$$\text{and } i_{Cc} = -3\text{pF}(2\text{V}/\mu\text{s}) = -6\mu\text{A}$$

$$\therefore i_6 = 95\mu\text{A} - 20\mu\text{A} - 6\mu\text{A} = 69\mu\text{A} \Rightarrow g_{m6} = 805\mu\text{S}$$

The dominant pole is $p_1 \approx (R_{I}g_{m6}R_{II}C_c)^{-1}$ but the GB is $g_{mI}/C_c = 94.25\mu\text{S}/3\text{pF} = 31.42 \times 10^6$ rads/sec and stays constant. Thus we must look elsewhere for the reason.

Recall that $p_2 \approx g_{m6}/C_L$ which explains the difference.

$$\therefore p_2(95\mu\text{A}) = 94.25 \times 10^6 \text{ rads/sec, } p_2(121\mu\text{A}) = 106.6 \times 10^6 \text{ rads/sec, and } p_2(69\mu\text{A}) = 80.05 \times 10^6 \text{ rads/sec. Thus, the phase margin is less during the fall time than the rise time.}$$

SECTION 6.6 - MACROMODELS FOR OP AMPS

Macromodel

A *macromodel* is a model that captures some or all of the performance of a circuit using different components (generally simpler).

A *macromodel* uses resistors, capacitors, inductors, controlled sources, and some active devices (mostly diodes) to capture the essence of the performance of a complex circuit like an op amp without modeling every internal component of the op amp.

Op Amp Characterization

- Small signal, frequency independent
- Small signal, frequency dependent
- Large signal
 - Time independent
 - Time dependent

SMALL SIGNAL, FREQUENCY INDEPENDENT, OP AMP MODELS

Simple Model

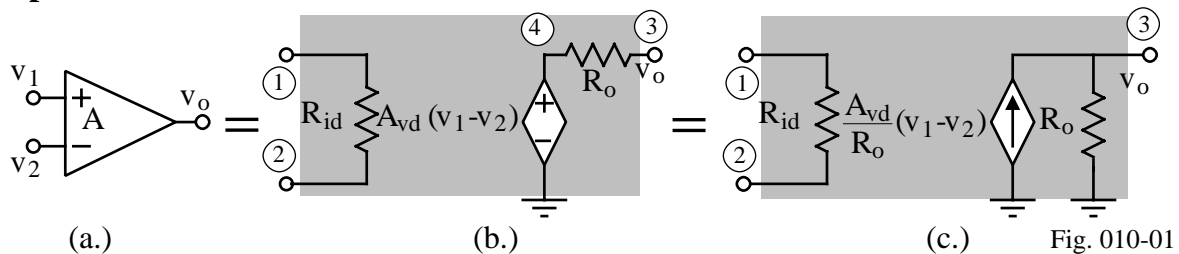


Figure 1 - (a.) Op amp symbol. (b.) Thevenin form of simple model. (c.) Norton form of simple model.

SPICE Description of Fig. 1c

```
RID 1 2 {Rid}
RO 3 0 {Ro}
GAVD 0 3 1 2 {Avd/Ro}
```

Subcircuit SPICE Description for Fig. 1c

```
.SUBCKT SIMPLEOPAMP 1 2 3
RID 1 2 {Rid}
RO 3 0 {Ro}
GAVD 0 3 1 2 {Avd/Ro}
.ENDS SIMPLEOPAMP
```

Example 6.6-1 - Use of the Simple Op Amp Model

Use SPICE to find the voltage gain, v_{out}/v_{in} , the input resistance, R_{in} , and the output resistance, R_{out} of Fig. 2. The op amp parameters are $A_{vd} = 100,000$, $R_{id} = 1\text{M}\Omega$, and $R_o = 100\Omega$. Find the input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, A_v , of the noninverting voltage amplifier configuration when $R_1 = 1\text{k}\Omega$ and $R_2 = 100\text{k}\Omega$.

Solution

The circuit with the SPICE node numbers identified is shown in Fig. 2.

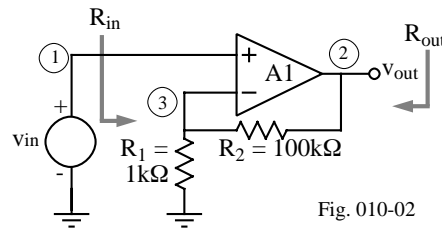


Fig. 010-02

Figure 2 – Noninverting voltage amplifier for Ex. 6.6-1.

The input file for this example is given as follows.

```
Example 1
VIN 1 0 DC 0 AC 1
XOPAMP1 1 3 2 SIMPLEOPAMP
R1 3 0 1KOHM
R2 2 3 100KOHM
.SUBCKT SIMPLEOPAMP 1 2 3
RID 1 2 1MEGOHM
RO 3 0 100OHM
GAVD/RO 0 3 1 2 1000
.ENDS SIMPLEOPAMP
.TF V(2) VIN
.END
```

The command .TF finds the small signal input resistance, output resistance, and voltage or current gain of an amplifier. The results extracted from the output file are:

```
**** SMALL-SIGNAL CHARACTERISTICS
V(2)/VIN = 1.009E+02
INPUT RESISTANCE AT VIN = 9.901E+08
OUTPUT RESISTANCE AT V(2) = 1.010E-01.
```

Common Mode Model

Electrical Model:

$$v_o = A_{vd}(v_1 - v_2) + \frac{A_{cm}(v_1 + v_2)}{2}$$

Macromodel:

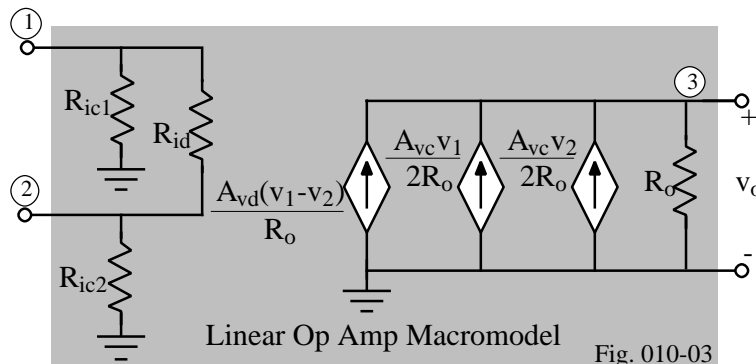


Fig. 010-03

Figure 3 - Simple op amp model including differential and common mode behavior.

SPICE File:

```
.SUBCKT LINOPAMP 1 2 3
RIC1 1 0 {Ric}
RID 1 2 {Rid}
RIC2 2 0 {Ric}
GAVD/RO 0 3 1 2 {A_vd/R_o}
GAVC1/RO 0 3 1 0 {A_vc/2R_o}
GAVC2/RO 0 3 2 0 {A_vc/2R_o}
RO 3 0 {R_o}
.ENDS LINOPAMP
```


SMALL SIGNAL, FREQUENCY DEPENDENT OP AMP MODELS

Dominant Pole Model

$$A_{vd}(s) = \frac{A_{vd}(0)}{(s/\omega_1) + 1} \quad \text{where } \omega_1 = \frac{1}{R_1 C_1} \quad (\text{dominant pole})$$

Model Using Passive Components:

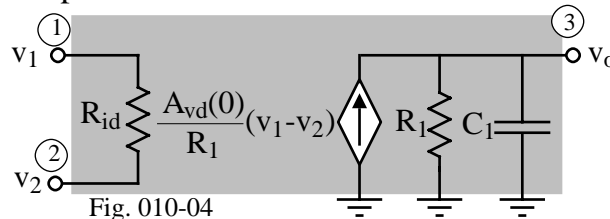


Fig. 010-04

Figure 4 - Macromodel for the op amp including the frequency response of A_{vd} .

Model Using Passive Components with Constant Output Resistance:

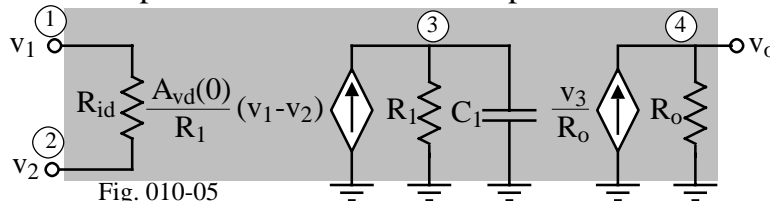


Fig. 010-05

Figure 5 - Frequency dependent model with constant output resistance.

Example 6.6-2 - Frequency Response of the Noninverting Voltage Amplifier

Use the model of Fig. 4 to find the frequency response of Fig. 2 if the gain is +1, +10, and +100 V/V assuming that $A_{vd}(0) = 10^5$ and $\omega_1 = 100$ rads/sec.

Solution

The parameters of the model are $R_2/R_1 = 0, 9$, and 99 . Let us additionally select $R_{id} = 1\text{M}\Omega$ and $R_o = 100\Omega$. We will use the circuit of Fig. 2 and insert the model as a subcircuit. The input file for this example is shown below.

Example 2

```
VIN 1 0 DC 0 AC 1
*Unity Gain Configuration
XOPAMP1 1 31 21
LINFREQOPAMP
R11 31 0 15GOHM
R21 21 31 1OHM
*Gain of 10 Configuration
XOPAMP2 1 32 22
LINFREQOPAMP
R12 32 0 1KOHM
R22 22 32 9KOHM
*Gain of 100 Configuration
XOPAMP3 1 33 23
LINFREQOPAMP
R13 33 0 1KOHM
R23 23 33 99KOHM
.SUBCKT
LINFREQOPAMP 1 2 3
RID 1 2 1MEGOHM
GAVD/RO 0 3 1 2 1000
R1 3 0 100
C1 3 0 100UF
.ENDS
.AC DEC 10 100 10MEG
.PRINT AC V(21) V(22) V(23)
.PROBE
.END
```

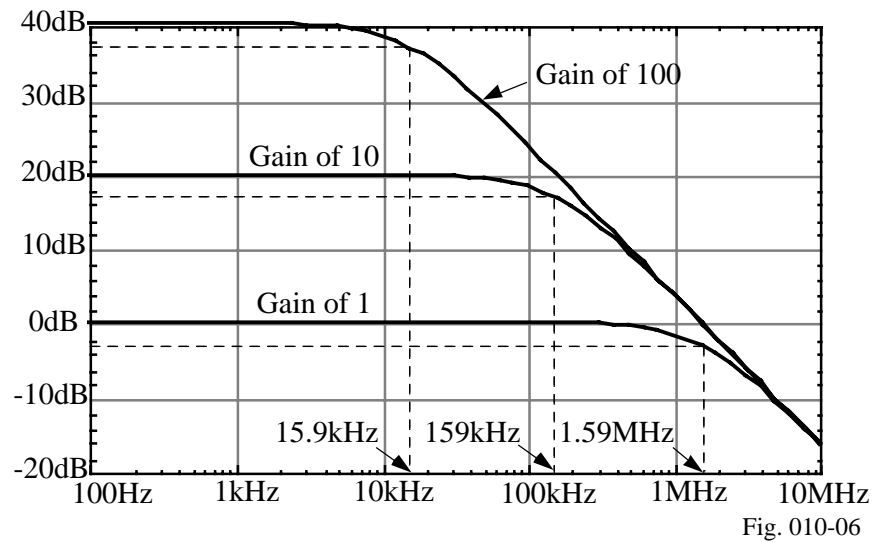
Example 6.6-2 - Continued

Figure 6 - Frequency response of the three noninverting voltage amplifiers of Ex. 6.6-2.

Behavioral Frequency Model

Use of Laplace behavioral modeling capability in PSPICE.

GAVD/RO 0 3 LAPLACE {V(1,2)} = {1000/(0.01s+1)}.

Implements,

$$G_{AVd/RO} = \frac{A_{vd}(s)}{R_o} = \frac{\frac{A_{vd}(0)}{R_o}}{\frac{s}{\omega_1} + 1}$$

where $A_{vd}(0) = 100,000$, $R_o = 100\Omega$, and $\omega_1 = 100$ rps

Differential and Common Mode Frequency Dependent Models

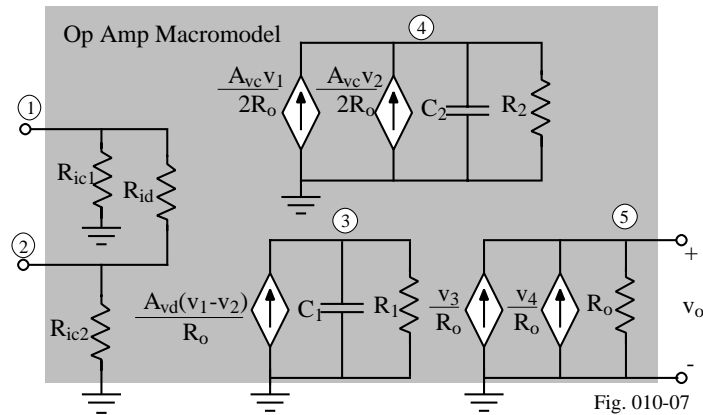


Figure 7 - Op amp macromodel for separate differential and common voltage gain frequency responses.

Zeros in the Transfer Function

Models:

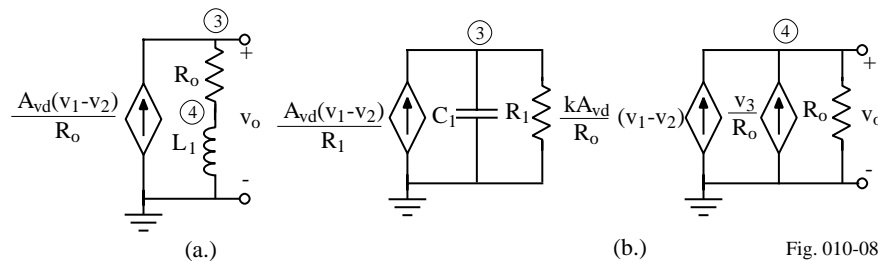


Figure 8 - (a.) Independent zero model. (b.) Method of modeling zeros without introducing new nodes.

Inductor:

$$V_o(s) = \left(\frac{A_{vd}(0)}{R_o} \right) (sL_1 + R_o) [V_1(s) - V_2(s)] = A_{vd}(0) \left(\frac{s}{R_o/L_1} + 1 \right) [V_1(s) - V_2(s)] .$$

Feedforward:

$$V_o(s) = \left(\frac{A_{vd}(0)}{(s/\omega_1) + 1} \right) [1 + k(s/\omega_1) + k] [V_1(s) - V_2(s)] .$$

The zero can be expressed as $z_1 = -\omega_1 \left(1 + \frac{1}{k} \right)$

where k can be + or - by reversing the direction of the current source.

Example 6.6-3 - Modeling Zeros in the Op Amp Frequency Response

Use the technique of Fig. 8b to model an op amp with a differential voltage gain of 100,000, a pole at 100rps, an output resistance of 100Ω, and a zero in the right-half, complex frequency plane at 10^7 rps.

Solution

The transfer function we want to model is given as

$$V_o(s) = \frac{10^5(s/10^7 - 1)}{(s/100 + 1)} .$$

Let us arbitrarily select R_1 as 100kΩ which will make the GA_{VD}/R_1 gain unity. To get the pole at 100rps, $C_1 = 1/(100R_1) = 0.1\mu\text{F}$. Next, we want z_1 to be 10^7 rps. Since $\omega_1 = 100\text{rps}$, then Eq. (6) gives k as -10^{-5} . The following input file verifies this model.

Example 3	GV3/RO 0 4 3 0 0.01
VIN 1 0 DC 0 AC 1	GA _{VD} /RO 4 0 1 2 0.01
XOPAMP1 1 0 2 LINFREQOPAMP	RO 4 0 100
.SUBCKT LINFREQOPAMP 1 2 4	.ENDS
RID 1 2 1MEGOHM	.AC DEC 10 1 100MEG
GA _{VD} /R1 0 3 1 2 1	.PRINT AC V(2) VDB(2) VP(2)
R1 3 0 100KOHM	.PROBE
C1 3 0 0.1UF	.END

Example 6.6-3 - Continued

The asymptotic magnitude frequency response of this simulation is shown in Fig. 9. We note that although the frequency response is plotted in Hertz, there is a pole at 100rps (15.9Hz) and a zero at 1.59MHz (10Mrps). Unless we examined the phase shift, it is not possible to determine whether the zero is in the RHP or LHP of the complex frequency axis.

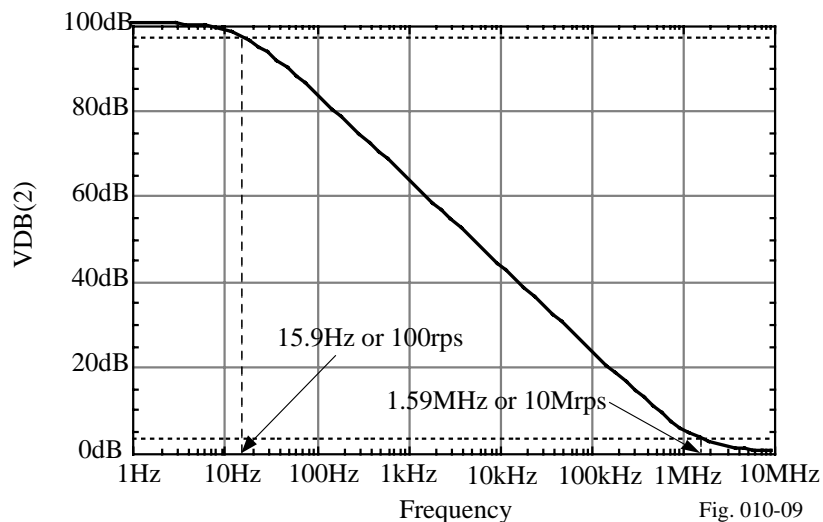


Figure 9 - Asymptotic magnitude frequency response of the op amp model of Ex. 6.6-3.

LARGE SIGNAL MACROMODELS FOR THE OP AMP

Output and Input Voltage Limitations

Figure 10 - Op amp macromodel that limits the input and output voltages.

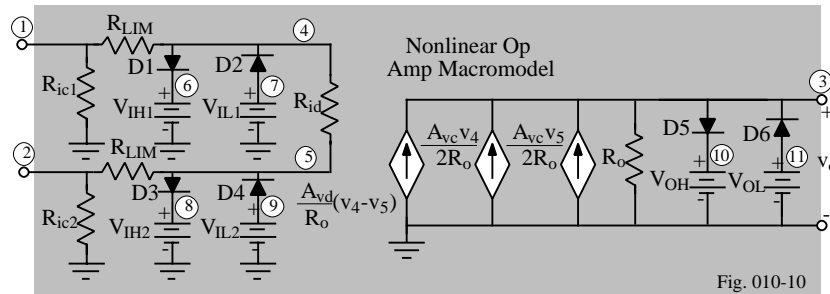


Fig. 010-10

Subcircuit Description

```
.SUBCKT NONLINOPAMP 1 2 3
RIC1 1 0 {R_icm}
RLIM1 1 4 0.1
D1 4 6 IDEALMOD
VIH1 6 0 {VIH1}
D2 7 4 IDEALMOD
VIL1 7 0 {VIL1}
RID 4 5 {R_id}
RIC2 2 0 {R_icm}
RLIM2 2 5 0.1
D3 5 8 IDEALMOD
VIH2 8 0 {VIH1}
D4 9 5 IDEALMOD
VIL2 9 0 {VIL2}
GAVD/RO 0 3 4 5 {A_vd/R_o}
GAVC1/RO 0 3 4 0 {A_vc/R_o}
GAVC2/RO 0 3 5 0 {A_vc/R_o}
RO 3 0 {R_o}
D5 3 10 IDEALMOD
VOH 10 0 {V_OH}
D6 11 3 IDEALMOD
VOL 11 0 {V_OL}
.MODEL IDEALMOD D N=0.001
.ENDS
```

Example 6.6-4 - Illustration of the Voltage Limits of the Op Amp

Use the macromodel of Fig. 10 to plot v_{OUT} as a function of v_{IN} for the noninverting, unity gain, voltage amplifier when v_{IN} is varied from -15V to +15V. The op amp parameters are $A_{vd}(0) = 100,000$, $R_{id} = 1\text{M}\Omega$, $R_{icm} = 100\text{M}\Omega$, $A_{vc}(0) = 10$, $R_o = 100\Omega$, $V_{OH} = -V_{OL} = 10\text{V}$, $V_{IH1} = V_{IH2} = -V_{IL1} = -V_{IL2} = 5\text{V}$.

Solution

The input file for this example is given below.

```
Example 4
VIN 1 0 DC 0
XOPAMP 1 2 2
NONLINOPAMP
.SUBCKT
NONLINOPAMP 1 2 3
RIC1 1 0 100MEG
RLIM1 1 4 0.1
D1 4 6 IDEALMOD
VIH1 6 0 5V
D2 7 4 IDEALMOD
VIL1 7 0 -5V
D4 9 5 IDEALMOD
VIL2 9 0 -5V
GAVD/RO 0 3 4 5 1000
GAVC1/2RO 0 3 4 0 0.05
GAVC2/2RO 0 3 5 0 0.05
RO 3 0 100
D5 3 10 IDEALMOD
VOH 10 0 10V
D6 11 3 IDEALMOD
VOL 11 0 -10V
.MODEL IDEALMOD D N=0.0001
.ENDS
.DC VIN -15 15 0.1
.PRINT V(2)
.PROBE
.END
```

Example 6.6-4 - Illustration of the Voltage Limits of the Op Amp - Continued


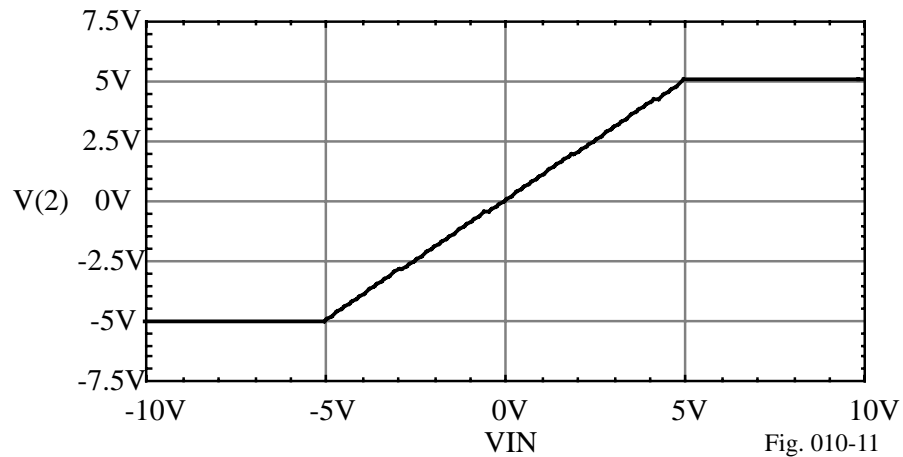



Figure 11 - Simulation results for Ex. 6.6-4.

Output Current Limiting

Technique:

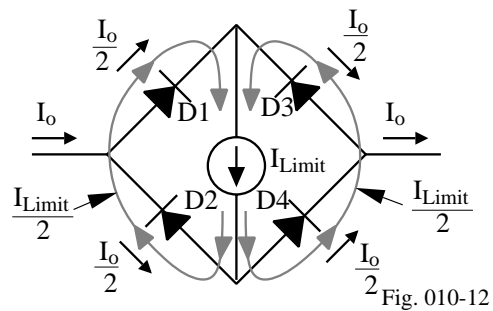

Macromodel for Output Voltage and Current Limiting:

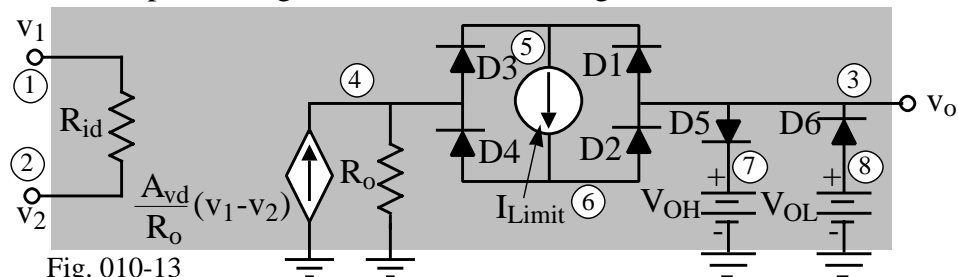

Example 6.6-5 - Influence of Current Limiting on the Amplifier Voltage Transfer Curve

Use the model above to illustrate the influence of current limiting on the voltage transfer curve of an inverting gain of one amplifier. Assume the $V_{OH} = -V_{OL} = 10V$, $V_{IH} = -V_{IL} = 10V$, the maximum output current is $\pm 20mA$, and $R_1 = R_2 = R_L = 500\Omega$ where R_L is a resistor connected from the output to ground. Otherwise, the op amp is ideal.

Solution

For the ideal op amp we will choose $A_{vd} = 100,000$, $R_{id} = 1M\Omega$, and $R_o = 100\Omega$ and assume one cannot tell the difference between these parameters and the ideal parameters. The remaining model parameters are $V_{OH} = -V_{OL} = 10V$ and $I_{Limit} = \pm 20mA$.

Example 5 - Influence of Current Limiting on the Amplifier Voltage Transfer Curve

```
VIN 1 0 DC 0
R1 1 2 500
R2 2 3 500
RL 3 0 500
XOPAMP 0 2 3 NONLINOPAMP
.SUBCKT NONLINOPAMP 1 2 3
RID 1 2 1MEGOHM
GAVD 0 4 1 2 1000
RO 4 0 100
D1 3 5 IDEALMOD
D2 6 3 IDEALMOD
D3 4 5 IDEALMOD
D4 6 4 IDEALMOD
ILIMIT 5 6 20MA
D5 3 7 IDEALMOD
VOH 7 0 10V
D6 8 3 IDEALMOD
VOL 8 0 -10V
.MODEL IDEALMOD D N=0.00001
.ENDS
.DC VIN -15 15 0.1
.PRINT DC V(3)
.PROBE
.END
```

Example 6.6-5 - Continued

The resulting plot of the output voltage, v_3 , as a function of the input voltage, v_{IN} is shown in Fig. 14.

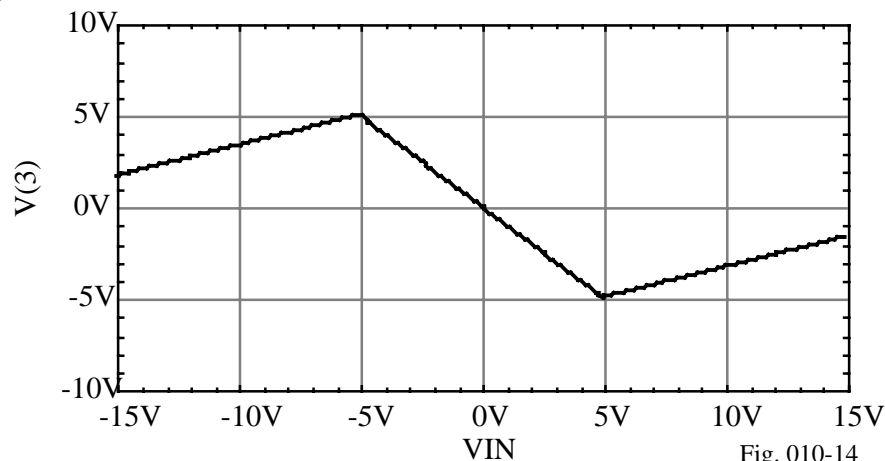


Fig. 010-14

Figure 14 - Results of Example 6.6-5.

Slew Rate Limiting (Time Dependency)

Slew Rate:

$$\frac{dv_o}{dt} = \frac{\pm I_{SR}}{C_1} = \text{Slew Rate}$$

Macromodel:

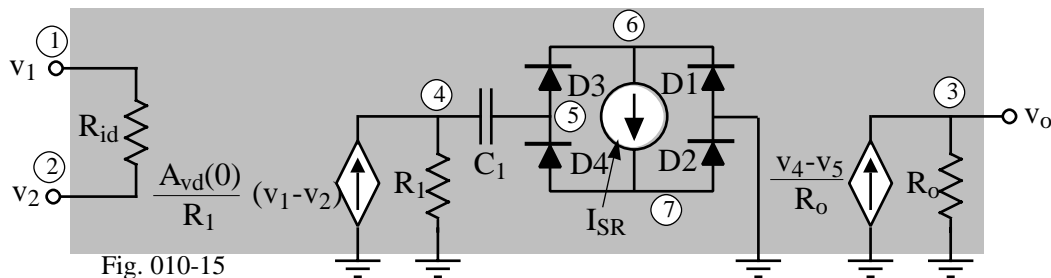


Fig. 010-15

Example 6.6-6 - Simulation of the Slew Rate of A Noninverting Voltage Amplifier

Let the gain of a noninverting voltage amplifier be 1. If the input signal is given as

$$v_{in}(t) = 10 \sin(4 \times 10^5 \pi t)$$

use the computer to find the output voltage if the slew rate of the op amp is $10\text{V}/\mu\text{s}$.

Solution

We can calculate that the op amp should slew when the frequency is 159kHz. Let us assume the op amp parameters of $A_{vd} = 100,000$, $\omega_1 = 100\text{rps}$, $R_{id} = 1\text{M}\Omega$, and $R_o = 100\Omega$. The simulation input file based on the macromodel of Fig. 15 is given below.

Example 6.6-6 - Simulation of slew rate limitation

```
VIN 1 0 SIN(0 10 200K)
XOPAMP 1 2 2 NONLINOPAMP
.SUBCKT NONLINOPAMP 1 2 3
RID 1 2 1 MEGOHM
GAVD/R1 0 4 1 2 1
R1 4 0 100KOHM
C1 4 5 0.1UF
D1 0 6 IDEALMOD
D2 7 0 IDEALMOD
D3 5 6 IDEALMOD
D4 7 5 IDEALMOD
ISR 6 7 1A
GVO/R0 0 3 4 5 0.01
RO 3 0 100
.MODEL IDEALMOD D N=0.0001
.ENDS
```


Example 6.6-6 - Continued

The simulation results are shown in Fig. 16. The input waveform is shown along with the output waveform. The influence of the slew rate causes the output waveform not to be equal to the input waveform.

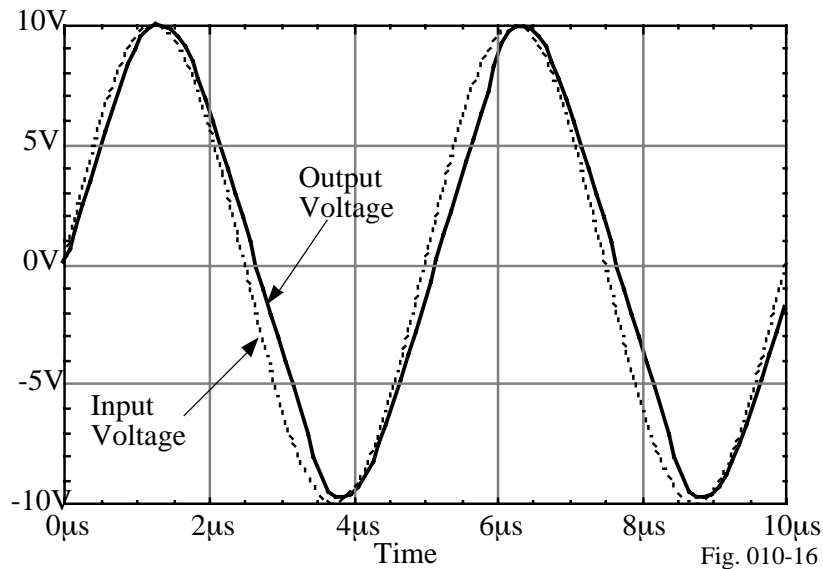


Figure 16 - Results of Ex. 6.6-6 on modeling the slew rate of an op amp.

SPICE Op Amp Library Models

Macromodels developed from the data sheet for various components.

Key Aspects of Op Amp Macromodels:

- Use the simplest op amp macromodel for a given simulation.
- All things being equal, use the macromodel with the min. no. of nodes.
- Use the SUBCKT feature for repeated use of the macromodel.
- Be sure to verify the correctness of the macromodels before using.
- Macromodels are a good means of trading simulation completeness for decreased simulation time.

SECTION 6.8 - SUMMARY

Topics

- Design of CMOS op amps
- Compensation of op amps
 - Miller
 - Self-compensating
 - Feedforward
- Two-stage op amp design
- Cascode op amps
- Simulation and measurement of op amps
- Macromodels of op amps

Chapter Objective

Purpose of this chapter is to introduce the simple two-stage op amp and the cascode op amp to illustrate the concepts of op amp design and to form the starting point for the improvement of performance of the next chapter.

Design Procedures

The design procedures given in this chapter are for the purposes of understanding and applying the design relationships and should not be followed rigorously as the designer gains experience.