

# Complete system testbech

Espen Klein Nilsen and  
Vegard Midtbøen

March 29, 2016

## 1 Report contents

This report contains a brief explanation of the different part in our project.

## 2 Structure

The overall structure of the system is seen in Figure 1.

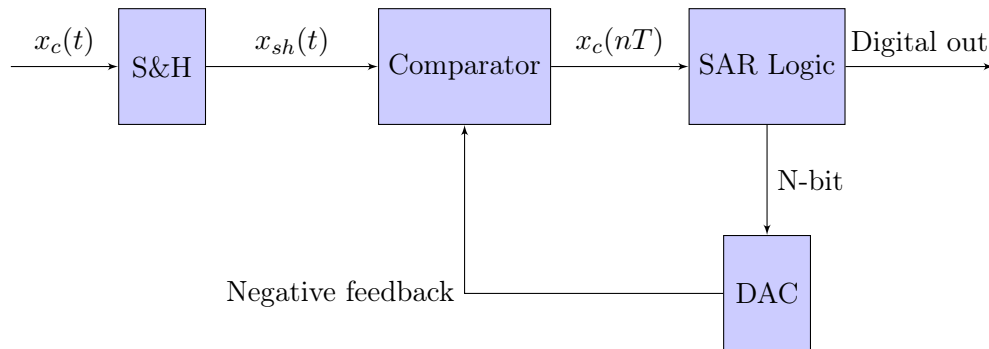


Figure 1: Block diagram

## 3 Schematic

We have not completed our research in circuits to use in this project. We have created schematics for some simple circuitis but we expect that some (or all) of the circuits is going to change.

### Schematic: SAR\_system

The SAR\_system is the complete schematic for the whole system. It consists of a sample and hold block, a comarator block, the SAR logic and the

digital-to-analog converter block. Figure 2 shows the schematic that has been created.

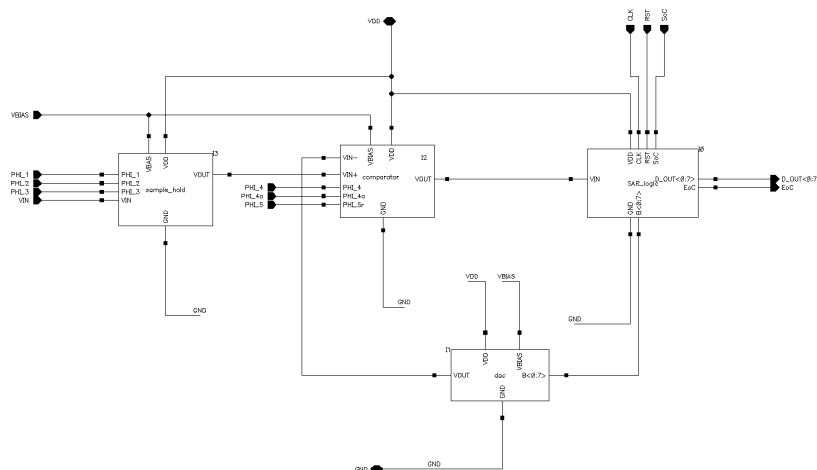


Figure 2: SAR system

Schematic: sample hold

The sample and hold (S/H) is based on a circuit provided by R. Jacob Baker in the book CMOS Mixed-Signal Circuit Design [**CMOS-baker**]. The implementation is a single-ended S/H implementation. When  $\phi_1$  and  $\phi_2$  is high,  $\phi_3$  is low, and the bottom plate of the hold capacitor is charged by the input signal, while the top plate is held to ground by the feedback around the op amp. When the  $\phi_2$  is turned off, its charge will be injected into the low impedance input, VIN, since the impedance looking into the left of the  $\phi_2$  switch is large.

This implementation has not yet been tested, and may therefore be changed during the project.

### Schematic: comparator

The design of the comparator is based on a design in the book Analog Integrated Circuit Design by Carusone, Johns and Martin [**Analog-integrated**].

 


Figure 3: Single-ended S/H operation [CMOS-baker]

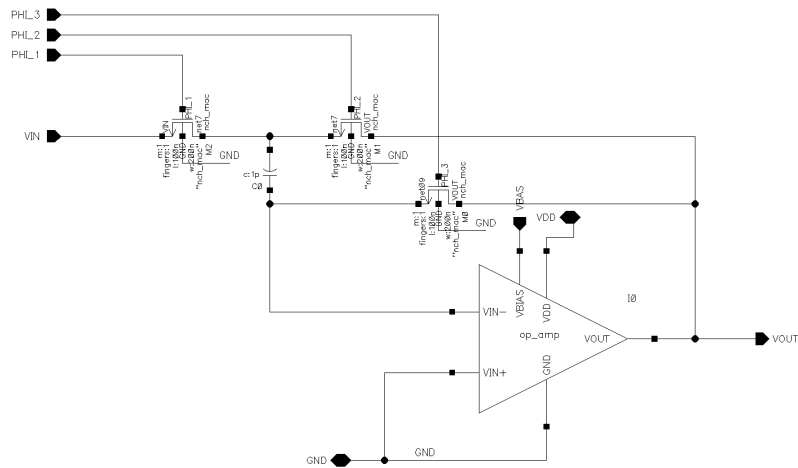


Figure 4: Sample and hold

**Schematic: SAR\_logic**

**Schematic: dac**

This DAC circuit is based on the R-2R ladder from the book Analog Integrated Circuit Design by Carusone, Johns and Martin [Analog-integrated].

**Schematic: op\_amp**

The op-amp circuit is ....

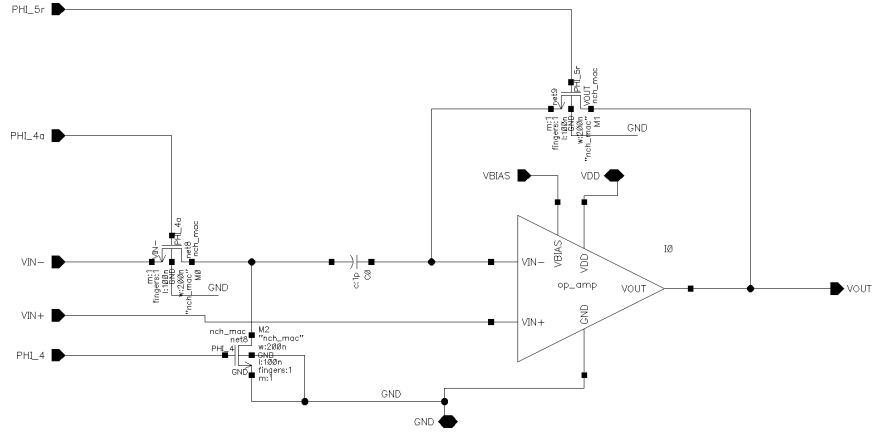


Figure 5: Comparator

 


Figure 6: DAC

## 4 Test bench

In this section a short overview of the different test-benches for our components is presented.

## **Schematic: SIM\_system**

This is a complete system test bench. Here all the different components come together to form the full SAR-DAC architecture. Testing on a system level is necessary to ensure that the circuit performs according to the interface the circuit provides to the outside world. This test scenario is quite hard to set up since many signals have to be timed to each other. The verification of the circuit is also challenging since many signals have to be considered. In order to manage this test we need to generate a test procedure with the specified stimuli and check the results to an expected pattern.

## **Schematic: SIM\_sample\_hold**

## **Schematic: SIM\_comparator**

## **Schematic: SIM\_SAR\_logic**

## **Schematic: SIM\_dac**

## **Schematic: SIM\_op\_amp**